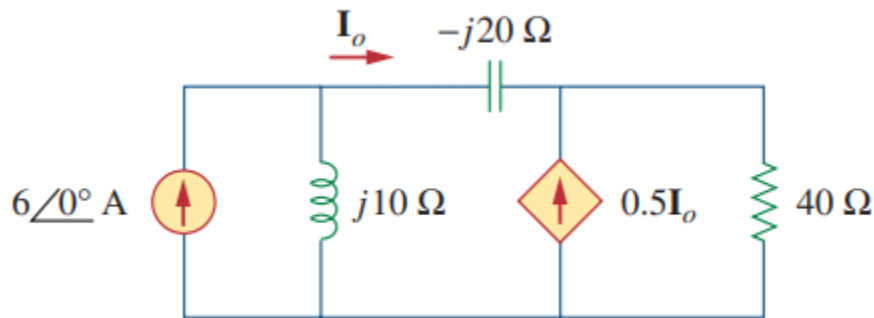



EENG 224, Quiz#1 Solution, 2022-23 FALL

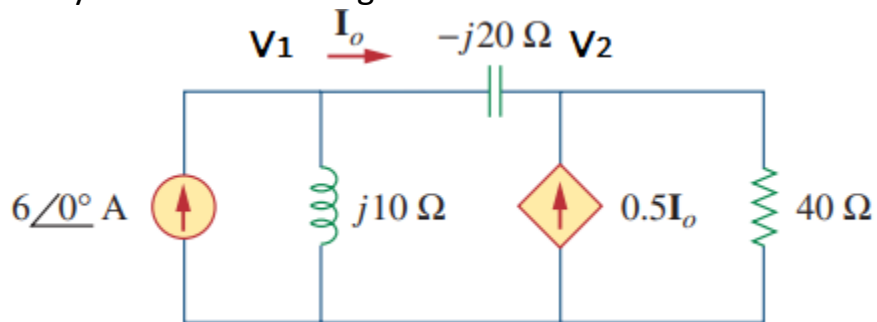Q.1 For the circuit shown below determine the average power absorbed by 40 Ω resistor.



Solution#1

By applying Nodal analysis to the following circuit



At node 1;

$$6 = \frac{V_1}{j10} + \frac{V_1 - V_2}{-j20}$$

Multiply both sides by 20 j and rearrange the above equation;

$$V_1 = j120 - V_2 \tag{1}$$

At node 2;

$$0.5I_o + I_o = \frac{V_2}{40}$$

But,
$$I_o = \frac{V_1 - V_2}{-j20}$$

Hence,
$$\frac{1.5(V_1 - V_2)}{-j20} = \frac{V_2}{40}$$

Multiply both sides by 40 j and rearrange

$$3V_1 = (3 - j)V_2 \tag{2}$$

Substituting (1) into (2),


$$j360 - 3V_2 - 3V_2 + jV_2 = 0$$

$$V_2 = \frac{j360}{6-j} = \frac{360}{37}(-1+j6) \quad \longrightarrow \quad I_2 = \frac{V_2}{40} = \frac{9}{37}(-1+j6)$$

$$P = \frac{1}{2} |I_2|^2 R = \frac{1}{2} \left(\frac{9}{\sqrt{37}} \right)^2 (40) = 43.78 \text{ W}$$

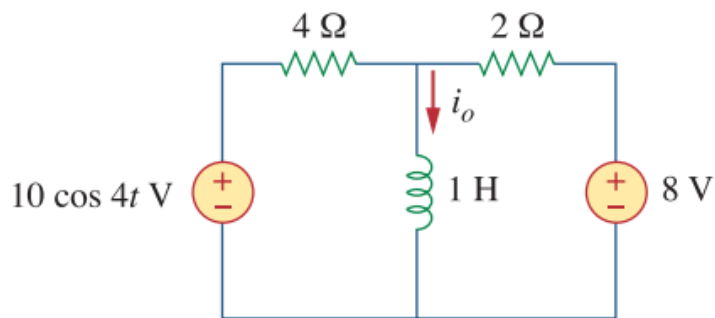
Q.2

By using principles of superposition find i_o in the circuit shown below.



Solution#2

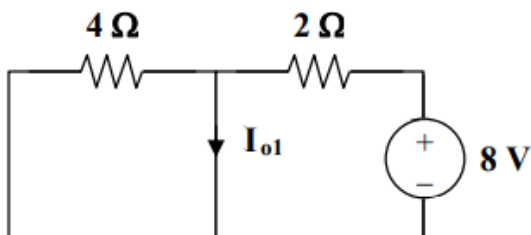
Let $i_o = i_{o1} + i_{o2}$, where i_{o1} is due to the dc source and i_{o2} is due to the ac source. For i_{o1} , consider the circuit shown below.




Clearly,

$$i_{o1} = 8/2 = 4 \text{ A}$$

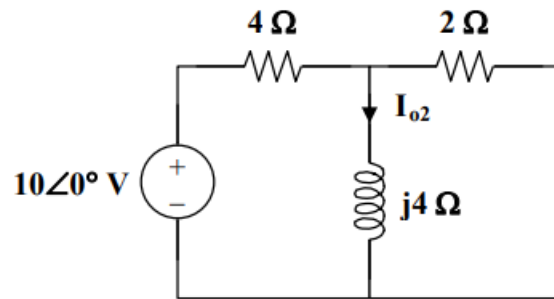For I_{o2} , consider the circuit shown below.



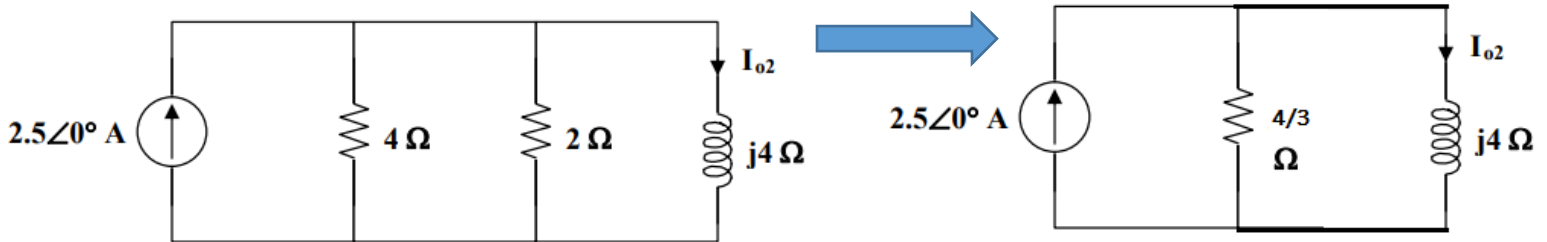If we transform the voltage source, we have the circuit shown below, where $(4\Omega \parallel 2\Omega) = 4/3 \Omega$.



By the current division principle,


$$\mathbf{I}_{o2} = \frac{4/3}{4/3 + j4} (2.5\angle 0^\circ) = 0.25 - j0.75 = 0.79\angle -71.56^\circ$$

Thus

$$i_o = i_{o1} + i_{o2} = [4 + 0.79 \cos(4t - 71.56^\circ)] \text{ A}$$

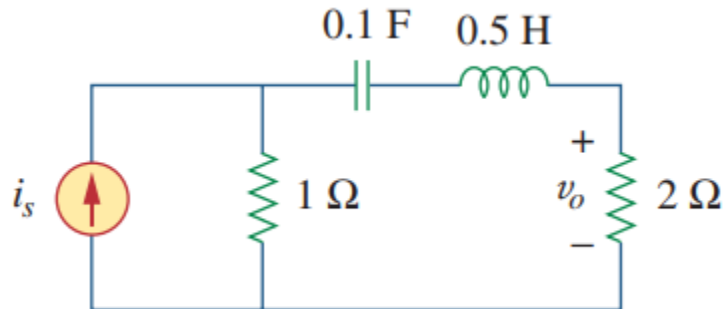Q.3

If the voltage v_0 across the $2\ \Omega$ resistor is $10 \cos 2t$ V, find i_s .




Solution#3

$$0.1\ \text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(0.1)} = -j5$$

$$0.5\ \text{H} \longrightarrow j\omega L = j(2)(0.5) = j$$

where $V_0 = 10 \angle 0^\circ$

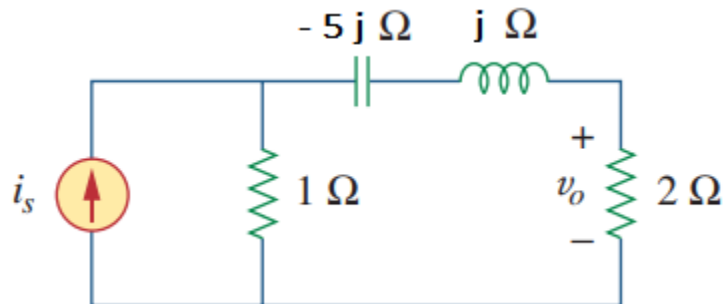

The current I through the $2\text{-}\Omega$ resistor is

$$\mathbf{I} = \frac{1}{1 - j5 + j + 2} \mathbf{I}_s = \frac{\mathbf{I}_s}{3 - j4}, \quad \text{where } \mathbf{I} = \frac{10}{2} \angle 0^\circ = 5$$

Therefore

$$\mathbf{I}_s = (5)(3 - j4) = 25 \angle -53.13^\circ$$

Hence

$$i_s = 25 \cos(2t - 53.13^\circ)\ \text{A}$$