

EASTERN MEDITERRANEAN UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT
CMPE224 DIGITAL LOGIC SYSTEMS
EXPERIMENTAL WORK #4
COUNTERS IN VeriLog HDL

OBJECTIVES:

This laboratory work aims to introduce a practical work on the design of Counters from architectural and behavioral descriptions. The architectural description covers both the schematic and the software implementation of circuits designed through the conventional design procedure. The behavioral descriptions cover the implementation using state transition diagrams.

Important Note: *For each of the following experimental tasks (in each phase), open a new project to avoid compilation errors due to multiple use of components within the same project's files.*


Phase 1: Schematic-Entry

Assume that we want to design the following multi-function counter that is controlled by two control inputs S1 and S0 as follows:

Mode Control		Register Operation
S1	S0	
0	0	<i>Count Up</i>
0	1	<i>Count Down</i>
1	0	<i>Parallel Load</i>
1	1	<i>No Change</i>

The schematic circuit corresponding to this multi-function counter is given below:

1.1. Draw the circuit of this multifunction counter, compile and simulate it in VeriLog HDL environment and verify its mode of operations. Adjust and apply appropriate waveforms to observe different function modes easily.

 

Phase 2: Implementing the Architectural Design of Multi-Function Counter in Verilog HDL

Enter the following architectural Verilog code of multifunction counter design into Quartus Lite development suite. Compile and simulate your code to verify its correctness.

/* Multifunction counter controlled by two control inputs S1 and S0 as follows:

S1	S0	Operation Mode
0	0	Count up
0	1	Count down
1	0	Parallel load
1	1	No change

*/

```
module MultiFuncCounter_Arch(CLK, Clear, S, PL, Q);
    input CLK, Clear;
    input [1:0] S;
    input [3:0] PL;          // Parallel load
    output reg [3:0]Q;      // Counter outputs

    wire [3:0] W;
    wire [3:0] QT;

    MUX_4_1 m1(W[0],S[1],S[0],I31,I21,I11,I01);
    MUX_4_1 m2(W[1],S[1],S[0],I32,I22,I12,I02);
    MUX_4_1 m3(W[2],S[1],S[0],I33,I23,I13,I03);
    MUX_4_1 m4(W[3],S[1],S[0],I34,I24,I14,I04);

    T_FF t1(QT[0],W[0],CLK,Clear);
    T_FF t2(QT[1],W[1],CLK,Clear);
    T_FF t3(QT[2],W[2],CLK,Clear);
    T_FF t4(QT[3],W[3],CLK,Clear);

    assign

        I31=1'b0,
        I21=QT[0]^PL[0],
        I11=1'b1,
        I01=1'b1,

        I32=1'b0,
        I22=QT[1]^PL[1],
        I12=QT[0],
        I02=~QT[0],

        I33=1'b0,
        I23=QT[2]^PL[2],
        I13=QT[1]&QT[0],
        I03=~QT[1] & ~QT[0],

        I34=1'b0,
        I24=QT[3]^PL[3],
        I14=QT[2]&QT[1]&QT[0],
```

```
I04=~QT[2] & ~QT[1] & ~QT[0];
```

```
always  
  Q <= QT;
```

```
endmodule
```

```
module MUX_4_1(Y,S1,S0,I3,I2,I1,I0);  
  input S1,S0,I3,I2,I1,I0;  
  output reg Y;
```

```
always @(S1,S0,I3,I2,I1,I0)  
begin  
  if (S1==0 & S0==0)  
    Y=I0;  
  else if (S1==0 & S0==1)  
    Y=I1;  
  else if (S1==1 & S0==0)  
    Y=I2;  
  else if (S1==1 & S0==1)  
    Y=I3;
```

```
end
```

```
endmodule
```

```
module T_FF(QT,T,CLK,CLR);  
  input T,CLK,CLR;  
  output reg QT;
```

```
always @ (posedge CLK)  
  if (CLR == 1'b1)  
    QT <= 1'b0;  
  else  
    QT <= T ^ QT;
```

```
endmodule
```

HOMEWORK #4 : (Behavioral Description of a Multi-function Counter)

Behavioral VeriLog code of the above described multifunction counter is given below:

```
/* Behavioral description of a multifunction counter in veriLog HDL
s1 s0 =00 Count up
S1 S0 =01 Count down
S1 S0 =10 Parallel load
S1 S0 =11 No change
*/
```

```
module MultiFunctCounter_Behav(CLK, Clear, S, PL, Q);
    input CLK, Clear;
    input [1:0] S;
    input [3:0] PL;          // Parallel load
    output reg [3:0] Q;      // Counter outputs
    reg[3:0] QT;

    always @ (posedge CLK)
    begin
        if (Clear == 1)
            QT <= 4'b0000;
        else if (S[1]==0 & S[0]==0) // Count up
            QT <= QT+1;
        else if (S[1]==0 & S[0]==1) // Count down
            QT <= QT-1;
        else if (S[1]==1 & S[0]==0) // Parallel load
        begin
            QT[3] <= PL[3]; QT[2] <= PL[2];
            QT[1] <= PL[1]; QT[0] <= PL[0];
        end
        else if (S[1]==1 & S[0]==1)
        begin
            QT=QT;
        end
    end
    always
        Q <= QT;
Endmodule
```

Modify the above-given behavioral code to design a 4-bit multifunction counter that operates as follows:

Enable	S1	S0	Operation Mode
0	x	x	<i>No change</i>
1	0	0	<i>Complement</i>
1	0	1	<i>Count up by two</i>
1	1	0	<i>Count down by two</i>
1	1	1	<i>Shift left</i>

Submit your homework at the beginning of the 5-th experimental work.

Prepared by Assoc. Prof. Dr. Adnan ACAN