

EENG224 Homework I

1. Find $i_x(t)$ if $v_s(t) = 20 \cos(100t - 40^\circ)$ in the circuit of Fig.1


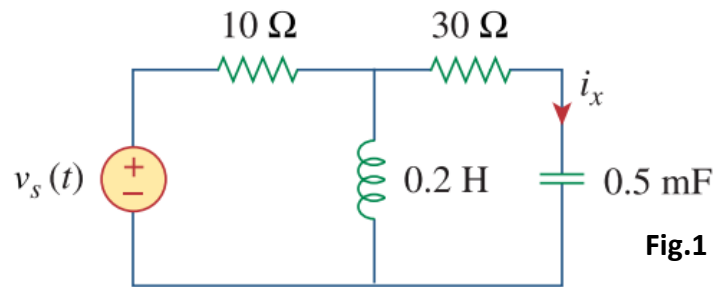


Fig.1

Soln.:

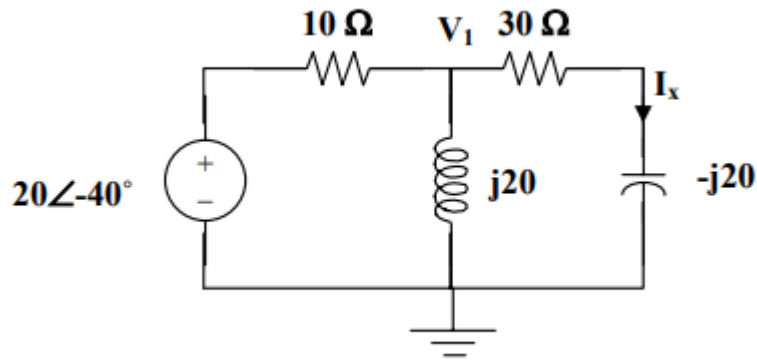Converting the circuit to the frequency domain, we get:



We can solve this using nodal analysis.

$$\frac{V_1 - 20\angle -40^\circ}{10} + \frac{V_1 - 0}{j20} + \frac{V_1 - 0}{30 - j20} = 0$$


$$V_1(0.1 - j0.05 + 0.02307 + j0.01538) = 2\angle -40^\circ$$

$$V_1 = \frac{2\angle 40^\circ}{0.12307 - j0.03462} = 15.643\angle -24.29^\circ$$

$$I_x = \frac{15.643\angle -24.29^\circ}{30 - j20} = 0.4338\angle 9.4^\circ$$

$$i_x = 0.4338 \cos(100t + 9.4^\circ) \text{ A}$$

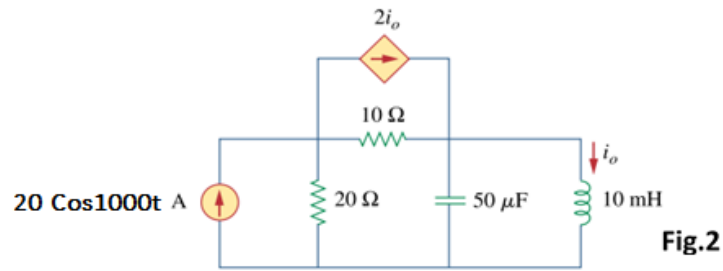2. By nodal analysis, find $i_o(t)$ in the circuit of Fig.2




Soln.:

$$20 \cos(1000t) \longrightarrow 20 \angle 0^\circ, \quad \omega = 1000$$

$$10 \text{ mH} \longrightarrow j\omega L = j10$$

$$50 \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10^3)(50 \times 10^{-6})} = -j20$$

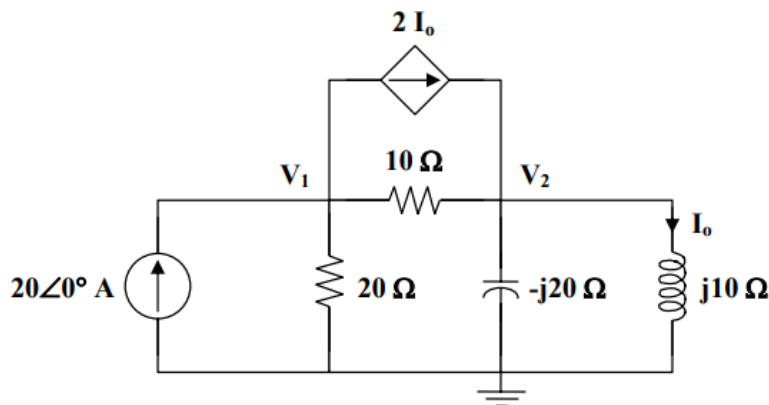Converting the circuit to the frequency domain, we get:



At node 1,

$$20 = 2I_o + \frac{V_1}{20} + \frac{V_1 - V_2}{10}, \quad \text{where } I_o = \frac{V_2}{j10}$$

$$20 = \frac{2V_2}{j10} + \frac{V_1}{20} + \frac{V_1 - V_2}{10}$$

$$400 = 3V_1 - (2 + j4)V_2 \quad (1)$$

At node 2,

$$\frac{2V_2}{j10} + \frac{V_1 - V_2}{10} = \frac{V_2}{-j20} + \frac{V_2}{j10}$$

$$j2V_1 = (-3 + j2)V_2$$

or

$$V_1 = (1 + j1.5)V_2 \quad (2)$$

Substituting (2) into (1),


$$400 = (3 + j4.5)V_2 - (2 + j4)V_2 = (1 + j0.5)V_2$$

$$V_2 = \frac{400}{1 + j0.5}$$

$$I_o = \frac{V_2}{j10} = \frac{40}{j(1 + j0.5)} = 35.74 \angle -116.6^\circ$$

Therefore, $i_o(t) = \underline{35.74 \cos(1000t - 116.6^\circ) \text{ A}}$

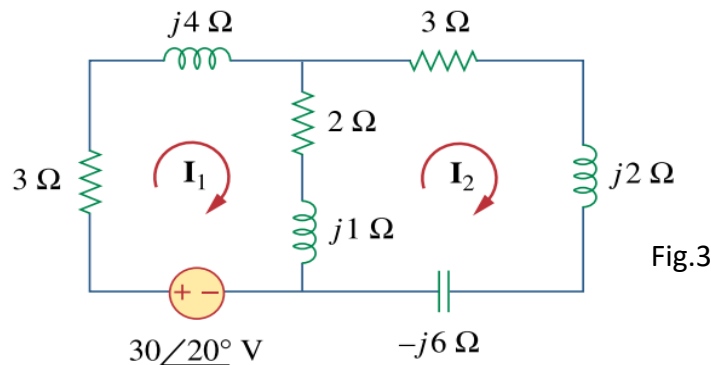3. By using mesh analysis, find I_1 and I_2 in the circuit in Fig. 3.



Soln.:

For mesh 1,

$$(5 + j5)I_1 - (2 + j)I_2 - 30\angle 20^\circ = 0$$

$$30\angle 20^\circ = (5 + j5)I_1 - (2 + j)I_2 \quad (1)$$

For mesh 2,

$$(5 + j3 - j6)I_2 - (2 + j)I_1 = 0$$

$$0 = -(2 + j)I_1 + (5 - j3)I_2 \quad (2)$$

From (1) and (2),

$$\begin{bmatrix} 30\angle 20^\circ \\ 0 \end{bmatrix} = \begin{bmatrix} 5 + j5 & -(2 + j) \\ -(2 + j) & 5 - j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta = 37 + j6 = 37.48 \angle 9.21^\circ$$


$$\Delta_1 = (30\angle 20^\circ)(5.831 \angle -30.96^\circ) = 175 \angle -10.96^\circ$$

$$I_1 = \frac{\Delta_1}{\Delta} = \underline{4.67 \angle -20.17^\circ \text{ A}}$$

$$\Delta_2 = (30\angle 20^\circ)(2.356 \angle 26.56^\circ) = 67.08 \angle 46.56^\circ$$


$$I_2 = \frac{\Delta_2}{\Delta} = \underline{1.79 \angle 37.35^\circ \text{ A}}$$

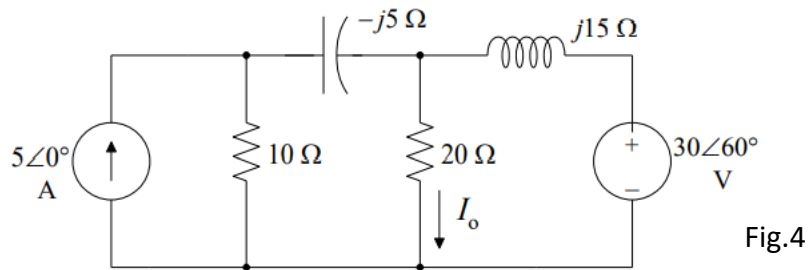4. In the circuit shown in Fig.4, use source transformation to find the current I_o




Soln.:

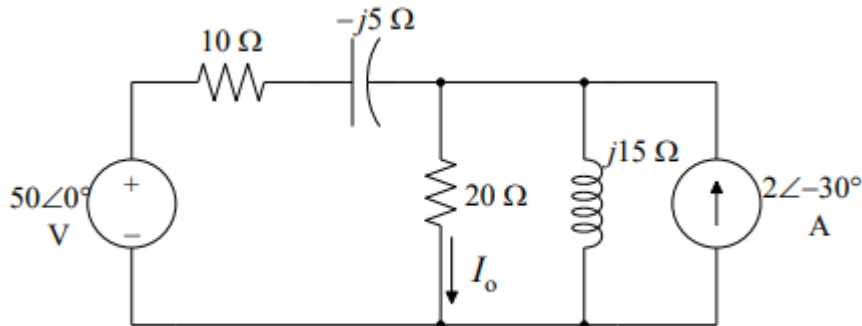Transform the $5\angle 0^\circ$ A current source into a voltage source, and the $30\angle 60^\circ$ V source into a current source:



Transform the voltage source $50\angle 0^\circ$ V source into a current source; then combine the current sources and the impedances in parallel:

$$\frac{50}{10 - j5} = 4 + j2$$

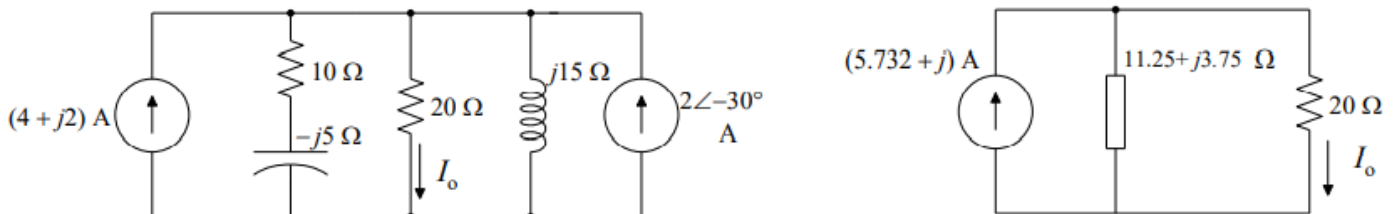

$$j15 \parallel (10 - j5) = \frac{j15(10 - j5)}{10 + j10} = 11.25 + j3.75$$


$$4 + j2 + 2\angle -30^\circ = 5.732 + j$$

By current division:

$$I_o = \frac{11.25 + j3.75}{31.25 + j3.75} \times (5.732 + j) \text{ A}$$


$$I_o = 2.04 + j0.8031 = 2.1923\angle 21.49^\circ \text{ A}$$

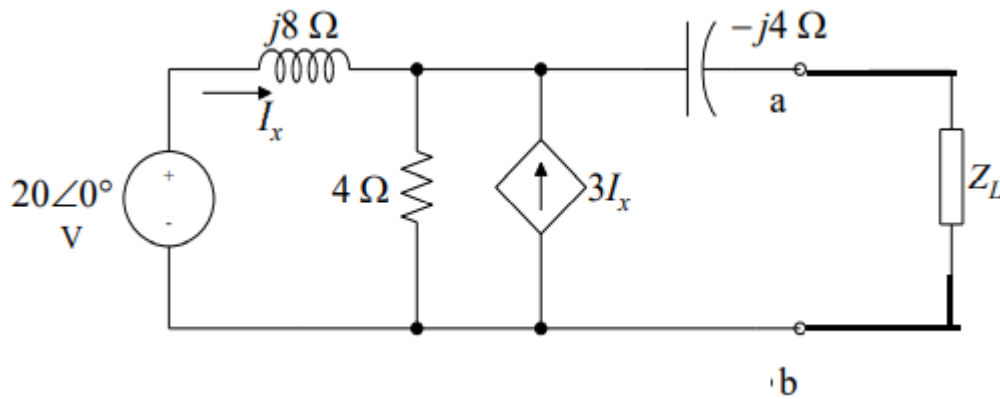5. Determine the load impedance Z_L that maximizes the average power drawn from the circuit shown in Fig.5. What is the maximum average power?



Soln.:

V_{Th} :

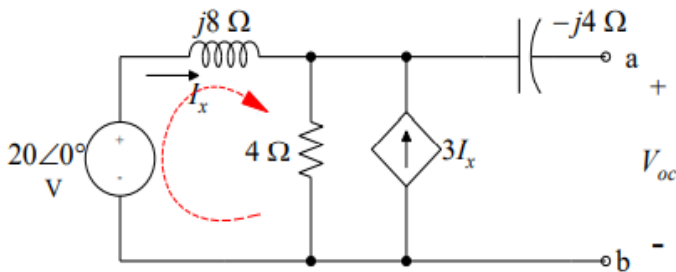


KVL for the loop:

$$-20\angle 0^\circ + j8I_x + 4(4I_x) = 0 \Rightarrow I_x = \frac{20\angle 0^\circ}{16 + j8}$$

$$V_{oc} = 4(4I_x) = 16I_x = \frac{16}{16 + j8} 20\angle 0^\circ$$

$$= 16 - j8 \text{ V} = 17.89\angle -26.57^\circ \text{ V}$$

Z_{Th} :

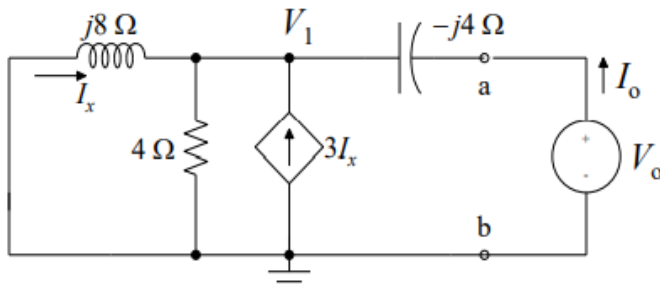

KCL eqn. at node V_1 :

$$\frac{V_1}{j8} + \frac{V_1}{4} + \frac{V_1 - V_o}{-j4} - 3I_x = 0$$

$$I_x = -\frac{V_1}{j8}$$

$$V_1 = -\frac{V_o}{1+j} \Rightarrow I_o = \frac{V_o - V_1}{-j4} = \frac{2+j}{(-j4)(1+j)} V_o \Rightarrow Z_{Th} = \frac{V_o}{I_o} = 0.8 - j2.4 \Omega$$

The Load impedance draws the maximum power from the circuit when

$$Z_L = Z_{TH}^* = 0.8 + j2.4 \Omega$$

The maximum average power is $P_{max} = \frac{|V_{TH}|^2}{8R_{TH}} = \frac{17.89^2}{8 \times 0.8} = 50 \text{ W}$