

EENG224 Homework I

Due on 16 th of November 2022

1. Find $i_x(t)$ if $v_s(t) = 20 \cos(100t - 40^\circ)$ in the circuit of Fig.1

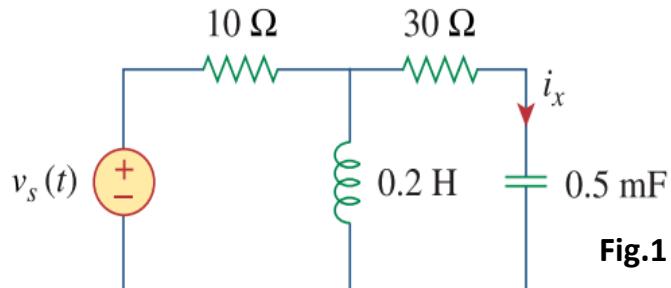


Fig.1

2. By nodal analysis, find $i_o(t)$ in the circuit of Fig.2

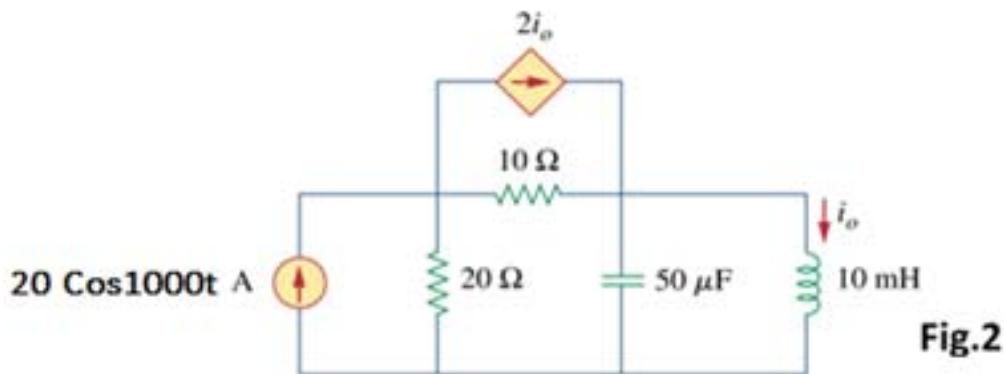


Fig.2

3. By using mesh analysis, find I_1 and I_2 in the circuit in Fig. 3.

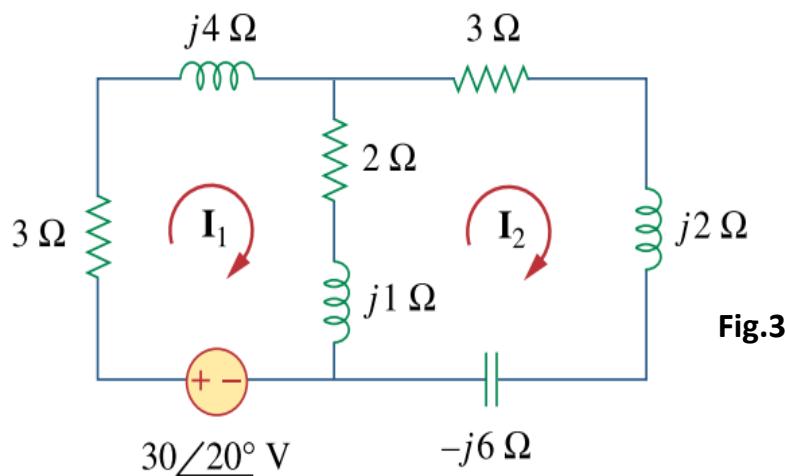


Fig.3

4.

In the circuit shown in Fig.4, use source transformation to find the current I_o

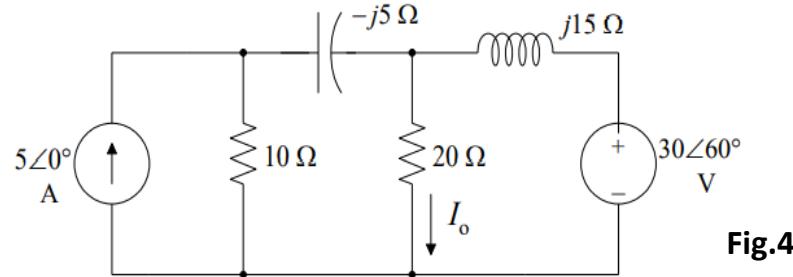


Fig.4

5.

Determine the load impedance Z_L that maximizes the average power drawn from the circuit shown in Fig.5. What is the maximum average power?

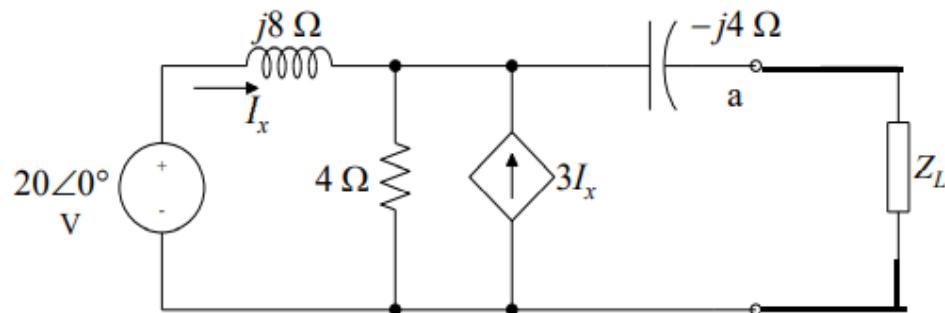


Fig.5