



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG224 *Circuit Theory II*

FALL 2022-2023

Instructor: A. Doğanalp

MIDTERM EXAM
November 23, 2022

Duration : 100 minutes

Number of Problems: 4


Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	

Problem		Points
1		15
2		25
3		30
4		30
TOTAL		100

PROBLEM 1

If $i_s = 5 \cos(10t + 40^\circ)$ A in the circuit, find i_o .

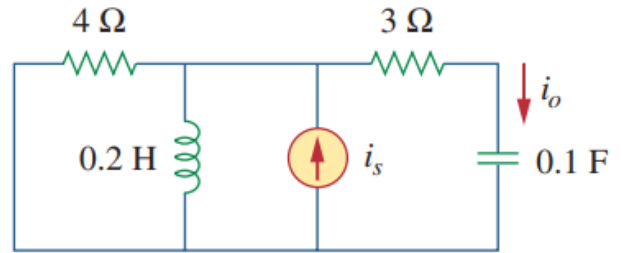**SOLUTION:**

Step 1: Transfer from time domain to phasor domain.

$$i_s = 5 \cos(10t + 40^\circ) \longrightarrow \mathbf{I}_s = 5 \angle 40^\circ$$

$$0.1 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10)(0.1)} = -j$$

$$0.2 \text{ H} \longrightarrow j\omega L = j(10)(0.2) = j2$$

Step 2:

$$\text{Let } \mathbf{Z}_1 = 4 \parallel j2 = \frac{j8}{4 + j2} = 0.8 + j1.6 \quad \text{and} \quad \mathbf{Z}_2 = 3 - j$$

Step 3: By applying current division rule

$$\mathbf{I}_o = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}_s = \frac{0.8 + j1.6}{3.8 + j0.6} (5 \angle 40^\circ)$$

$$\mathbf{I}_o = \frac{(1.789 \angle 63.43^\circ)(5 \angle 40^\circ)}{3.847 \angle 8.97^\circ} = 2.325 \angle 94.46^\circ$$


Step 4:

$$\text{Thus, } i_o(t) = 2.325 \cos(10t + 94.46^\circ) \text{ A}$$

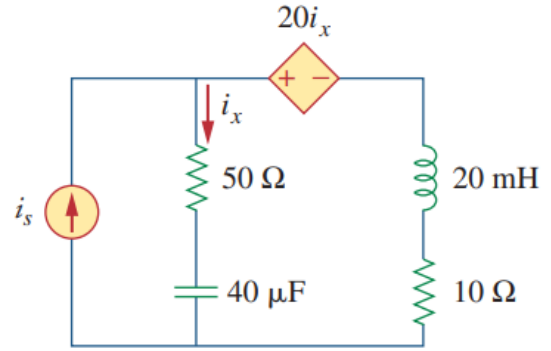PROBLEM 2

For the circuit shown $i_s = 6 \cos(10^3 t)$ A.

Find the average power absorbed by 50 Ω resistor.




SOLUTION:

Step 1: Transfer from time domain to phasor domain.

$$20 \text{ mH} \longrightarrow j\omega L = j10^3 \times 20 \times 10^{-3} = j20$$

$$40 \mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j10^3 \times 40 \times 10^{-6}} = -j25$$

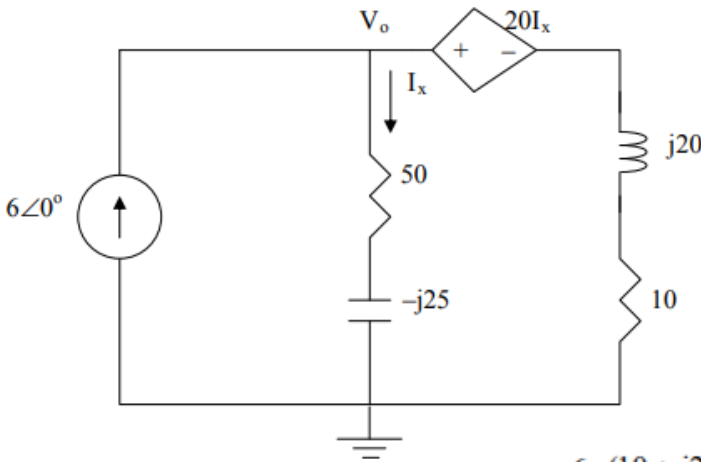Step 2: Apply Nodal analysis to the circuit below.



$$\frac{V_o - 20I_x}{10 + j20} + \frac{V_o}{50 - j25} = 6$$

$$\text{But } I_x = \frac{V_o}{50 - j25}$$

Substituting this and solving for V_o leads

$$6 (10 + j20) (50 - j25) = V_o [10 + j20 + 50 - j25 - 20]$$

$$\left(\frac{1}{10 + j20} - \frac{20}{(10 + j20)(50 - j25)} + \frac{1}{50 - j25} \right) V_o = 6$$

$$\frac{6 (10 + j20) (50 - j25)}{40 - j5} = V_o \quad \longrightarrow \quad V_o = 186.05 \angle 43.99^\circ \text{ volts.}$$

$$I_x = \frac{186.05 \angle 43.99^\circ}{(50 - j25)} = \frac{186.05 \angle 43.99^\circ}{55.9 \angle -26.57^\circ} = 3.328 \angle 70.55^\circ \text{ A}$$


Step 3: We can now calculate the average power absorbed by the 50-Ω resistor.

$$P_{avg} = \frac{1}{2} |I_x|^2 R$$


$$P_{avg} = [(3.328)^2/2] \times 50 = 276.8 \text{ W.}$$

PROBLEM 3

In the circuit shown below, find *the value of Z_L* that will absorb the maximum power and the *value of the maximum power*

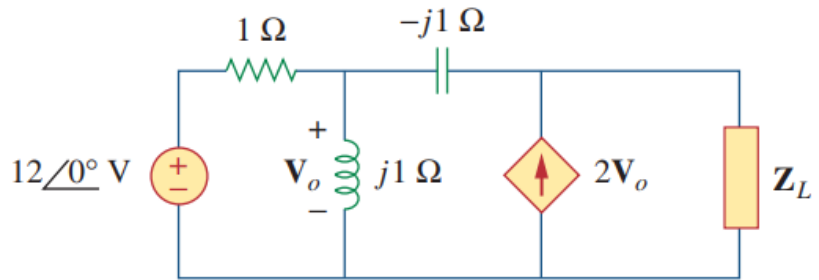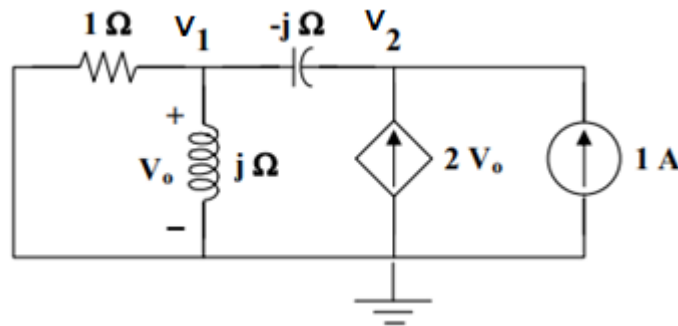**SOLUTION:**

Step 1: To find Z_{eq} insert a 1 A (arbitrary number) current source at the load terminals as shown below.



At node 1,

$$\frac{V_o}{1} + \frac{V_o}{j} = \frac{V_2 - V_o}{-j} \longrightarrow V_o = jV_2 \quad (1)$$

At node 2,

$$1 + 2V_o = \frac{V_2 - V_o}{-j} \longrightarrow 1 = jV_2 - (2 + j)V_o \quad (2)$$


Substituting (1) into (2),

$$1 = jV_2 - (2 + j)(j)V_2 = (1 - j)V_2$$

$$V_2 = \frac{1}{1 - j}$$

$$Z_{eq} = \frac{V_2}{1} = \frac{1 + j}{2} = 0.5 + j0.5 \quad \longrightarrow \quad Z_L = Z_{eq}^* = [0.5 - j0.5] \Omega$$

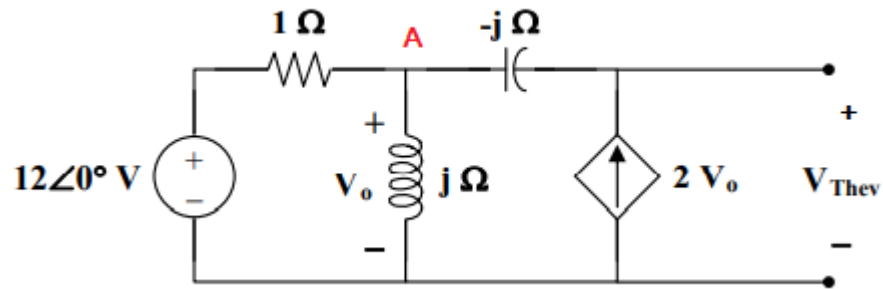Step 2: To obtain V_{Thev} consider the circuit shown below.



Apply KCL to node A $\Rightarrow -2V_o + \frac{V_o - 12}{1} + \frac{V_o}{j} = 0 \Rightarrow V_o = \frac{-12}{1+j}$

$$-V_o - (-j \times 2V_o) + V_{Th} = 0$$

$$V_{Thev} = (1-j2)V_o = \frac{(-12)(1-j2)}{1+j} = \frac{-12 + j24}{1+j} = \frac{26.83 \angle 116.57^\circ}{1.41 \angle 45^\circ} = 19.02 \angle 71.57 \text{ volt}$$

$$P_{\max} = \frac{|V_{Th}|^2}{8R_{Th}} \Rightarrow P_{\max} = \frac{|19.02|^2}{8 \times 0.5 \text{ Ohm}}$$

$$P_{\max} = 90.44 \text{ Watt}$$

PROBLEM 4


In the circuit shown, a feeder with impedance $Z_f = 0.1 + j0.5 \Omega$ supplies power to the loads **L1** and **L2**. The voltage across the loads $V_L = 250 \angle 0^\circ$ V rms. The loads absorb the powers given below.

L1: 8 kW, power factor 0.8, leading.

L2: 20 kVA, power factor 0.6, lagging.

Find

- (a) The total complex power absorbed by the loads. (10 pts)
- (b) The current I_s and the voltage of the source V_s . (6 pts)
- (c) The average power loss on the feeder. (4 pts)
- (d) A capacitor is to be connected across the loads to raise the power factor of the loads to 1.0. Taking the frequency of the source to be 50 Hz, find the value C of the capacitance required. (10 pts)

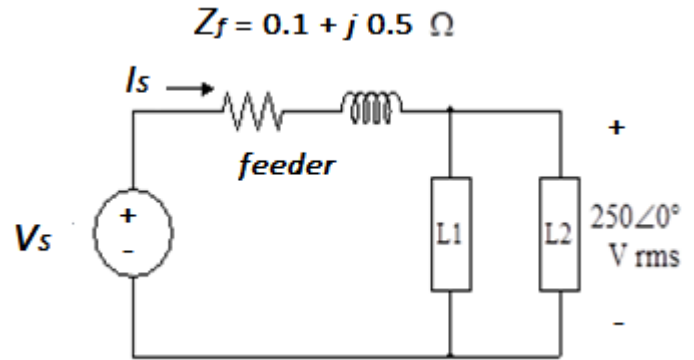**SOLUTION:**

- (a) **Reactive power absorbed by L1:**

$$\theta_1 = \cos^{-1}(0.8) = 36.87^\circ, \quad Q_1 = -8 \times \tan(36.87^\circ) = -6 \text{ kVAR}$$

$$\longrightarrow S_1 = (8 - j6) \text{ kVA}$$

Average and reactive power absorbed by L2;

$$\theta_2 = \cos^{-1}(0.6) = 53.13^\circ \quad \sin(\theta_2) = 0.8$$

$$\longrightarrow S_2 = 20(0.6 + j0.8) = (12 + j16) \text{ kVA}$$

$$S_{\text{total}} = (20 + j10) \text{ kVA}$$

- (b)

$$S_{\text{total}} = V_L I_s^* \Rightarrow I_s = \left(\frac{S_{\text{total}}}{V_L} \right)^* = \frac{20000 - j10000}{250} = 80 - j40 \text{ A} = 89.44 \angle -26.57^\circ \text{ A}$$

$$V_s = Z_f I_s + V_L = (0.1 + j0.5)(80 - j40) + 250 = 278 + j36 \text{ V} = 280.32 \angle 7.38^\circ \text{ V}$$

- (c) $P_{\text{loss}} = 0.1 \times |I_s|^2 = 0.1 \times 89.44^2 = 799.95 \text{ W}$

- (d) The capacitor must generate the reactive power 10 kVAR \Rightarrow

$$\frac{|V_L|^2}{X_C} = 10^4 \Rightarrow X_C = \frac{250^2}{10^4} = 6.25 \Omega = \frac{1}{2\pi fC} \Rightarrow C = \frac{1}{100\pi \times 6.25} = 509.3 \mu\text{F}$$