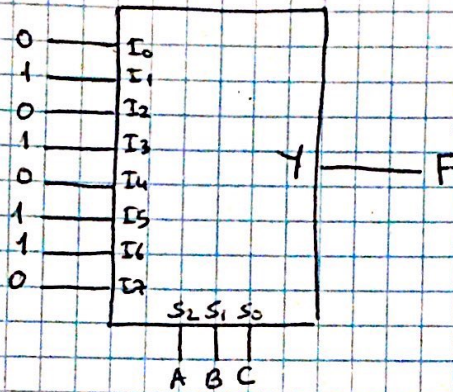


### Implementing Boolean functions with MUXs:

Any Boolean function can be implemented with MUXs. If a function has  $n$  input variables, it can be implemented by using  $2^n$ -to-1 MUX. The function should be expressed in sum of minterms form.

Example: Implement the function  $F(A,B,C) = \sum(1,3,5,6)$  using MUX.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0



However, it is possible to generate any function of  $n+1$  variables with a  $2^n$ -to-1 multiplexer. We connect  $n$  of the variables to the selection lines and the remaining single variable is used for the inputs of the MUX.

Example: Implement the previous function with 4-to-1 MUX.

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	①	2	③
$A$	4	⑤	⑥	7
MUX inputs	0	1	A	$A'$

↙ implementation table

- 1- Express  $F$  in sum of minterms
- 2- Use the leftmost variable (for the inputs of the MUX and the remaining  $n$  variables are connected to the selection lines  $S_{n-1}, S_{n-2}, \dots, S_0$ )   
 → (Assume it is A)
- 3- List the inputs of the MUX and under them list all the minterms in two rows (1st row corresponds to the complement of the leftmost variable ( $A'$ ) and 2nd row corresponds to the leftmost variable ( $A$ ))
- 4- Circle the minterms of the function   
 Apply 0 of the two minterms.



