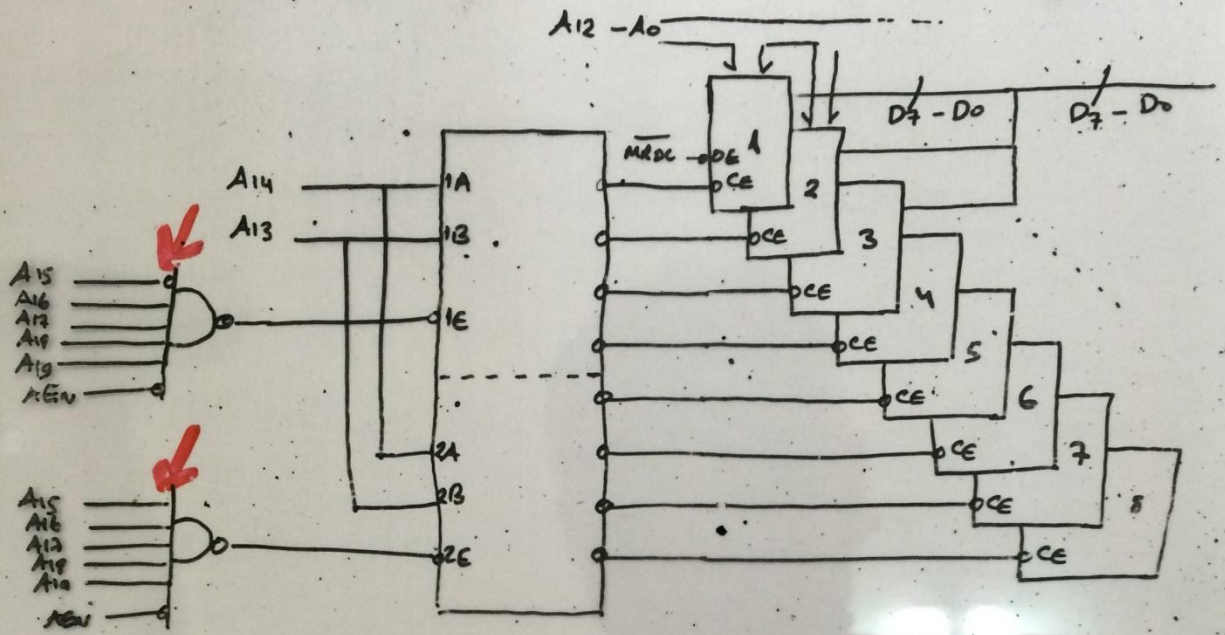




Q.1) 8 (8Kx8) EPROMS in the address range: F0000-FFFF using 74LS139




Q.2) 6 (8Kx8) EPROMS and 1 (16Kx8) EPROM in the address range F0000H - FFFFFH using NAND gates.

EPROM1: F0000 - F1FFF

i.e. 

1111	0000	0000	0000	0000
1111	0001	1111	1111	1111

 in-chip addressing (A12-A0)

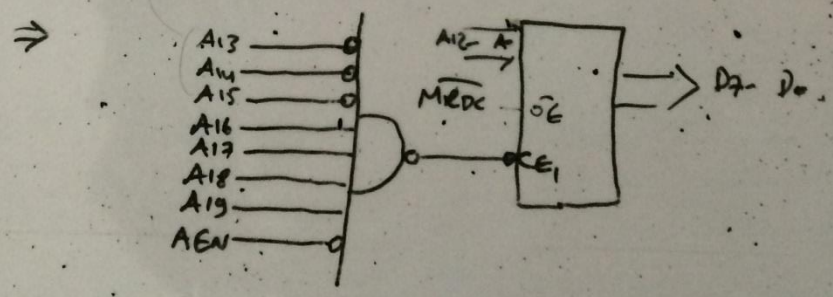




Similarly,

EPROM2: F2000 - F3FFF

i.e

1111	0010	0000	0000	0000
1111	0011	1111	1111	1111

in-chip addressing

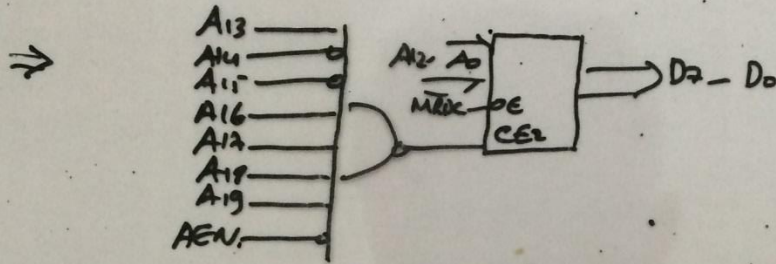


EPROM7: (16K) FC000 - FFFFF


i.e

1111	1100	0000	0000	0000
1111	1111	1111	1111	1111

in-chip addressing (A13 - A0)

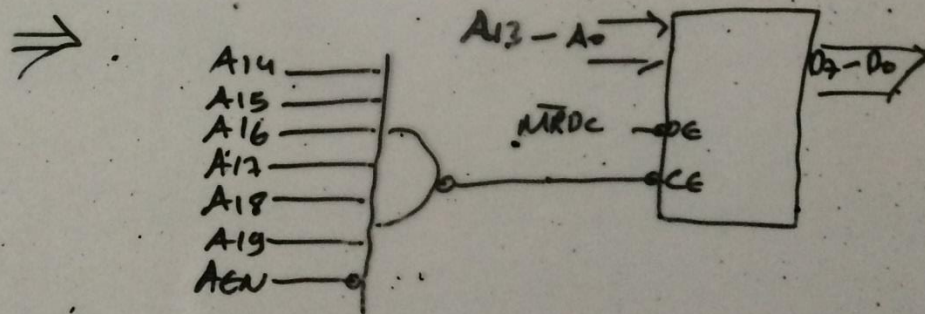

(Q.4) Repeat Q.2 using 74LS 139 decoder

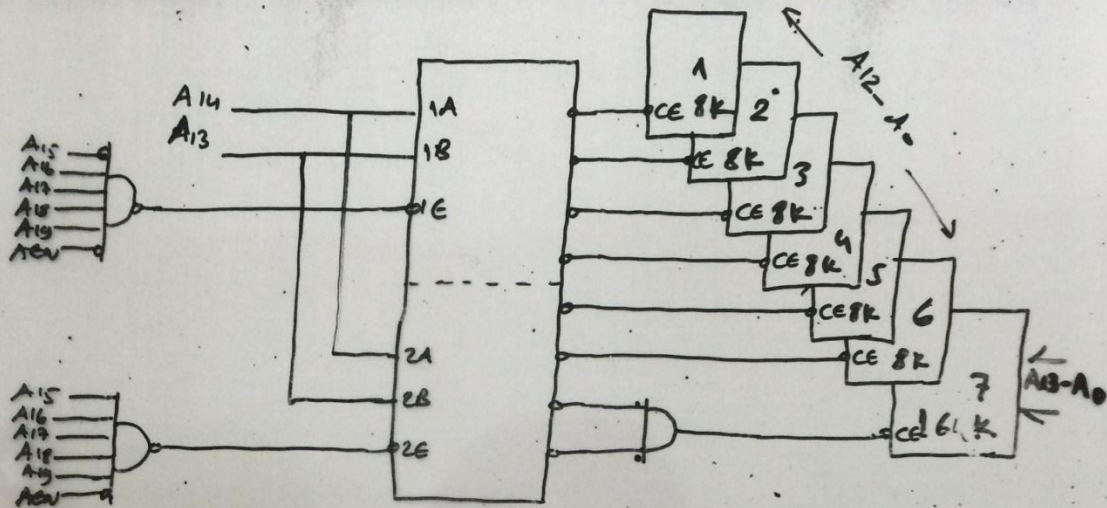




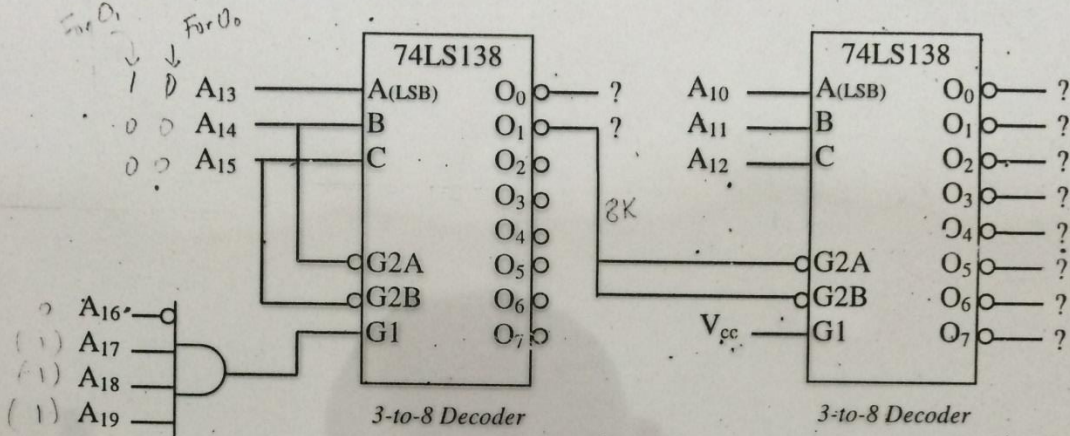**Q.1) [20 pts]**

$2^{20} = 1MB$

For an 80386 system working in real mode, the following address decoding circuit is given. (AEN is neglected).



- a) [15 pts] What range of addresses (in H) correspond to each output of the decoders?
- b) [5 pts] What is the total number of bytes in all ranges decoded by this circuit?

**Answer:**

$2^{13} = 8K = 1FFF$

[A]

a) 1<sup>st</sup> Decoder outputs:

	A <sub>19</sub>	A <sub>18</sub>	A <sub>17</sub>	A <sub>16</sub>	A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	.....	A <sub>0</sub>
For O <sub>0</sub> ≡	1	1	1	0	0	0	0	0	0000	0000 0000
	1	1	1	0	0	0	0	1	1111	1111 1111

≡ E0000-E1FFF = 8K

For O <sub>1</sub> ≡	1	1	1	0	0	0	1	0	0000	0000 0000
	1	1	1	0	0	0	1	1	1111	1111 1111

≡ E2000-E3FFF = 8K

2<sup>nd</sup> Decoder outputs:

	A <sub>19</sub>	A <sub>18</sub>	A <sub>17</sub>	A <sub>16</sub>	A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub>	A <sub>10</sub>	.....	A <sub>0</sub>
For O <sub>0</sub> ≡	1	1	1	0	0	0	1	0	0	0	0000	0000
	1	1	1	0	0	0	1	0	0	0	1111	1111

≡ E2000-E23FF = 1K

Similarly,

- For O<sub>1</sub> ≡ E2400-E27FF = 1K
- For O<sub>2</sub> ≡ E2800-E2BFF = 1K
- For O<sub>3</sub> ≡ E2C00-E2FFF = 1K
- For O<sub>4</sub> ≡ E3000-E33FF = 1K
- For O<sub>5</sub> ≡ E3400-E37FF = 1K
- For O<sub>6</sub> ≡ E3800-E3BFF = 1K
- For O<sub>7</sub> ≡ E3C00-E3FFF = 1K

$0100\ 0000\ 0000 = 2^{10} = 1024 = 1K$   
 (4 0 0 0)  
 - 0 0 1 H  
 3 + 5 = 1023


b) 8K + 8K = 16K [same answer for [B]]

[B]




a) 1<sup>st</sup> Decoder outputs: For O<sub>0</sub> ≡ 70000-71FFF = 8K For O<sub>1</sub> ≡ 72000-73FFF = 8K  
 2<sup>nd</sup> Decoder outputs: For O<sub>0</sub> ≡ 72000-723FF = 1K For O<sub>1</sub> ≡ 72400-727FF = 1K  
 For O<sub>2</sub> ≡ 72800-72BFF = 1K For O<sub>3</sub> ≡ 72C00-72FFF = 1K  
 For O<sub>4</sub> ≡ 73000-733FF = 1K For O<sub>5</sub> ≡ 73400-737FF = 1K  
 For O<sub>6</sub> ≡ 73800-73BFF = 1K For O<sub>7</sub> ≡ 73C00-73FFF = 1K

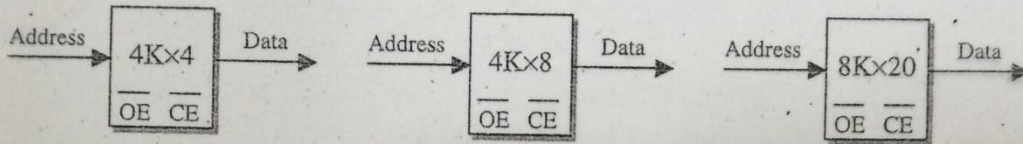**Q.3) [25pts]**

Using a **minimum** number of the PROM chips shown below, construct a  $8K \times 32$  bit PROM memory. (Show your design as block diagrams indicating the necessary connections of address, data and control signals).



**Answer:**

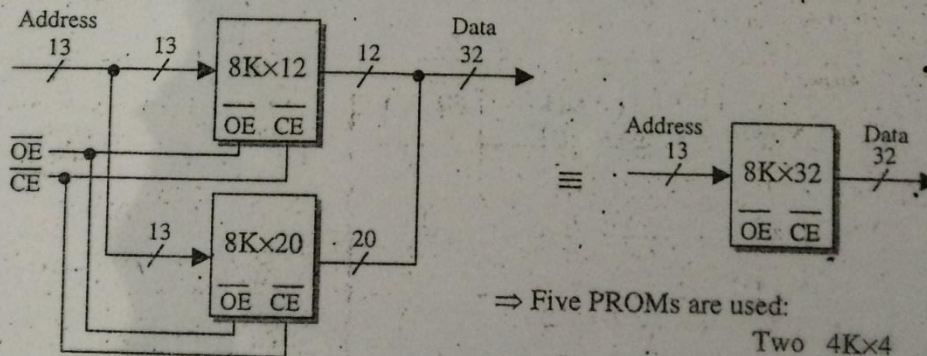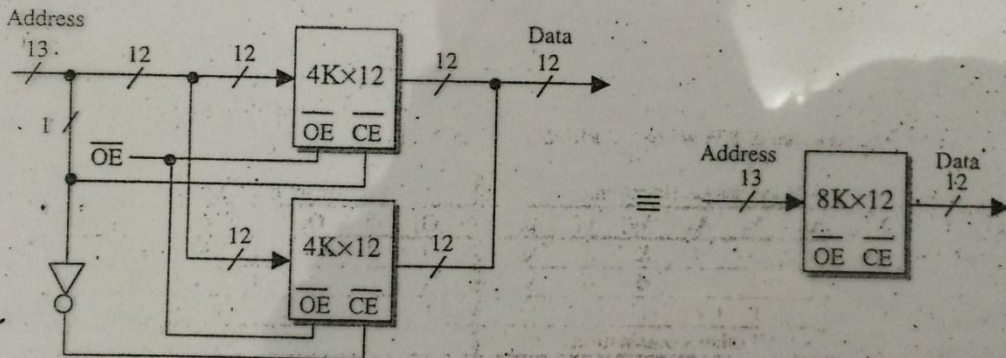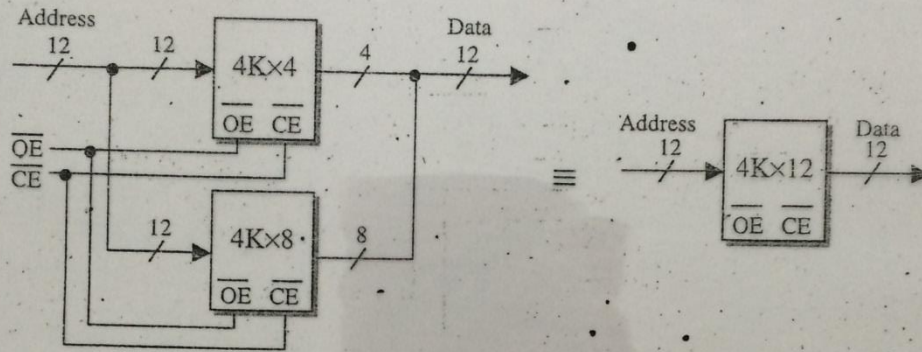

⇒ Five PROMs are used:

- Two  $4K \times 4$
- Two  $4K \times 8$
- One  $8K \times 20$




**Q3) [30 points]**

There is a need to add 56K byte of memory to an 80386 microprocessor based system (20-bit address bus and 8-bit data bus) in the address range A0000H-ADFFFH. The quantity of memory chips and the corresponding address ranges are as follows:

- 4 (8Kx8) RAM chips will be used to decode A0000H-A7FFFH
- 2 (4Kx8) RAM chips will be used to decode A8000H-A9FFFH
- 1 (16Kx8) RAM chip will be used to decode AA000H-ADFFFH

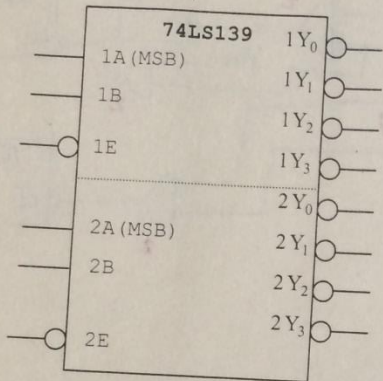
- a) (16p) Design an address decoding circuit using a 74LS139 decoder. Show all connections and signals in detail.
- b) (6) Determine the address range and its size in KB available in the memory map for any additional memory chip.



a)

$A_{19}$	$A_{18}$	$A_{17}$	$A_{16}$	$A_{15}$	$A_{14}$	$A_{13}$	$A_{12}$	$A_{11}$	$A_{10}$	...	$A_0$	
1	0	1	0	0	0	0	0	0	0	...	0	} A0000 - A1FFF
1	0	1	0	0	0	0	1	1	...	1		
1	0	1	0	0	0	1	0	0	...	0	} A2000 - A3FFF	
1	0	1	0	0	0	1	1	1	...	1		
1	0	1	0	0	1	0	0	0	...	0	} A4000 - A5FFF	
1	0	1	0	0	1	0	1	1	...	1		
1	0	1	0	0	1	1	0	0	...	0	} A6000 - A7FFF	
1	0	1	0	0	1	1	1	1	...	1		
1	0	1	0	1	0	0	0	0	...	0	} A8000 - A8FFF	
1	0	1	0	1	0	0	1	1	...	1		
1	0	1	0	1	0	0	1	0	...	0	} A9000 - A9FFF	
1	0	1	0	1	0	0	1	1	...	1		
1	0	1	0	1	0	1	0	0	...	0	} AA000 - ADFFF	
1	0	1	0	1	1	0	1	1	...	1		

## Address Decoder

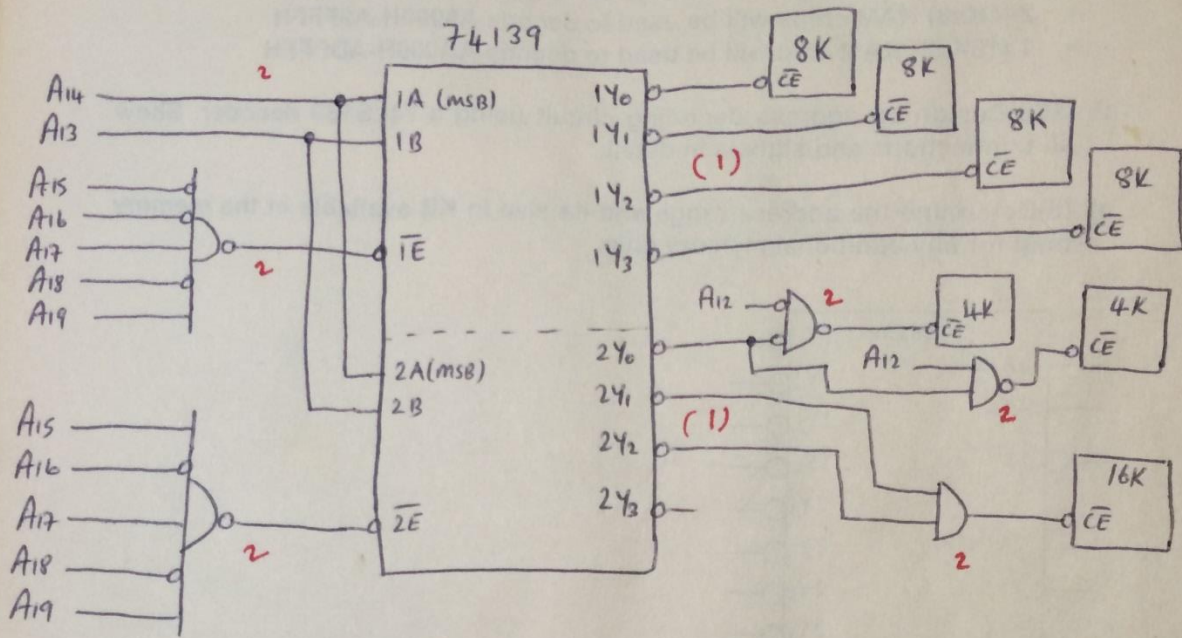

b) Available address ranges are

00000 - 9FFFF

AE000 - FFFFF

Total size of the available memory is 944KB.