



EASTERN MEDITERRANEAN UNIVERSITY

Faculty of Engineering
Department of Computer Engineering

CMPE 323: Microprocessors

Final Exam

Lecturer: Prof.Dr. Hasan Kömürcügil

Date: 27 / 01 / 2016
Time Allowed: 110 minutes

Name and Surname:..... **SOLUTION**


Student Number:.....

- There are 6 questions in this exam paper.
- Answer all questions.
- Write clearly and tidily.
- Correct answers without sufficient explanation might not get full points!
- Mobile phones must be switched off in the exam room.

Question	Points Gained
Q1 (24 points)	
Q2 (12 points)	
Q3 (20 points)	
Q4 (14 points)	
Q5 (14 points)	
Q6 (16 points)	
Total	

Q1) [24 points]

In the following system, the stepper motor is rotated clockwise (to the right) direction and "!" is displayed on the 7-segment if the switch (S_w) is closed. The motor rotates anti-clockwise (to the left) direction and "!" is displayed on the 7-segment if the switch is open. After each rotation, the switch position should be detected. Complete the following assembly program that fulfils this task.

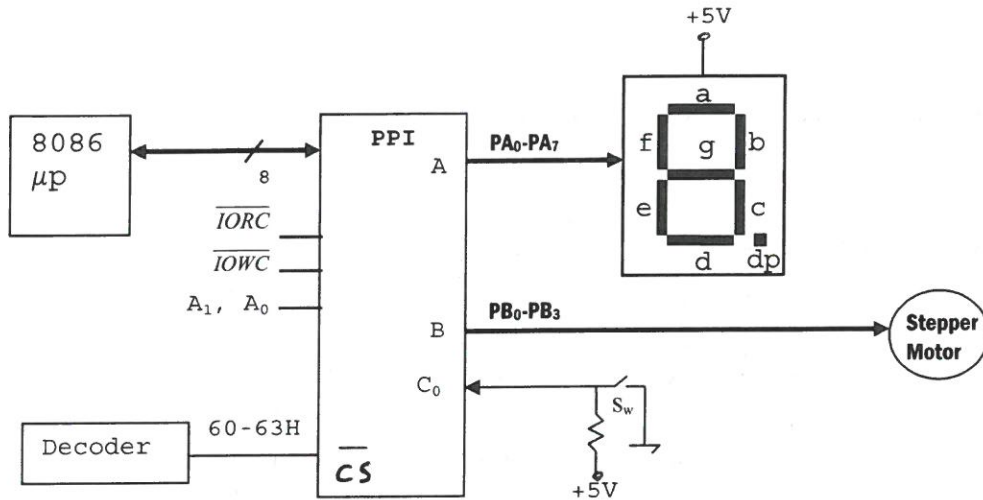

Note1: The command register format of the PPI is:

1 0 0 A Ch 0 B C1

1=Input
0=Output

Note 2: The 7-segmet display format is :

A7	A6	A5	A4	A3	A2	A1	A0
a	b	c	d	e	f	g	dp

```

Dosseg
.Model small
.Code
Switch:
    Mov al, 10000001B
    Out 63h, al
    Mov bl, 11001100B
    In al, 62h
    And al, 00000001B
    Shr al, 1
    Jnc Right
    Mov al, 11100011B
    Out 60h, al
    Rol bl, 1
    Mov al, bl
    Out 61h, al
    Call Delay
    Mov bl, al
    Jmp Switch
    
```


```

Right:
    Mov al, 01110011B
    Out 60h, al
    Ror bl, 1
    Mov al, bl
    Out 61h, al
    Call Delay
    Mov bl, al
    Jmp Switch

Delay:
    ..... 1µs
    ret
    
```

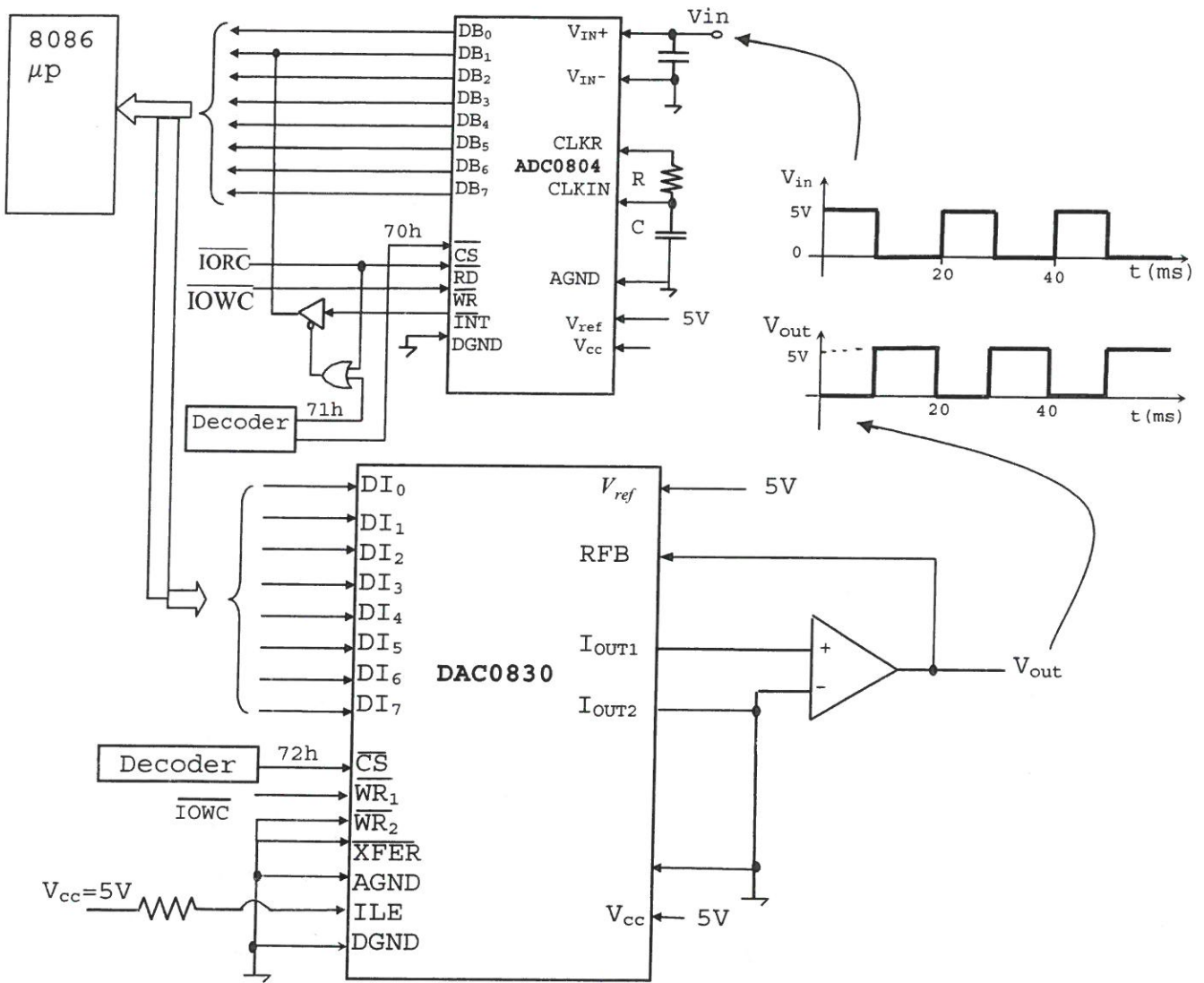Q2) [12 pts]

Consider the following system. The 8-bit ADC0804 converter takes samples from the square waveform (V_{in}) and converts each sample into its 8-bit binary equivalent. Each 8-bit binary data is then transferred to the microprocessor by the help of "in" instruction used in the assembly program. Thereafter, the 8-bit data is processed by the assembly program in the microprocessor so as to produce a square waveform (V_{out}) at the output of the DAC0830 converter as shown below. In both converters 5V corresponds to FFh. Complete the following assembly program that fulfils this task.



```

Start:
Notrdy:
    Dosseg
    .Model small
    .Code
    Out 70h, al
    In al, 71h
    Test al, 02h
    Jnz Notrdy
    In al, 70h
    Cmp al, 0FFh
    Je Reverse

Reverse:
    Mov al, 0FFh
    Out 72h, al
    Jmp Start
    Mov al, 0
    Out 72h, al
    Jmp Start
    
```

Q3) [20 points]


It is required to add 16KB of memory to an 80386 microprocessor based system which has 20-bit address and 8-bit data buses in the following address ranges:

- 2 (1Kx8) RAM chips to decode 00000h-007FFh
- 1 (2Kx8) RAM chip to decode 00800h-00FFFh
- 1 (4Kx8) RAM chip to decode 92000h-92FFFh
- 1 (8Kx8) RAM chip to decode 94000h-95FFFh

a) [7 points] Fill in the following table

A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	Range
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	00000
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	003FF
0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	00400
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	007FF
0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	00800
0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	00FFF
1	0	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	92000
1	0	0	1	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	92FFF
1	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	94000
1	0	0	1	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	95FFF

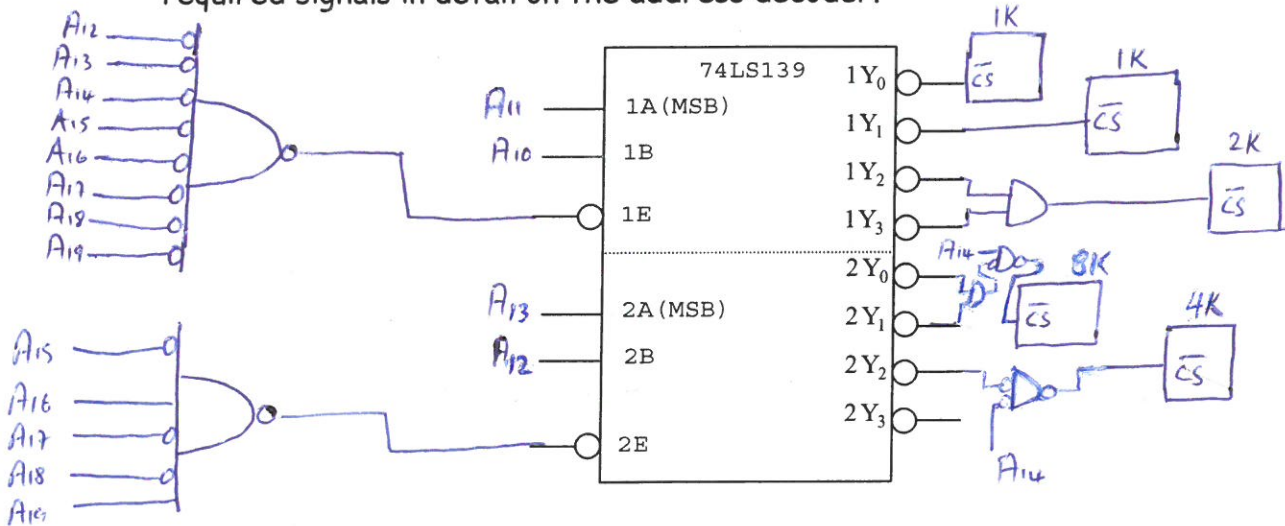b) [10 points] Using 74LS139 decoder shown below, design an address decoding circuit to decode the above address ranges. Show your connections and the required signals in detail on the address decoder.



c) [3 points] How much memory (both size and its range) is available in the memory map for an additional memory chip?


Available address ranges in the memory map.

01000 - 91FFF
 93000 - 93FFF
 96000 - FFFFF

$\Rightarrow 1024 - 16 = 1008 \text{ KB}$

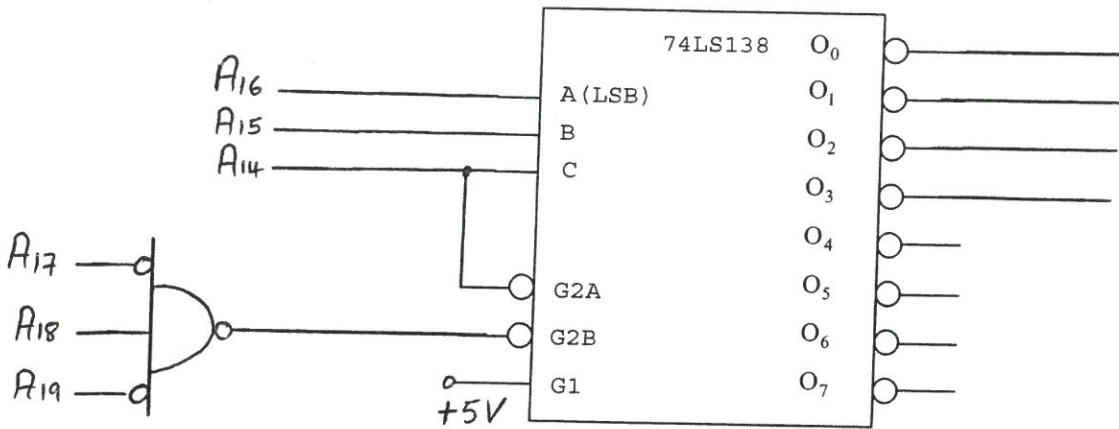Q4) [14 points]

Consider the following address decoding circuit.



- a) [12 points] Determine the address range (in Hexadecimal) and size (in KB) for the outputs O_0 , O_1 , O_2 and O_3 of the 74LS138 decoder.

A_{19}	A_{18}	A_{17}	A_{16}	A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	...	A_0	Range (in H)
0	1	0	0	0	0	0	0	0	0	...	0	$40000 - 43FFF \rightarrow O_0$ (16K)
0	1	0	0	0	0	1	1	1	1	...	1	
0	1	0	1	0	0	0	0	0	0	...	0	$50000 - 53FFF \rightarrow O_1$ (16K)
0	1	0	1	0	0	1	1	1	1	...	1	
0	1	0	0	1	0	0	0	0	0	...	0	$48000 - 4BFFF \rightarrow O_2$ (16K)
0	1	0	0	1	0	1	1	1	1	...	0	
0	1	0	1	1	0	0	0	0	0	...	0	$58000 - 5BFFF \rightarrow O_3$ (16K)
0	1	0	1	1	0	1	1	1	1	...	1	


- b) [2 points] What is the total size (capacity) of memory chip that can be connected to the other outputs of the decoder?

Since A_{14} is connected to $G2A$, then the decoder is never enabled when $A_{14} = 1$.


Therefore, the outputs $O_4, O_5, O_6,$ and O_7 cannot be connected to the memory chips. If they are connected to the memory chips, these chips will not be selected which results in 0KB.

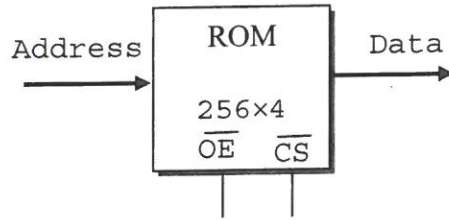Q5) [14 points]


Consider the following block diagram of a ROM chip.



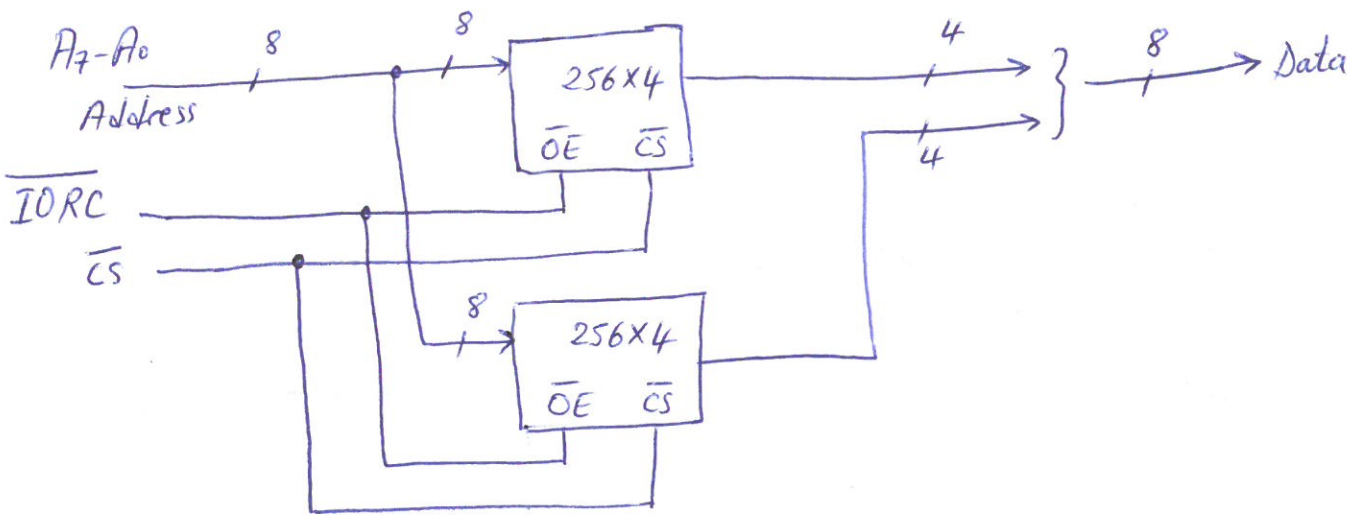a) [7 points] Using the ROM chip shown above, design a 256x8 ROM.




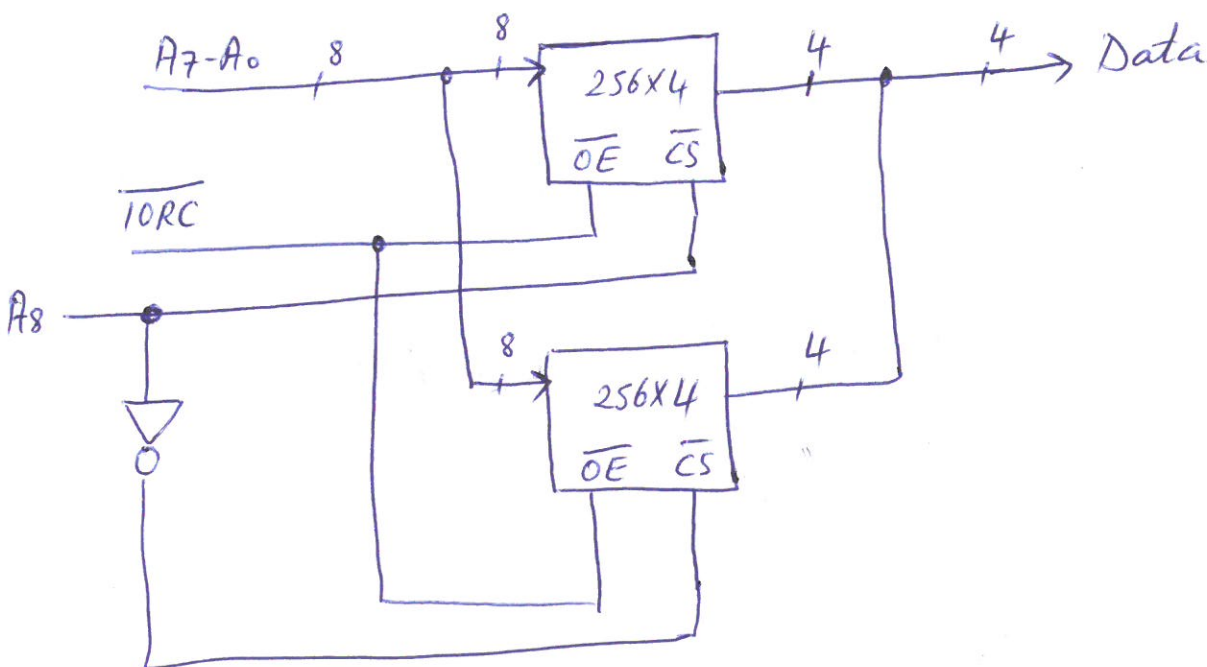b) [7 points] Using the ROM chip shown above, design a 512x4 ROM.



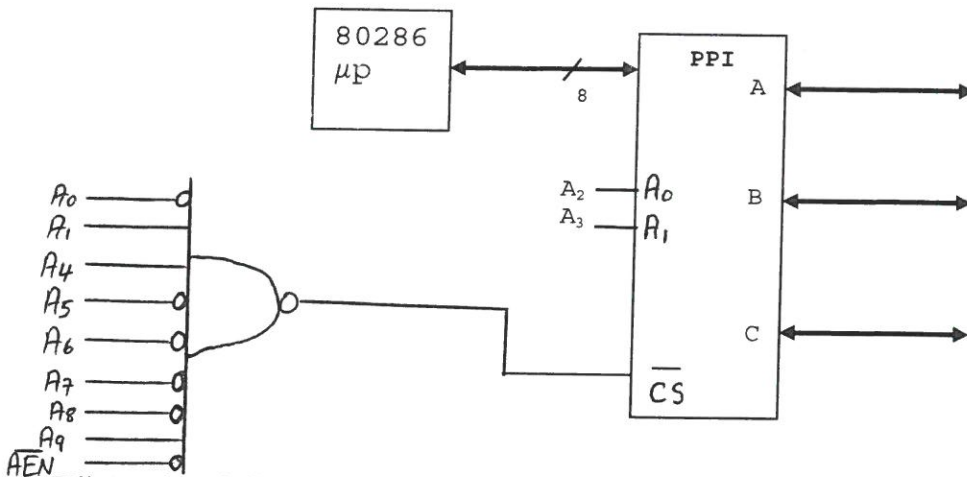Q6) [16 points]

Consider the following PPI register addressing circuit.



Fill in the following table and find the addresses of ports A, B, and C and the command register and record them into the table.

\overline{AEN}	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	Port Name or C. Register	Address (in Hex)
0	1	0	0	0	0	1	0	0	1	0	Port A	212
0	1	0	0	0	0	1	0	1	1	0	Port B	216
0	1	0	0	0	0	1	1	0	1	0	Port C	21A
0	1	0	0	0	0	1	1	1	1	0	Command Reg	21E

