



EASTERN MEDITERRANEAN UNIVERSITY

Faculty of Engineering
Department of Computer Engineering

CMPE 323: Microprocessors

Final Exam

Lecturer: Hasan K m rc gil

Date: 12 / 01 / 2018
Time Allowed: 120 minutes

Name and Surname: **SOLUTION**

Student Number:

- There are 5 questions in this exam paper.
- Answer all questions.
- Write clearly and tidily.
- Correct answers without sufficient explanation might not get full points!
- Mobile phones must be switched off in the exam room.

Question	Points Gained
Q1 (27 points)	
Q2 (20 points)	
Q3 (16 points)	
Q4 (23 points)	
Q5 (14 points)	
Total	

Q1) [27 points]


It is required to design the following microprocessor controlled greenhouse to provide the optimum conditions for growing plants. The system works as follows. The ADC gets data from the sensors (light, heat and humidity) through a multiplexer (MUX). The digital output of ADC is used to turn ON/OFF the grow light, heater and sprinkler and to CLOSE/OPEN the vent according to the following conditions.

- 1) (a) If there is enough light, the grow light is turned OFF ($A_0=0$)
 (b) If it is too dark, the grow light is turned ON ($A_0=1$)
- 2) (a) If it is too hot, the heater is turned OFF ($B_1=0$) and vent is OPENED ($B_0=1$)
 (b) If it is too cold, the heater is turned ON ($B_1=1$) and vent is CLOSED ($B_0=0$)
- 3) (a) If the soil is wet, the sprinkler is turned ON ($C_0=1$) $C_0=0$
 (b) If the soil is dry, the sprinkler is turned OFF ($C_0=0$) $C_0=1$

The digitized values of data received from the sensors are given in the following table.

Enough Light	Too Dark	Too Hot	Too Cold	Wet Soil	Dry Soil
10000000	00001000	01000000	00000100	00100000	00000010

Write down an assembly program to fulfil this task.

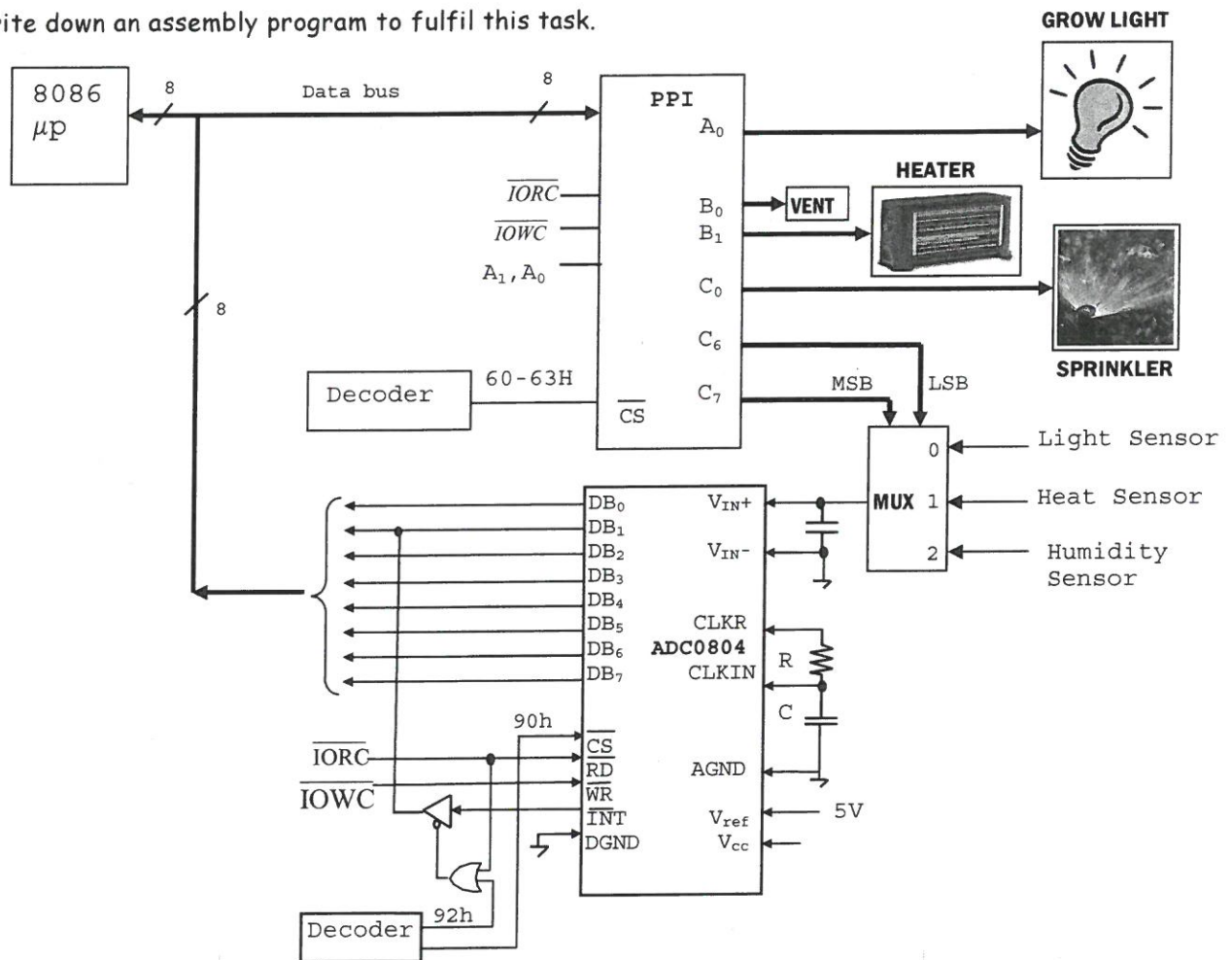

Note 1: The command register format of the PPI is:

1	0	0	A	C	h	0	B	C	l
---	---	---	---	---	---	---	---	---	---

1=Input
0=Output

Note 2: The 7-segmet display format is :

A7	A6	A5	A4	A3	A2	A1	A0
a	b	c	d	e	f	g	dp

• Code

```
mov al, 10000000b
out 63h, al
mov bl, 1
mov al, 0 ; select Light Sensor
out 62h, al
```

Start:
Notrdy:

```
out 90h, al
in al, 92h
test al, 02h
jnz Notrdy
in al, 90h
cmp bl, 1
je GrowL
cmp bl, 2
je Heater
cmp bl, 3
je Sprinkler
```

GrowL:

```
cmp al, 80h
Jb Dark
```

EnoughL:

```
mov al, 0 ; A0=0
out 60h, al
```

Dark:

```
jmp cont1
mov al, 1 ; A0=1
out 60h, al
```

cont1:

```
mov bl, 2
mov al, 40h ; Select Heat Sensor
out 62h, al
jmp start
```

Heater:

```
cmp al, 40h
Jb Cold
```

Hot:

```
mov al, 1 ; B1=0 & B0=1
out 61h, al
jmp cont2
```

Cold:

```
mov al, 2 ; B1=1 & B0=0
out 61h, al
```

cont2:

```
mov bl, 3
mov al, 80h ; Select H. Sensor
out 62h, al
jmp start
```

→ Sprinkler:

```
cmp al, 20h
jb DryS
```

Wets:

```
mov al, 0 ; C0=0
out 62h, al
```

DryS:


```
jmp cont3
mov al, 1 ; C0=1
out 62h, al
```

Cont3:

```
mov bl, 1
mov al, 0
out 62h, al
jmp start
```

Q2) [20 points]

In the following system, the stepper motor is rotated 5 turns in the clockwise direction (to the right) and "5" is displayed on the 7-segment display unit when the switch (S_w) is open. The motor rotates 8 rotations in the anti-clockwise direction (to the left) and "8" is displayed on the 7-segment display unit when the switch is closed. Once the stepper motor direction is determined, it is assumed that the position of switch is not changed until the motor completes its desired rotations. When the motor completes its rotation, the program should check the switch position to determine the new direction of rotation. Complete the following assembly program that fulfils this task.

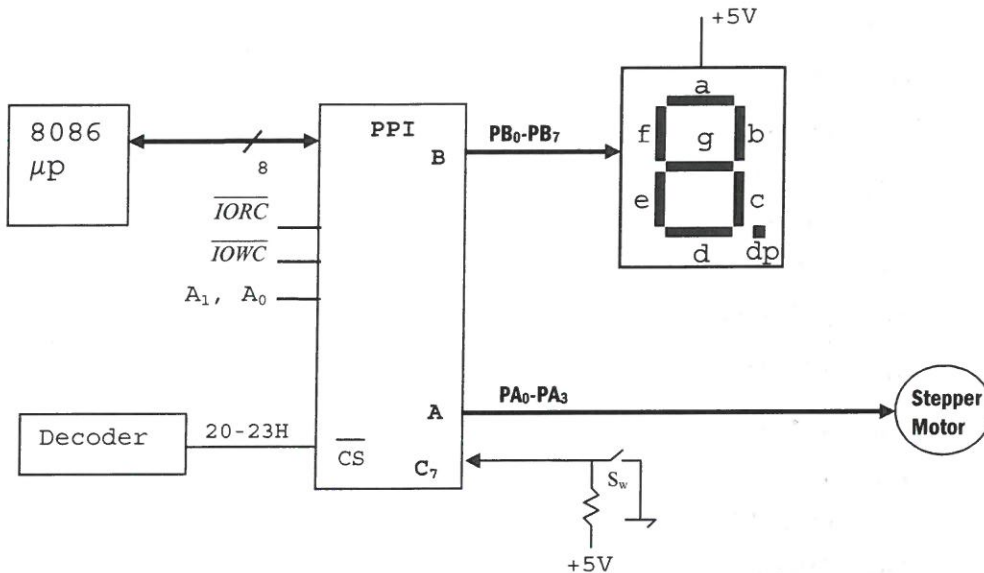

Note1: The command register format of the PPI is:

1	0	0	A	Ch	0	B	C1
---	---	---	---	----	---	---	----

1=Input
0=Output

Note 2: The 7-segmet display format is :

A7	A6	A5	A4	A3	A2	A1	A0
a	b	c	d	e	f	g	dp

```

Dosseg
.Model small
.Code
Mov al, 10001000B
Out 23h, al
Mov bl, 11001100B
Start: In al, 22h
And al, 10000000B
Shl al, 1
Jnc Left
Right: Mov al, 49h
Out 21h, al
Mov cx, 5
RotR: Ror bl, 1
Mov al, bl
Out 20h, al
Call Delay
Loop RotR
Mov bl, al
Jump Start
    
```

```


Left: Mov al, 01h
Out 21h, al
Mov cx, 8
RotL: Rot bl, 1
Mov al, bl
Out 20h, al
Call Delay
Loop RotL
Mov bl, al
Jump Start

Delay: ..... 1µs
ret
    
```


Q3) [16 points]

Consider the following DAC0830 interfaced to an 8086 microprocessor. An assembly program which is written to produce an analog waveform via DAC at V_{out} is provided below.

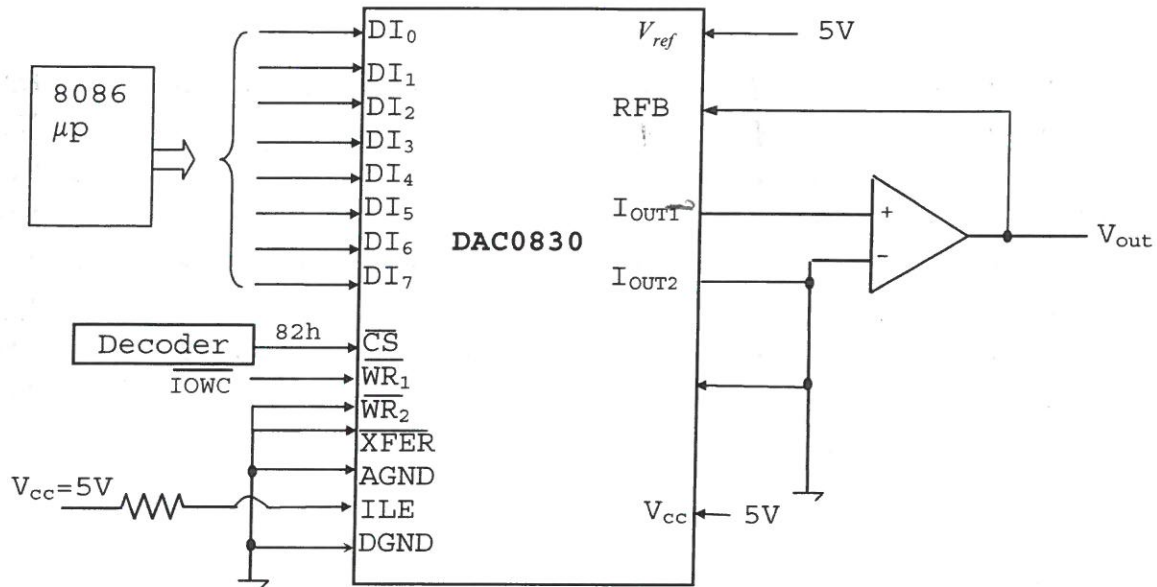
(a) [12 points] Assuming that the hexadecimal numbers 00h and FFh correspond to 0V and 5V, respectively, trace the assembly program and draw V_{out} for two periods. Show voltage levels and time on the waveform in detail.



```

Dosseg
.Model small
.Code
Start:  Mov al,127
Again:  Out 82h,al
        Call delay
Next:   Loop Again
        Inc al
        Out 82h,al
        Call delay
        Cmp al,255
        jb Next
Continue: Dec al
          Out 82h,al
          Call Delay
          Cmp al,0
          Ja Continue
Repeat:  Inc al
          Out 82h, al
          Call Delay
          Cmp al,127
          Jb Repeat
          Jmp Start

Delay:  ..... 2μs
        ret
    
```

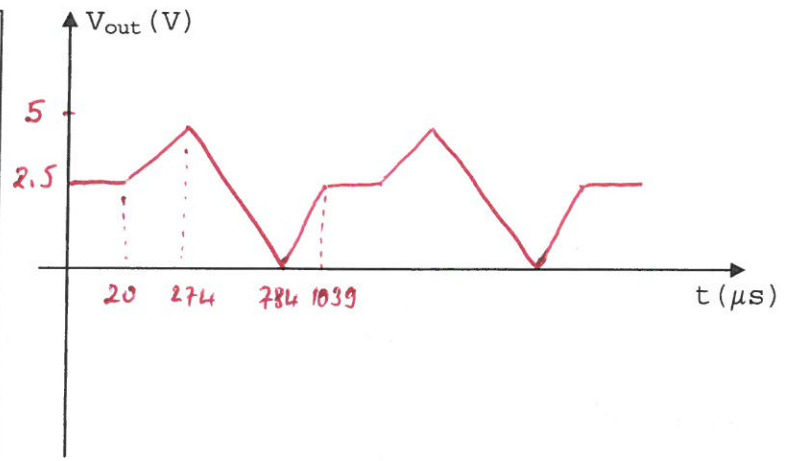

(b) [4 points] Find the approximate period and frequency of V_{out} .

$T = 1039 \mu s$

$f = \frac{1}{T} = \frac{1}{1039} \times 10^6 \text{ Hz}$

Q4) [23 pts]


It is required to interface the following memory chips to an 80386 microprocessor based system which has 20-bit address and 8-bit data buses in the following address ranges:

- 1 (2Kx8) ROM chip to decode 83000h-837FFh
- 2 (8Kx8) ROM chips to decode 84000h-87FFFh
- 1 (32Kx8) RAM chip to decode 88000h-8FFFFh

a) [4 points] Fill in the following table

A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	Range
φ	0	0	0	0	0	1	φ	0	0	0	0	0	0	0	0	0	0	0	0	83000
φ	0	0	0	0	0	1	φ	0	φ	1	1	1	1	1	1	1	1	1	1	837FF
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	84000
1	0	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	85FFF
1	0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	86000
1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	87FFF
1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	88000
1	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	8FFFF

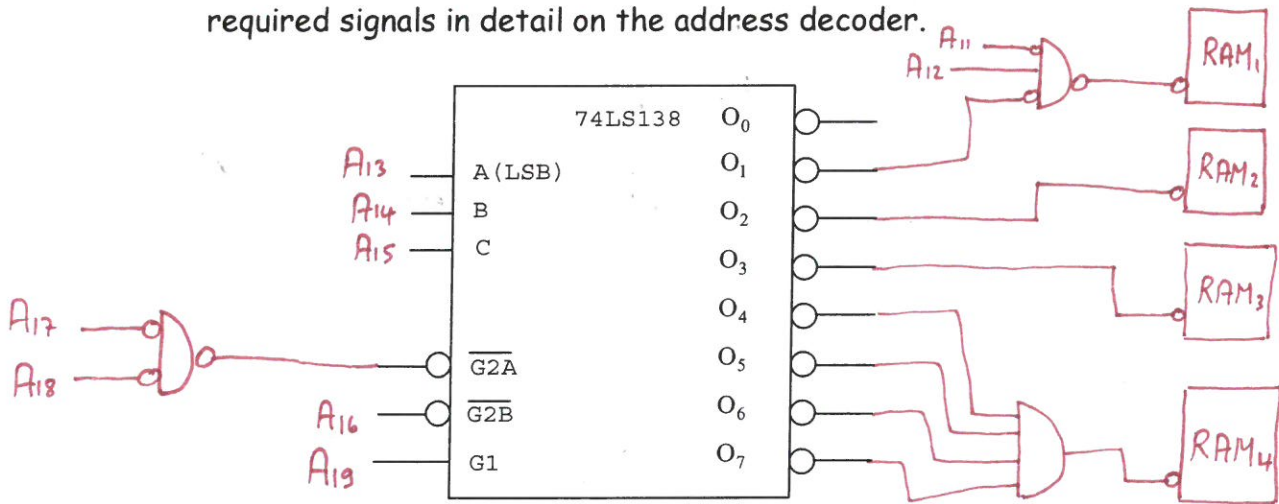b) [16 points] Using 74LS138 decoder shown below, design an address decoding circuit to decode the above address ranges. Show your connections and the required signals in detail on the address decoder.




c) [3 points] How much memory (both size and its range) is available in the memory map for an additional memory chip?

Available ranges: 00000 - 82FFF
 83800 - 83FFF
 90000 - FFFFF

Available size: 1024KB - (2+8+8+32) = 974KB

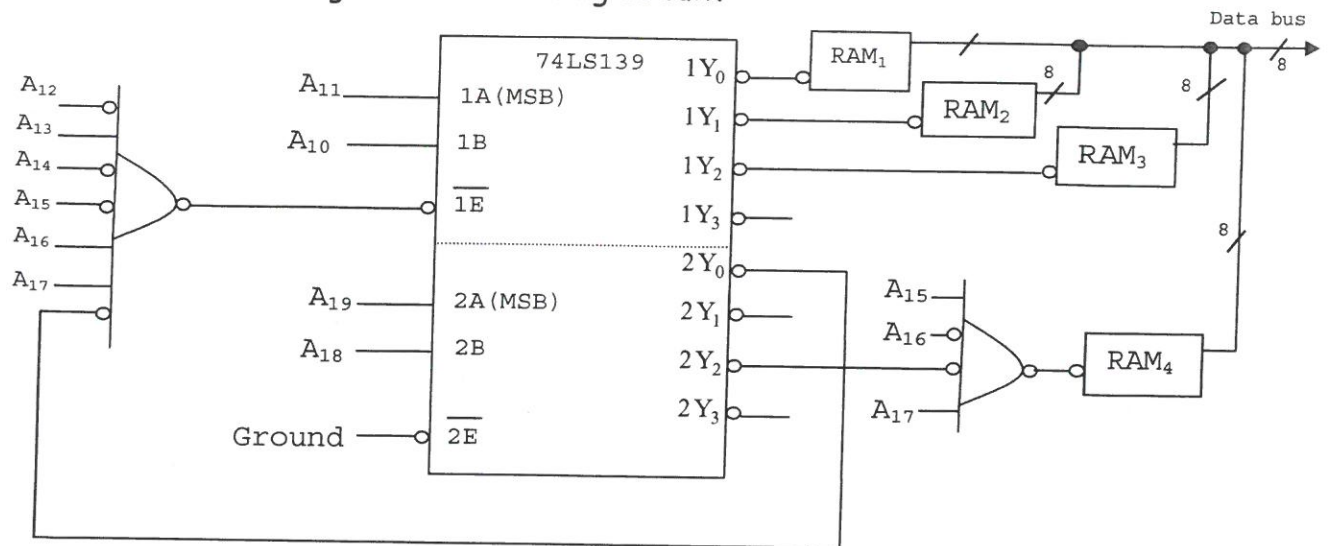Q5) [14 points]

Consider the following address decoding circuit.



- a) [8 points] Determine the decoded address range (in Hexadecimal) and size (in KB) for the RAM chips and record them into the following table.

	Decoded address range (in hex)	Decoded size (in KB)
RAM ₁	32000 - 323FF	1
RAM ₂	32400 - 327FF	1
RAM ₃	32800 - 32BFF	1
RAM ₄	A8000 - AFFFF	32

- b) [6 points] It is required to interface 3 additional RAM chips to the existing outputs (1Y₃, 2Y₁ and 2Y₃) of the address decoding circuit shown above. Find the possible address range and size of each RAM chip and record them into the following table.

	Decoded address range (in hex)	Decoded size (in MB)
1Y ₃ (RAM ₅)	32C000 - 32FFF	0.016
2Y ₁ (RAM ₆)	40000 - 7FFFF	0.256
2Y ₃ (RAM ₇)	C0000 - FFFFF	0.256

