



EASTERN MEDITERRANEAN UNIVERSITY

Faculty of Engineering
Department of Computer Engineering

CMPE 323: Microprocessors

Final Exam

Lecturer: Hasan Kömürçügil

Date: 30 / 05 / 2017

Time Allowed: 110 minutes

Name and Surname: SOLUTION

Student Number:

- There are 5 questions in this exam paper.
- Answer all questions.
- Write clearly and tidily.
- Correct answers without sufficient explanation might not get full points!
- Mobile phones must be switched off in the exam room.

Question	Points Gained
Q1 (24 points)	
Q2 (24 points)	
Q3 (16 points)	
Q4 (20 points)	
Q5 (16 points)	
Total	

Q1) [24 points]


Consider the following system. It is required to display "ON" or "OF" on the common anode 7-segment display units based on the actual temperature (temp) value which is sensed by the temperature sensor and digitized by the ADC as shown below.

When the $temp > 22^{\circ}C \rightarrow$ display "On" and send a signal ($C_7=1$) to A/C.

When the $temp < 22^{\circ}C \rightarrow$ display "OF" and send a signal ($C_7=0$) to A/C.

When the $temp = 22^{\circ}C \rightarrow$ display nothing and send a signal ($C_7=0$) to A/C.

Note that 8-bit binary representation of $22^{\circ}C$ in the ADC is 1000001. Write down an assembly program to fulfil this task.

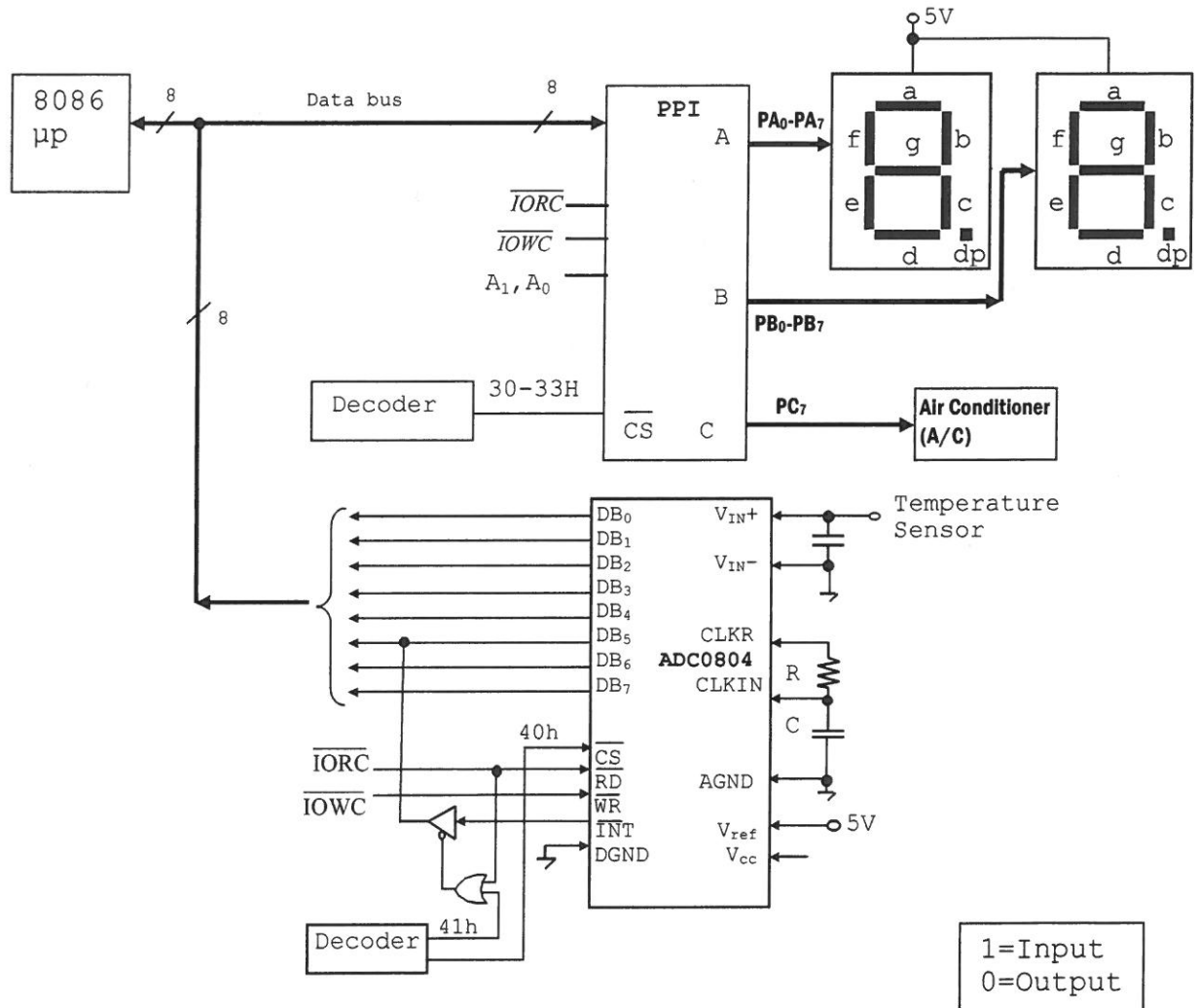

Note1: The command register format of the PPI is:

1	0	0	A	C	h	0	B	C	1
---	---	---	---	---	---	---	---	---	---

Note 2: The 7-segmet display format for A and B is :

A7	A6	A5	A4	A3	A2	A1	A0
dp	g	f	e	d	c	b	a

Dosseg

- Model small
- Code

Start: Mov al, 80h
Out 33h, al
Out 40h, al

Notrdy: In al, 41h
Test al, 20h
Jnz Notrdy
In al, 40h
Cmp al, 81h
Je Dark
Ja On

Off: Mov al, 11000000b ; display 0
Out 30h, al
Mov al, 10001110b ; display F
Out 31h, al
Mov al, 0
Out 32h, al
Jmp start

On: mov al, 11000000b ; display 0
Out 30h, al
mov al, 11001000b ; display 1
Out 31h, al
mov al, 80h
Out 32h, al
Jmp start


Dark: Mov al, 0FFh ; dark display
Out 30h, al
Out 31h, al
Mov al, 0
Out 32h, al
Jmp start

Q2) [24 pts]

Consider the following system. It is required to control the stepper motors as follows:

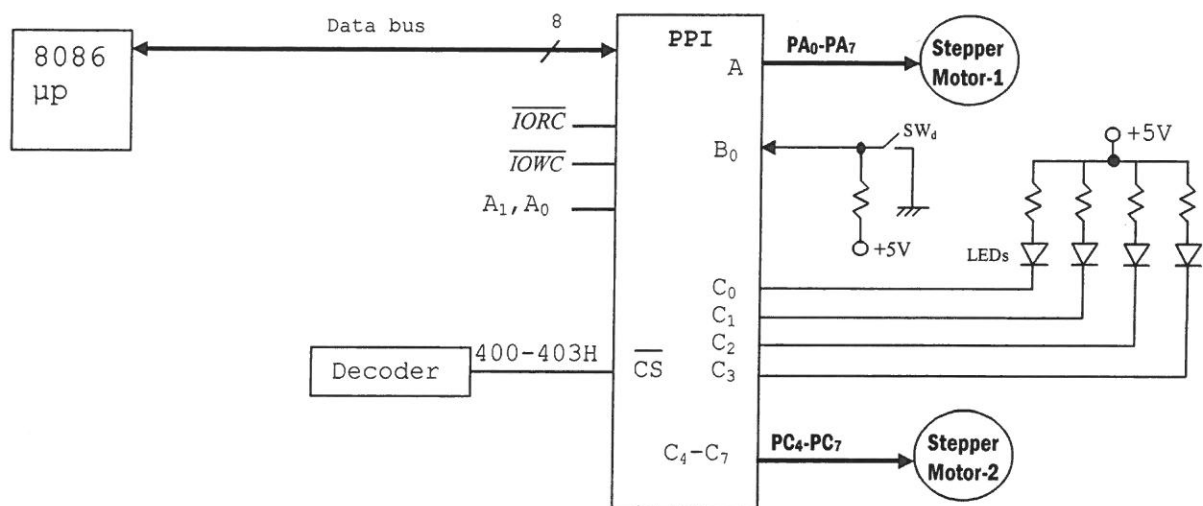- i) The direction of rotation is determined by the position of SW_d (**Closed**:clockwise, **Open**:anti-clockwise).
- ii) Each motor is supposed to make 20 rotations. The time between each rotation for stepper motor-1 and stepper motor-2 are 2μs and 4μs, respectively. This means that the stepper motor-1 is twice faster than the stepper motor-2.
- iii) The LEDs are turned ON or OFF with the same 4-bit data used to rotate the motors.

Complete the following an assembly program to accomplish the above task.



```

Dosseg
.Model small
.Code
Mov al, 82h
Mov dx, 403h
Out dx, al
Mov cx, 20
Mov bl, 11001100b
Start:
Mov dx, 401h
In al, dx
And al, 00000001b
Cmp al, 01h
Je Ccw
Cw:
Mov al, bl
Mov dx, 400h
Ror al, 1
Out dx, al
Call delay
Mov dx, 402h
Out dx, al
Call delay
Call delay
Loop Ccw
Mov bl, al
Jmp Start

Loop Cw
Mov bl, al
Jmp Start


Ccw:
Mov al, bl
Mov dx, 400h
Ror al, 1
Out dx, al
Call delay
Mov dx, 402h
Out dx, al
Call delay
Call delay
Loop Ccw
Mov bl, al
Jmp Start

Delay:
..... 2μs
.....
.....
ret
    
```

Q3) [16 points]

Consider the following DAC0830 interfaced to an 8086 microprocessor. It is required to produce an analog waveform (V_{out}) at the output of DAC.

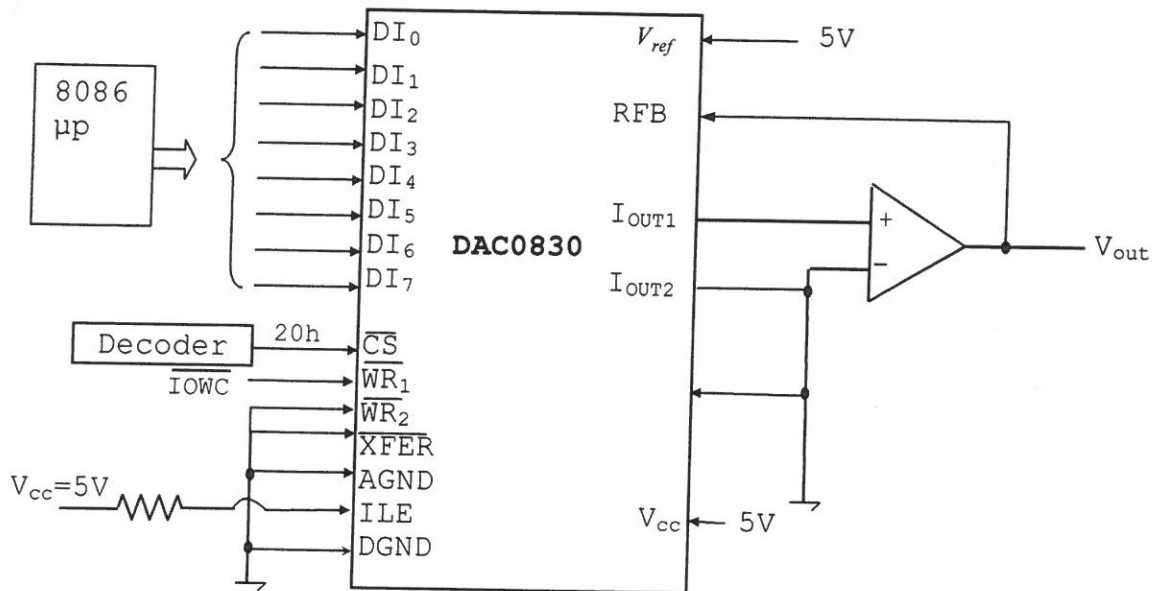
(a) [12 points] Assuming that the hexadecimal numbers 00h and FFh correspond to 0V and 5V, respectively, write an assembly program to produce V_{out} .



```

    .code
Start: mov cx, 25
      mov al, 127
T1:   out 20h, al
      call delay
      loop T1
      mov cx, 25
      mov al, 255
T2:   out 20h, al
      call delay
      loop T2
      mov cx, 25
      mov al, 127
T3:   out 20h, al
      call delay
      loop T3
      mov cx, 25
      mov al, 0
      out 20h, al
      call delay
      jmp start

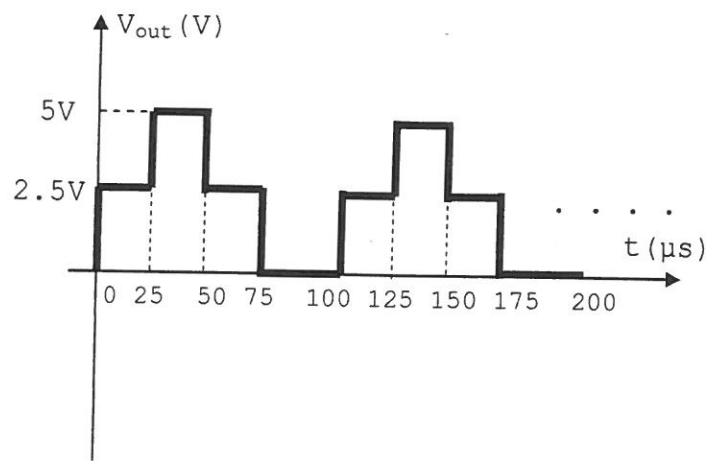Delay: .....1μs
      ....
      ret
    
```



(b) [4 points] Find the approximate period and frequency of V_{out} .

Period, $T = 100\mu s$

Frequency, $f = \frac{1}{T} = \frac{1}{100 \times 10^{-6}} = 10\text{kHz}$

Q4) [20 pts]


It is required to interface the following memory chips to an 80386 microprocessor based system which has 20-bit address and 8-bit data buses in the following address ranges:

- 2 (16Kx8) RAM chips to decode 80000h-87FFFh
- 2 (8Kx8) RAM chip to decode 88000h-8BFFFh
- 2 (4Kx8) RAM chip to decode 8C000h-8DFFFh

a) [3 points] Fill in the following table

A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	Range
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	80000
1	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	83FFF
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	84000-
1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	87FFF
1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	88000-
1	0	0	0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	89FFF
1	0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	8A000-
1	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	8BFFF
1	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	8C000-
1	0	0	0	1	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	8CFFF
1	0	0	0	1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	8D000-
1	0	0	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	8DFFF

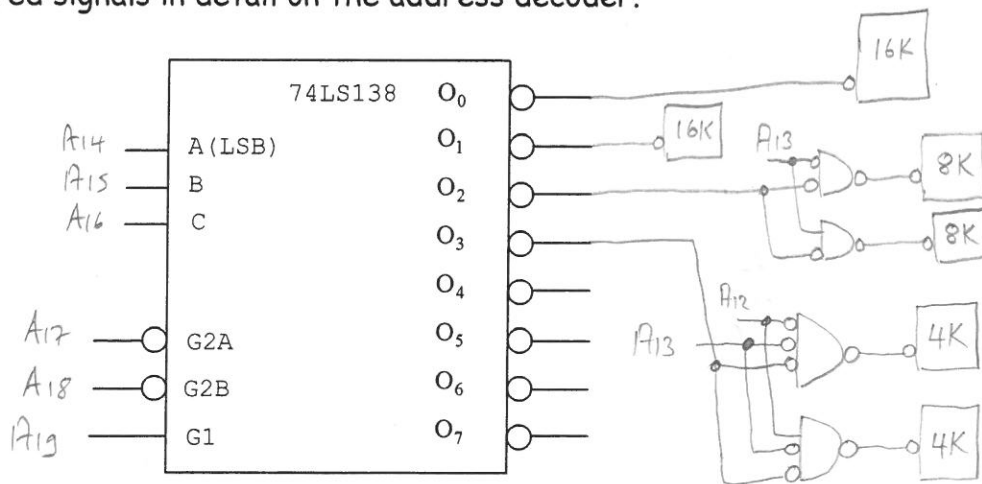b) [14 points] Using 74LS138 decoder shown below, design an address decoding circuit to decode the above address ranges. Show your connections and the required signals in detail on the address decoder.




c) [3 points] How much memory is available in the memory map for an additional memory chip? Give size and range.

Available Ranges: 00000 - 7FFFFF
8E000 - FFFFFF

Available Size = 1024 - (32 + 16 + 8) = 968 KB

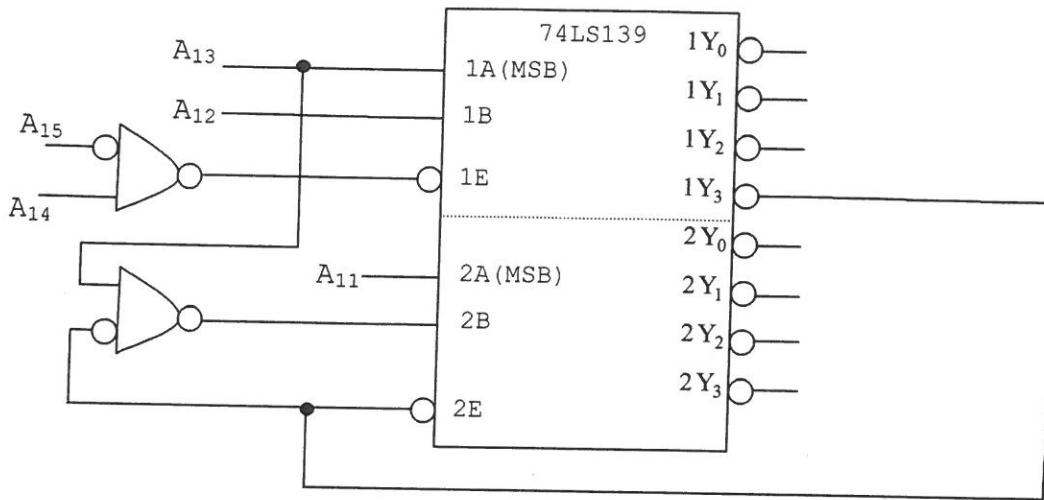Q5) [16 points]

Consider the following address decoding circuit.



Determine the address range (in Hexadecimal) and size (in KB) for the RAM chips and record them into the following table.

	Decoded address range (in hex)	Decoded size (in KB)
1Y ₀	4000-4FFF	4K
1Y ₁	5000-5FFF	4K
1Y ₂	6000-6FFF	4K
1Y ₃	7000-7FFF	4K
2Y ₀	7000-77FF	2K
2Y ₁	Does not exist	—
2Y ₂	7800-7FFF	2K
2Y ₃	Does not exist	—

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	-	-	-	-	-	-	A ₀	
0	1	0	0	0	0	-	-	-	-	-	-	0) 1Y ₀ : 4000-4FFF (4K)
0	1	0	0	1	1	-	-	-	-	-	1		
0	1	0	1	0	0	-	-	-	-	-	-	0) 1Y ₁ : 5000-5FFF (4K)
0	1	0	1	1	1	-	-	-	-	-	1		
0	1	1	0	0	0	-	-	-	-	-	-	0) 1Y ₂ : 6000-6FFF (4K)
0	1	1	0	1	1	-	-	-	-	-	1		
0	1	1	1	0	0	-	-	-	-	-	-	0) 1Y ₃ : 7000-7FFF (4K)
0	1	1	1	1	1	-	-	-	-	-	1		
0	1	1	1	0	0	-	-	-	-	-	-	0) 2Y ₀ : 7000-77FF (2K)
0	1	1	1	0	1	-	-	-	-	-	1		
0	1	1	1	1	0	-	-	-	-	-	-	0) 2Y ₂ : 7800-7FFF (2K)
0	1	1	1	1	1	-	-	-	-	-	1		

