

2. X OTHER LOGIC GATES

22'

There are 2^{2^n} different combinations ^(Functions) for n binary variables.

For $n=2$;

X Y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0 0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0 1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1 0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1 1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

1) Two functions that produce a constant 0 or 1

$F_0 = 0$ (Null)

$F_{15} = 1$ (Identity)

2) Four functions with unary operations: Complement and Transfer

$F_3 = x$ Transfer (x)

$F_5 = y$ Transfer (y)

$F_{10} = y'$ Complement (Not y)

$F_{12} = x'$ Complement (Not x)

3) Ten functions with binary operators:

Function	Another notation	Name	Comments
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x / y	Inhibition	x but not y
$F_4 = x'y$	y / x	Inhibition	y but not x
$F_6 = x'y + xy'$	$x \oplus y$	Exclusive-OR (XOR)	x or y but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$x \odot y$	Exclusive-NOR Equivalence (X-NOR)	x equals y
$F_{11} = x + y'$	$x \subset y$	Implication	If y then x
$F_{13} = x' + y$	$x \supset y$	Implication	If x then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND

Out of the above 16 functions, only the complement, transfer AND, OR, NAND, NOR, XOR, and Exclusive-NOR are used.

Name Graphic Symbol Function Truth table

AND



$F = xy$

xy	F
00	0
01	0
10	0
11	1

OR



$F = x+y$

xy	F
00	0
01	1
10	1
11	1


Inverter



$F = x'$

x	F
0	1
1	0


Buffer

 

$F = x$

x	F
0	0
1	1

NAND

 

$F = (xy)'$

xy	F
00	1
01	0
10	0
11	0


NOR



$F = (x+y)'$

xy	F
00	1
01	0
10	0
11	0


Exclusive-OR
XOR

 

$F = x \oplus y$
 $= xy' + x'y$

xy	F
00	0
01	1
10	1
11	0


Exclusive-NOR
XNOR
Equivalence

 

$F = x \odot y$
 $= xy + x'y'$



xy	F
00	1
01	0
10	0
11	1

Note that;

 

$(xy)'$ = $x' + y'$ is DeMorgan

$(x+y)'$ = $x' \cdot y'$

  

2.4 Boolean Functions:

A Boolean function F , is an expression formed with binary variables, the binary operators OR and AND, unary operator NOT, parentheses, and an equal sign. For a given values of the variables, the function can be either 0 or 1.

Example:

$F_1 = xyz'$, $\Rightarrow F_1 = 1$ if $x=1, y=1$, and $z'=1$ ($z=0$); otherwise $F_1 = 0$

Consider the functions:

$$F_2 = x + y'z$$

$$F_3 = x'y'z + x'yz + xy'$$

$$F_4 = xy' + x'z$$

x	y	z	F_1	F_2	F_3	F_4
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0





Is it possible to find two algebraic expressions to specify the same function? YES

$$F_3 \equiv F_4$$

$$F_3 = x'y'z + x'yz + xy'$$

$$= x'z(y' + y) + xy' = x'z + xy'$$

    A Boolean function may be transformed from an algebraic expression into a logic diagram.



Since $F_3 \equiv F_4$; it is more economical to implement F_4 because it has fewer gates \Rightarrow we should simplify the function as much as possible.

Algebraic Manipulation:

Defn: A literal is a single variable within a term which may or may not be complemented. for example, x, y, x', y'

The number of literals in a Boolean function can be minimized by algebraic manipulations. ~~using some~~ Unfortunately, there are no specific rules to follow that will guarantee the final answer.

Examples:

1) $x + x'y = (x + x') \cdot (x + y) = 1 \cdot (x + y) = x + y$ Axioms: 4(b), 5(a), 2(b)

2) $x(x' + y) = xx' + xy = 0 + xy = xy$ Axioms: 4(a), 5(b), 2(a)

3) $x'y'z + x'yz + xy' = x'z(y' + y) + xy' = x'z \cdot 1 + xy' = x'z + xy'$ Axioms: 4(a), 5(a), 2(b)

4) $xy + x'z + yz = xy + x'z + yz(x + x') = xy + x'z + yzx + yzx' = xy(1 + z) + x'z(1 + y) = xy + x'z$ Axioms: 5(a), 2(b), 4(a), 4(a), Theorem 2(a)

5) $(x + y)(x' + z)(y + z) = (x + y)(x' + z)(y + z + xx') = (x + y)(x' + z)(x + y + z)(x' + y + z) = (x + y)(x + y + z)(x' + z)(x' + y + z) = (x + y)(x' + z)$ 5(b), 2(a), 4(b), 3(b), Theorem 6(b)

6) $x'y'z' + x'y'z + xy'z' + xy'z + xyz' = x'y'(z' + z) + xy'(z' + z) + xyz' = x'y' + xy' + xyz' = (x' + x)y' + xyz' = y' + xyz' = y' + y \cdot (xz') = (y' + y) \cdot (y' + xz') = y' + xz'$

Complement of a function:

The complement of a function F is F' and is obtained from an interchange of 0's and 1's in the value of F and by applying the generalized DeMorgan's theorem.

$(A + B + C + D + \dots + G)' = A' \cdot B' \cdot C' \cdot D' \cdot \dots \cdot G'$

$(ABC \dots G)' = A' + B' + \dots + G'$

Examples:

1) Find the complement of $F_1 = x'y'z' + x'y'z$ by using DeMorgan's Theorem

$$F_1' = (x'y'z' + x'y'z)' = (x'y'z')' \cdot (x'y'z)'$$

$$= (x + y' + z) \cdot (x + y + z')$$

2) Find the complement of F_1 using the dual method {take the dual then, take complement of each part}

$$F_1 = (x'y'z') + (x'y'z)$$

$$\Rightarrow \text{dual of } F_1 = (x'y'z') \cdot (x'y'z)$$

$$\Rightarrow F_1' = (x'y'z')' \cdot (x'y'z)'' = (x + y' + z) \cdot (x + y + z')$$

Find the complement of $F_2 = (A'+B) + CD$

$$F_2' = ((A'+B) + CD)' = (A'+B)' \cdot (CD)' = (AB') \cdot (C'+D')$$

4) Repeat 3 with dual method

$$F_2 = (A'+B) + (CD)$$

$$\Rightarrow \text{dual of } F_2 = (A'+B) \cdot (CD)$$

$$\Rightarrow F_2' = (A'+B)' \cdot (CD)' = (AB') \cdot (C'+D')$$

5) Find the complement of $F_3 = X(y'z' + yz)$

$$F_3' = [X(y'z' + yz)]' = X' + (y'z' + yz)'$$

$$= X' + [(y'z')' \cdot (yz)']$$

$$= X' + (y + z) \cdot (y' + z')$$

6) Repeat 5 by the dual method.

$$F_3 = X \cdot (y'z' + yz)$$

$$\Rightarrow \text{dual of } F_3 = X + (y'z' + yz)$$

$$\Rightarrow F_3' = X' + (y'z' + yz)'$$

$$= X' + (y'z')' \cdot (yz)'' = X' + (y + z) \cdot (y' + z')$$

7) Find the complement of $F_4 = (A+B) \cdot C'D' + E + F'$

$$F_4' = ((A+B) \cdot C'D' + E + F)'' = ((A+B)C'D')' \cdot (E)'' \cdot (F)''$$

$$= ((A+B)' + C + D) \cdot E \cdot F = (A'B' + C + D)EF$$

8) Repeat 7 using Dual method. ^{or}

$$F_4 = ((A+B)\bar{C}\bar{D}) + E + \bar{F} \Rightarrow \text{dual} = (A \cdot B + \bar{C} + \bar{D}) \cdot E \cdot F'$$

$$\Rightarrow \text{dual of } F_4 = ((A+B)C'D') \cdot E \cdot F'$$

$$\Rightarrow F_4' = ((A+B)C'D')' \cdot E' \cdot F$$

$$= ((A+B)' + C + D) E' F$$

$$= (A'B' + C + D) E' F$$

Minterms and Maxterms:

(26)

- Any boolean expression may be expressed in terms of either minterms or maxterms.
 - A minterm is the Product of N distinct literals where each literal occurs exactly once. Each minterm is obtained from an AND term of the variables, with each variable being primed if the corresponding bit is a "0" and unprimed if "1".
 - A maxterm is the sum of N distinct literals where each literal occurs exactly once. Each maxterm is obtained from an OR term of the variables, with each variable being unprimed if the corresponding bit is a "0" and primed if a "1".
- ⇒ a maxterm is the complement of its corresponding minterm, and vice versa.

Example: with 3-variables

x y z	Minterms		Maxterms	
	Term	Symbol	Term	Symbol
0 0 0	$x'y'z'$	m_0	$x+y+z$	M_0
0 0 1	$x'y'z$	m_1	$x+y+z'$	M_1
0 1 0	$x'y z'$	m_2	$x+y'+z$	M_2
0 1 1	$x'y z$	m_3	$x+y'+z'$	M_3
1 0 0	$x y'z'$	m_4	$x'+y+z$	M_4
1 0 1	$x y'z$	m_5	$x'+y+z'$	M_5
1 1 0	$x y z'$	m_6	$x'+y'+z$	M_6
1 1 1	$x y z$	m_7	$x'+y'+z'$	M_7

This allows us to represent expressions in either Sum of Products or Product of Sums forms; which are called the standard forms.

Sum of Products: (SOP)

- The sum of products form represents an expression as a sum of minterms.
Standard form Canonical form
- To derive the SOP form from a truth table, OR together all of the minterms which give a value of 1.

Example: Consider the truth table

x	y	z	F1	F2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\Rightarrow F_1 = x'y'z + x'y'z' + xyz \quad \leftarrow \text{SOP form (Standard)}$$

$$= m_1 + m_4 + m_7$$

$$= \sum (1, 4, 7) \quad \leftarrow \text{canonical form}$$

$$F_2 = x'yz + xy'z + xyz' + xyz$$

$$= m_3 + m_5 + m_6 + m_7 = \sum (3, 5, 6, 7)$$

Products of Sums: (POS)

- The POS form represents an expression as a Product of maxterms.
- To derive the POS form from a truth table, AND together all of the maxterms which give a value of 0.

for the above example,

$$F_1 = (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z')(x'+y'+z) \quad \leftarrow \text{POS form (Standard)}$$

$$= M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 \quad \leftarrow \text{canonical form}$$

$$= \prod (0, 2, 3, 5, 6)$$

Important: In fact, we can obtain POS from SOP and vice versa.

For the above example:

$$F_1' = x'y'z' + x'y'z + x'y'z + xy'z + xyz'$$

$$F_1 = (F_1')' = (x'y'z' + x'y'z + x'y'z + xy'z + xyz')'$$

$$= (x'y'z')' \cdot (x'y'z)' \cdot (x'y'z)' \cdot (xy'z)' \cdot (xyz')'$$

$$= (x+y+z) \cdot (x+y'+z) \cdot (x+y'+z') \cdot (x'+y+z') \cdot (x'+y'+z)$$

$$= M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

Example: Consider the truth table;

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\Rightarrow F = x'y'z + xy'z' + xy'z + xyz' + xyz = \sum m(1, 4, 5, 6, 7)$$

$$\text{or } F = (x+y+z) \cdot (x+y'+z) \cdot (x+y'+z') = \prod (0, 2, 3)$$

$$\text{or } F' = x'y'z' + x'y'z + x'y'z$$

$$F = (F')' = (x'y'z' + x'y'z + x'y'z)'$$

$$= (x+y+z) \cdot (x+y'+z) \cdot (x+y'+z')$$

similarly to obtain SOP from POS;

$$\begin{aligned}
 F' &= (x+y+z')(x'+y+z)(x'+y+z')(x'+y'+z)(x'+y'+z') \\
 \Rightarrow F &= (F')' = (x+y+z')' + (x'+y+z)' + (x'+y+z')' + (x'+y'+z)' + (x'+y'+z')' \\
 &= x'y'z + xy'z' + xy'z + xyz' + xyz \\
 &= m_1 + m_4 + m_5 + m_6 + m_7 = \sum(1, 4, 5, 6, 7)
 \end{aligned}$$

Example: Express the function $F = xy + x'z$ in POS form.

$$\begin{aligned}
 F &= xy + x'z \\
 &= xy(z+z') + x'z(y+y') \\
 &= \underbrace{xyz}_{m_7} + \underbrace{xy'z'}_{m_6} + \underbrace{x'y'z}_{m_3} + \underbrace{x'y'z'}_{m_1}
 \end{aligned}$$

$$\begin{aligned}
 F' &= m_0 + m_2 + m_4 + m_5 \\
 &= x'y'z' + x'y'z + xy'z' + xy'z
 \end{aligned}$$

$$\begin{aligned}
 F &= (F')' = (x'y'z')' \cdot (x'y'z)' \cdot (xy'z')' \cdot (xy'z)' \\
 &= \underbrace{(x+y+z)}_{M_0} \cdot \underbrace{(x+y'+z)}_{M_2} \cdot \underbrace{(x'+y+z)}_{M_4} \cdot \underbrace{(x'+y'+z')}_{M_5} = M_0 \cdot M_2 \cdot M_4 \cdot M_5
 \end{aligned}$$

Another solution: form the truth table and proceed!

Exercise!

Example: Express the function: $(AB+CD)(A'B'+C'D')$ in SOP

$$\begin{aligned}
 (AB+CD)(A'B'+C'D') &= \underbrace{ABA'B'}_0 + ABC'D' + A'B'CD + \underbrace{CDC'D'}_0 \\
 &= ABC'D' + A'B'CD
 \end{aligned}$$

Extension to Multiple Inputs:

• AND and OR operations are both commutative and associative:

i.e. $x+y = y+x$; $x \cdot y = y \cdot x$ {commutative}


$(x+y)+z = x+(y+z) = x+y+z$; $(x \cdot y) \cdot z = x \cdot (y \cdot z) = x \cdot y \cdot z$ {associative}

• NAND and NOR functions are commutative, but not associative





$$\begin{aligned}
 \underline{\text{Ex!}} \quad & [(x+y)' + z]' = (x+y) \cdot z' = xz' + yz' \\
 & [x+(y+z)']]' = x' \cdot (y+z) = x'y + x'z
 \end{aligned}
 \quad \Rightarrow \quad ((x+y)' + z)' \neq (x+(y+z)')]'$$

⇒ To overcome the difficulty, define multiple ~~NOR and NAND~~ ^{inputs gates}



$((x+y)' + z)'$ \equiv

 

$(x + (y+z)')'$

    

  • The XOR and XNOR functions are both commutative and associative and they can be extended to more than two inputs.



x	y	z	F = x ⊕ y ⊕ z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Integrated Circuits : (IC) Read 2.8

	⊕		⊕
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	0


The Map Method:

Boolean functions may be simplified by means of the map method which is a simple straightforward procedure. The map method is also known as the "Karnaugh map". It relies on two-dimensional tables where


⊕ Each square represents one minterm. ⊗

Two-variable map:

 
There are four minterms for two variables, hence the map consists of four squares (2x2 table):



 
Example: Consider the function $F_1 = xy$



Example: $F_2 = x + y$


 


Example: $F_3 = (xy)'$

 

Three-variable map.

  
There are eight minterms (squares) for 3 variables, hence the map consists of 8 squares (2x4).



x	y	z	Min terms
0	0	0	x'y'z' m ₀
0	0	1	x'y'z m ₁
0	1	0	x'yz' m ₂
0	1	1	x'yz m ₃
1	0	0	xy'z' m ₄
1	0	1	xy'z m ₅
1	1	0	xyz' m ₆
1	1	1	xyz m ₇

- Note that the combination of yz follows the sequence 00,01,11,10 not the numerical sequence 00,01,10,11. This ensures that adjacent entries in the Karnaugh Map differs only by one variable.
- The map should be considered as being drawn on a surface where edges touch each other. (for example in case of 3 variables map m₀ is adjacent to m₂; m₄ is adjacent to m₆).

 Example: Simplify the Boolean function $F(x,y,z) = \sum(2,3,4,5)$




Main idea: Combine the ^{adjacent} 1's in the largest possible group of power of 2. (overlap may occur).

$\Rightarrow F = x'y + xy'$

Remember (previous chapter):


$$F = x'y'z' + x'y'z + xy'z' + xy'z = x'y(z'+z) + xy'(z'+z) = x'y + xy'$$

 Example: Simplify the Boolean function $F(x,y,z) = \sum(3,4,6,7)$



$\Rightarrow F = xz' + yz$

 Example: Simplify the Boolean function $F(x,y,z) = \sum(0,2,4,5,6)$



- Notes:
- 1 square represents a product term of 3 literals
 - 2 adjacent squares = " " " " 2 literals
 - 4 " " " " " " = one.

$F = z' + xy'$


Example: Given the Boolean function $F = A'C + A'B + AB'C + BC$

- (a) Express F in sum of minterms
- (b) Find the minimal SOP expression

(a)

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$\Rightarrow F = \sum(1, 2, 3, 5, 7)$

 


$\Rightarrow F = C + A'B$

Example: Given the Boolean function $F = x'y' + yz + x'yz'$

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


$\Rightarrow F = \sum(0, 1, 2, 3, 7)$

 

$\Rightarrow F = x' + yz$


Four-Variable Map

 There are 16 minterms for 4 variables, the map has 16 squares (4x4)



- One square represents a term of 4 lit.
 - Two squares = a term of 3 literals
 - Four = = = 2 =
 - Eight = = = 1 =
- (w, x, y, z)

 Example: Simplify the function $F = \sum(1, 3, 4, 5, 10, 12, 13)$



$\Rightarrow F = xy' + wx'z + wx'yz'$

Example:

Simplify $F(A,B,C,D) = \sum(0,2,3,5,6,7,8,10,11,14,15)$

		D			
	CD	00	01	11	10
AB	00	1		1	1
	01		1	1	1
	11			1	1
	10	1		1	1

$\Rightarrow F = C + B'D' + A'BD$

Example: simplify $F = A'B'C' + B'CD' + A'BCD' + AB'C'$

		D			
	CD	00	01	11	10
AB	00	1	1		1
	01				1
	11				
	10	1	1		1

$\Rightarrow F = B'C' + B'D' + A'CD'$

Five-Variable Map

There are 32 minterms for 5 variables organized as two separate 16 squares. (e.g. $F(A,B,C,D,E) \Rightarrow A$ distinguishes between the two four-variable maps).

		E			
	DE	00	01	11	10
BC	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10


A=0

		E			
	DE	00	01	11	10
BC	00	16	17	19	18
	01	20	21	23	22
	11	28	29	31	30
	10	24	25	27	26

A=1


- 1 square represents a product term of 5 literals
- 2 " (s) " " " " 4 =
- 4 " " " " " 3 =
- 8 " " " " " 2 =
- 16 " " " " " 1 =

(a) F in SOP \Rightarrow Combine 1's

 

$$\Rightarrow F = B'C' + B'D' + A'C'D$$

(b) F' in SOP \Rightarrow Combine 0's

 


$$F' = AB + CD + BD'$$


$$\Rightarrow F = (F')' = (AB + CD + BD')' = (A'+B')(C'+D')(B'+D)$$

Assume that the complements of the input variables are available \Rightarrow

$$F = B'C' + B'D' + A'C'D$$

 


$$F = (A'+B')(B'+D)(C'+D')$$

 


Important Note: The procedure for obtaining the POS simplification is also valid when the function is originally expressed in the product of maxterms.

Example: Simplify the function $F(x, y, z) = \prod (0, 2, 5, 7)$ in

(a) SOP and (b) POS

 

$$\Rightarrow F = x'z + xz'$$

 

$$F' = xz + x'z'y$$


$$\Rightarrow F = (F')' = (x+z')(x+z)$$

Note:


In order to enter a function expressed in product of sums in the map, the complement of the function is taken and from F', the squares to be marked with 0's are found.

 Example: Simplify the function $F = (A' + B' + C')(B + D)$ in the two standard forms (i.e. SOP, POS)

Take the complement $F' = ABC + B'D'$ {in order to see where 0's are}




$\Rightarrow F = A'B + BC' + B'D$

 


$F' = ABC + B'D'$
 $\therefore F = (F')' = (A' + B' + C')(B + D)$

Example: Simplify the function $F = (A+B)(A'+B'+C')(A+B+C+D)(A'+B'+C+D)$ in (a) sum of products (b) product of sums.

$F' = A'B' + ABC + A'B'CD' + ABC'D$

 

$\Rightarrow F = AB' + A'B + BC'D'$

 


$F' = A'B' + ABC + ABD$

$\Rightarrow F = (A+B)(A'+B'+C')(A'+B'+D')$

Go to don't care NAND and NOR IMPLEMENTATION:


Digital circuits are more frequently implemented with NAND or NOR gates than AND and OR gates since NAND and NOR are easier to fabricate. Therefore we have to convert other gates to these gates.

Remember:



 


Negative-AND

(i.e. NAND)

 


Negative-OR

   

NAND Implementation:

The implementation of a function with NAND gates requires that the function must be simplified in the sum of products form.

 Example: Implement the function $F = A + BC' + B'CD$ with NAND gates.




Procedure for designing a minimum two-level NAND-NAND logic diagram:

- 1) Simplify the function in sum of products form.
- 2) Draw a NAND gate for each product term that has at least two literals. The literals are the inputs.
- 3) Draw a single NAND gate in the second level, with inputs coming from the outputs of the first-level gates.
- 4) A term with a single literal will be complemented and applied as an



There is a second method to implement a Boolean function with NAND gates: - Express F' in SOP by combining 0's and implement it with two levels NAND gates - Insert an Inverter at the output to obtain F .

 Example: Implement $F(x,y,z) = \sum(0,6)$ with NAND gates




$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

  


 Example:

Implement the function $F(A,B,C,D) = AB' + ABD + ABD' + A'C'D' + A'BC'$ with two-level NAND gate circuit.



$$F = A + BC' + C'D'$$

 

NOR Implementation:

1. Simplify the function in product of sums form.
2. Draw a NOR gate for each sum that has at least two literals.
3. Draw a single NOR gate in the second level, with inputs coming from outputs of first level NOR gates.
4. A term with single literal requires an inverter or may be complemented