

# CMPE 226 Electronics Lab Report

## Experiment # 3

### Thevenin's Theorem


	Std. No	Name	Group	Date
1.	_____	_____	_____	_____
2.	_____	_____	_____	_____
3.	_____	_____	_____	_____

*Aim of the Experiment: To find a method of simplifying a network in order to obtain the current flowing in one particular branch of the network*

**Step1:** Connect the power supply unit to the mains supply line. Ensure that the variable d.c. Control is at minimum. DO NOT switch on yet.

**Step2 :**Connect up the following circuit as below and apply 10V dc from variable supply


**Fig.1**

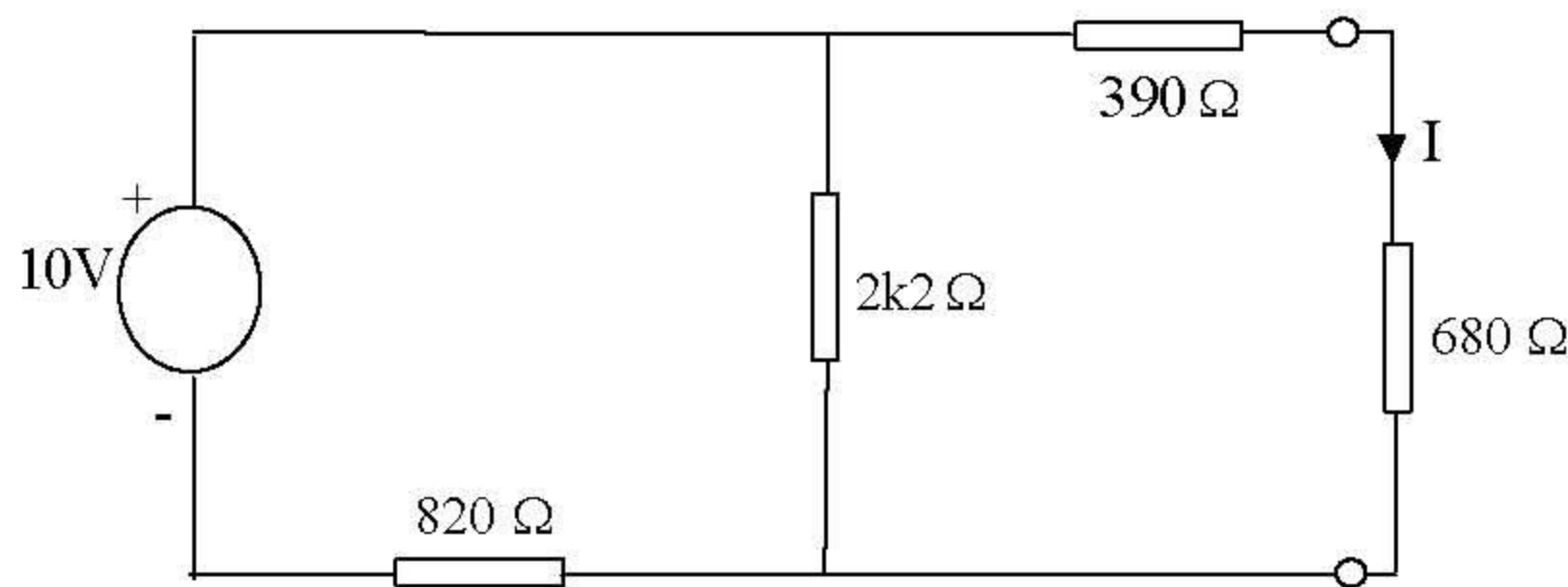

**Step3:** Measure the current in 680 Ω resistor                      I=.....mA

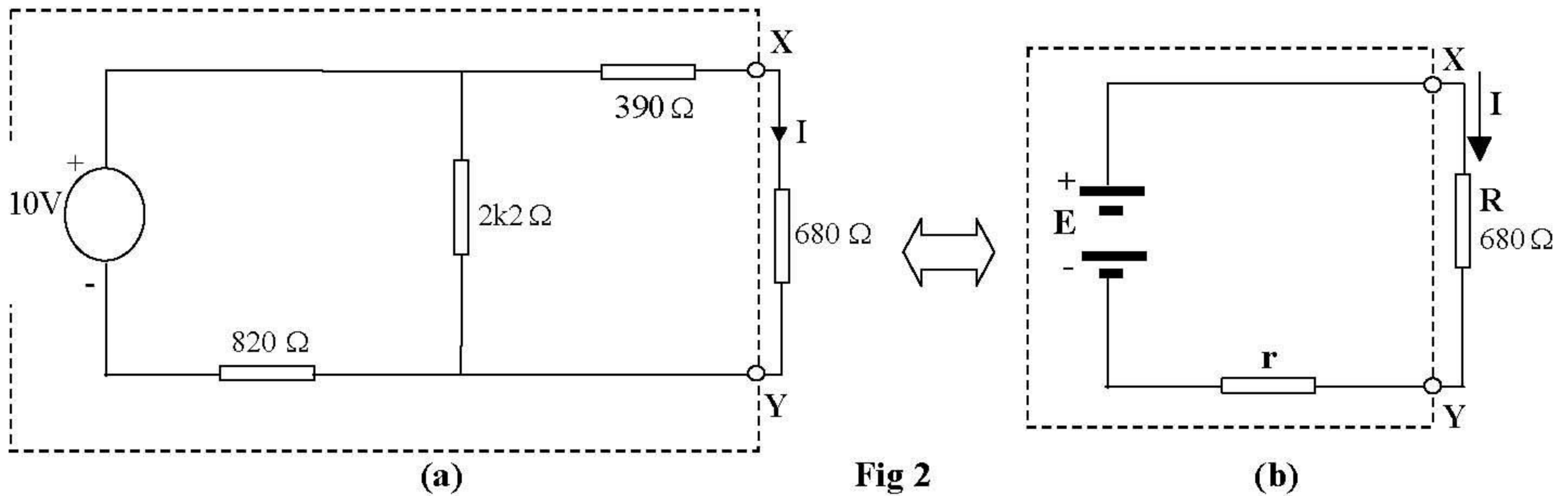**Q1)** Calculate the theoretical value of I using mesh-current law. Does the measured value of current correspond with the calculated value?

**Step4:** Consider the Thevenin equivalent with open-circuited terminals as shown in Fig 2b




**E** represents open circuit voltage of the source, **r** its internal resistance.

**Step5:** Lets us measure open circuit voltage **E** of the source, and its resistance **r**,

- To measure the voltage, disconnect the 680Ω resistor from the circuit, and measure the voltage between **X** and **Y** as shown in Fig2a.

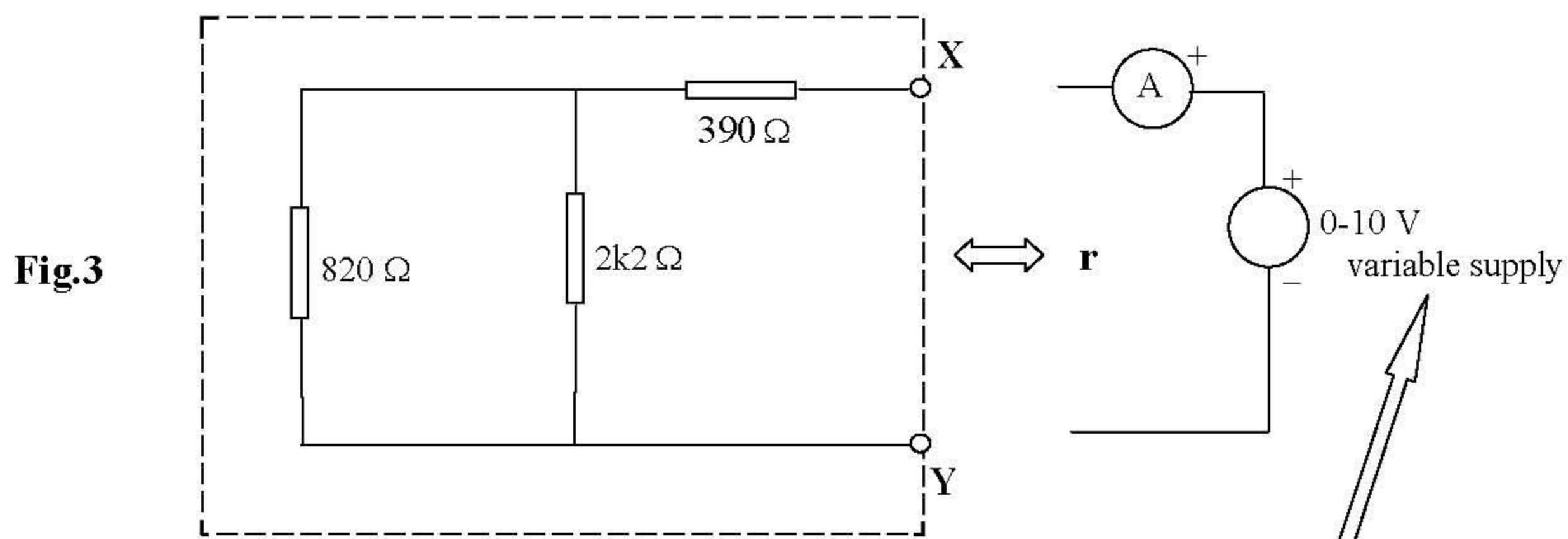**Q2)** The magnitude of **E** was found to be ..... volts?

- Now we wish to determine the internal resistance **r** of the equivalent source. The internal resistance of a source is the resistance seen between the terminals of the source (**X** and **Y** in this case) with the source **E** is removed. This gives the network shown in Fig 3.



**Q3)** The magnitude of **r** was found to be ..... Ω.

Step6) Or the resistance of the above network may be found by connecting a voltages 2V, 4V, 6V and 8V to points **X** and **Y**, and measuring the resultant current, copy these result to following table.

Voltage (V)	Current (mA)	Resistance, $r$ ( $\Omega$ )
2V		
4V		
6V		
8V		
Average value of $r$ =		

It can be seen from Fig2b that required Current  $I$ , can easily be found by dividing the  $E$  by the total resistance

$$I = \frac{E}{R + r} \text{ where } R \text{ is the resistance of required branch}$$

**O4)** Calculate the resistance using Ohm's Law, and take the average of the values is found. (insert the average values to above table)

**O5)** Calculate  $I = \frac{E}{R + r}$  and compare the value with the current measured (in Step3) initially in the 680 $\Omega$  resistor

### **Conclusions**