
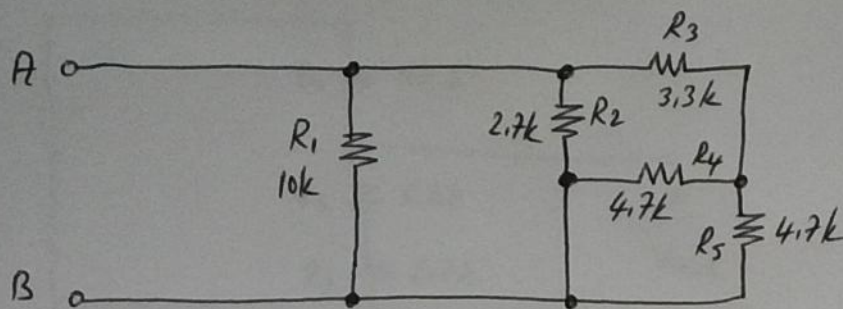


HW #2 - Solutions

10)

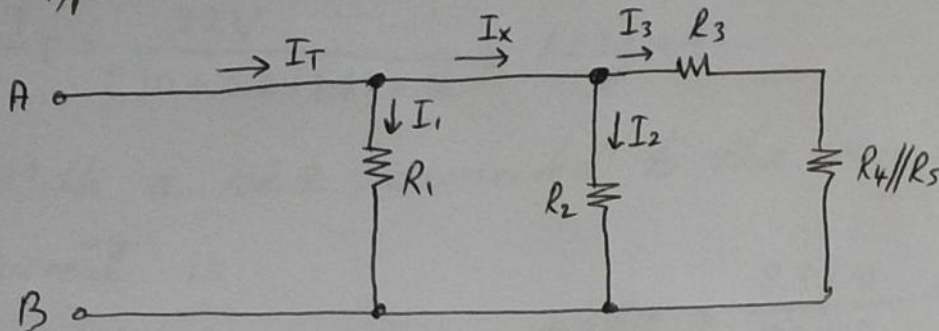

a) $R_4 // R_5 = 2.35 \text{ k}\Omega$




$$R_{3,eq} = R_3 + R_4 // R_5 = 3.3 + 2.35 = 5.65 \text{ k}\Omega$$

$$R_{2,eq} = R_{3,eq} // R_2 = \frac{2.7 \times 5.65}{2.7 + 5.65} = 1.826 \text{ k}\Omega$$

$$R_T = R_1 // R_{2,eq} = \frac{10 \times 1.826}{10 + 1.826} = \underline{\underline{1.544 \text{ k}\Omega}}$$

b)

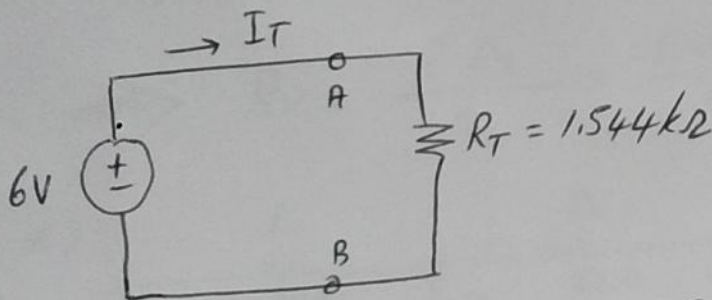

$$I_T = \frac{6V}{1.544 \text{ k}\Omega} = \underline{\underline{3.88 \text{ mA}}}$$

c) $I_1 = \frac{6V}{10 \text{ k}\Omega} = 0.6 \text{ mA}$

$$I_x = I_T - I_1 = 3.88 - 0.6 = 3.28 \text{ mA}$$

$$I_2 = \frac{6V}{2.7 \text{ k}\Omega} = 2.22 \text{ mA}$$


$$I_3 = I_x - I_2 = 3.28 - 2.22 = 1.06 \text{ mA}$$

Current Division

$$I_5 = \frac{R_4}{R_4 + R_5} I_3 = \frac{4.7}{4.7 + 4.7} 1.06 = \underline{\underline{0.53 \text{ mA}}}$$

d) $V_{R_2} = 6V \Rightarrow V_{R_2} = I_2 \times R_2 = \underline{\underline{6V}}$

16)

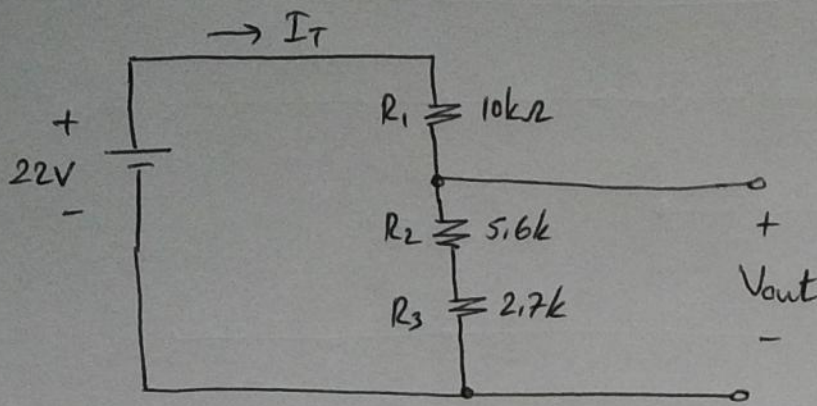

$$I_T = \frac{22V}{(10 + 5.6 + 2.7) k\Omega} = \underline{1.202 mA}$$

With a $10k\Omega$ connected to the terminals, the total current is

$$R_{eq1} = (R_2 + R_3) \parallel 10k\Omega = 8.3 \parallel 10 = \frac{8.3 \times 10}{8.3 + 10} = \underline{4.535 k\Omega}$$

$$R_T = R_1 + R_{eq1} = 10 + 4.535 = \underline{14.535 k\Omega}$$


$$I_T = \frac{22V}{14.535 k\Omega} = \underline{1.513 mA}$$

24)

$R_V R_2 = R_1 R_3$ for a balanced bridge.

$$\Rightarrow R_V = \frac{R_1 R_3}{R_2} = \frac{390 \times 560}{1000} = \underline{218.4 \Omega}$$

28) a)

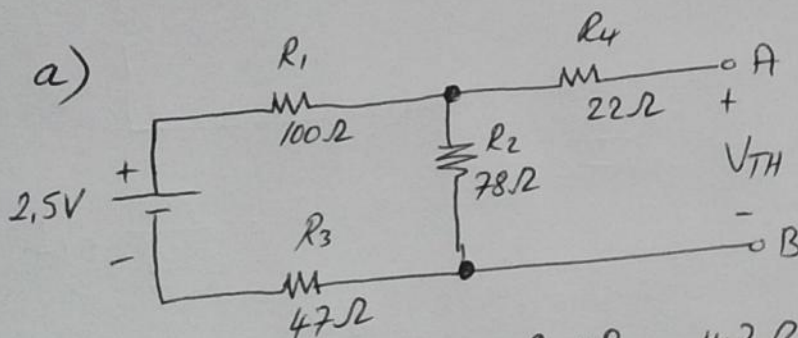


$$V_{TH} = V_{R2} = \frac{78}{100 + 78 + 47} \times 2.5 = \underline{0.867 V}$$

$$R_{TH} = ? \quad (\text{Kill } 2.5V) \quad R_1 + R_3 = 147 \Omega$$


$$(R_1 + R_3) \parallel R_2 = \frac{147 \times 78}{147 + 78} = 50.96 \Omega \quad R_{TH} = R_4 + 50.96 = \underline{72.96 \Omega}$$

Thevenin equivalent $\Rightarrow$

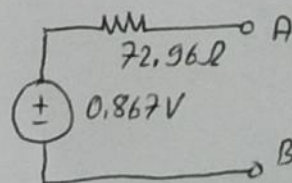

(2)

51) Step 1: Kill 3V

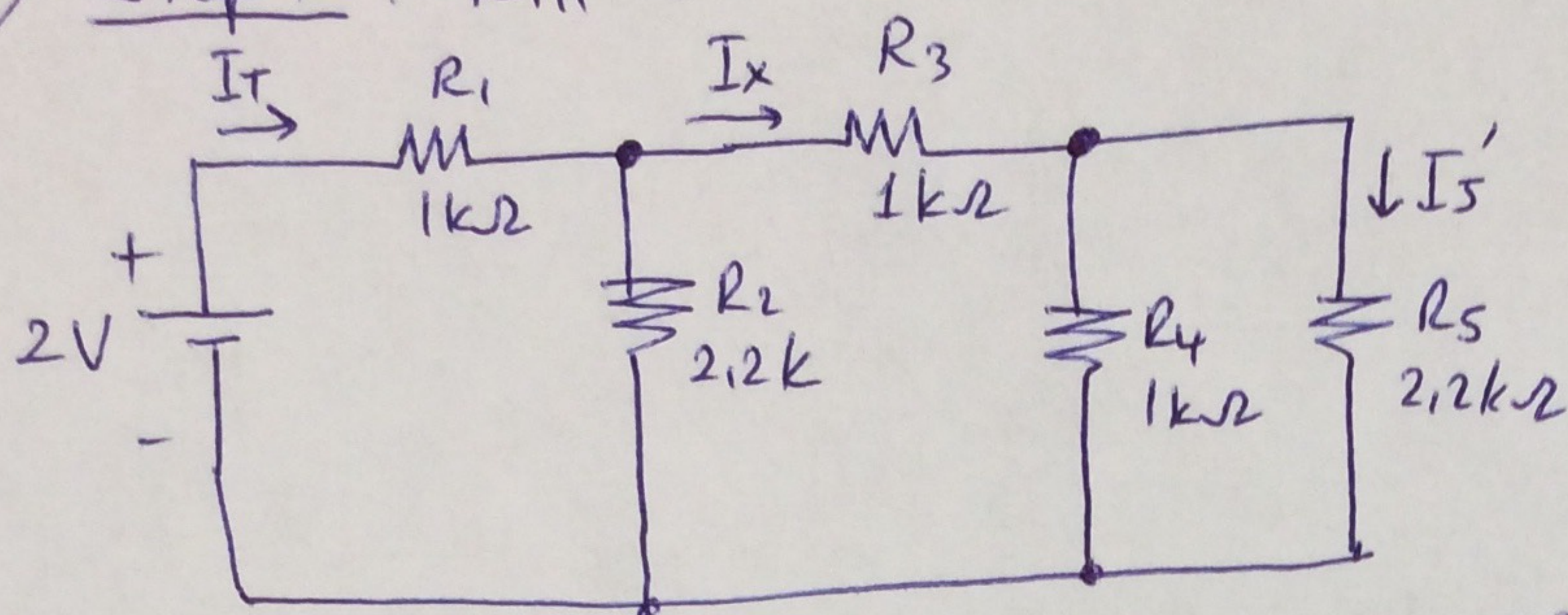

$$R_4 // R_5 = 0.6875 \text{ k}\Omega \quad \Rightarrow \quad R_3 + 0.6875 = 1.6875 \text{ k}\Omega$$

$$R_2 // 1.6875 = 0.955 \text{ k}\Omega \quad \Rightarrow \quad R_T = R_1 + 0.955 \text{ k}\Omega = \underline{\underline{1.955 \text{ k}\Omega}}$$

$$I_T = \frac{2V}{R_T} = \frac{2V}{1.955 \text{ k}\Omega} = 0.511 \text{ mA}$$


$$\text{From current division, } I_X = \frac{R_2}{R_2 + 1.6875} \times I_T = \frac{2.2}{2.2 + 1.6875} \times 0.511$$

$$= \underline{\underline{0.289 \text{ mA}}}$$

$$\text{From current division, } I_{S'} = \frac{R_4}{R_4 + R_5} I_X$$

$$= \frac{1}{1 + 2.2} \times 0.289 = \underline{\underline{0.09 \text{ mA}}}$$

Step 2: Kill 2V

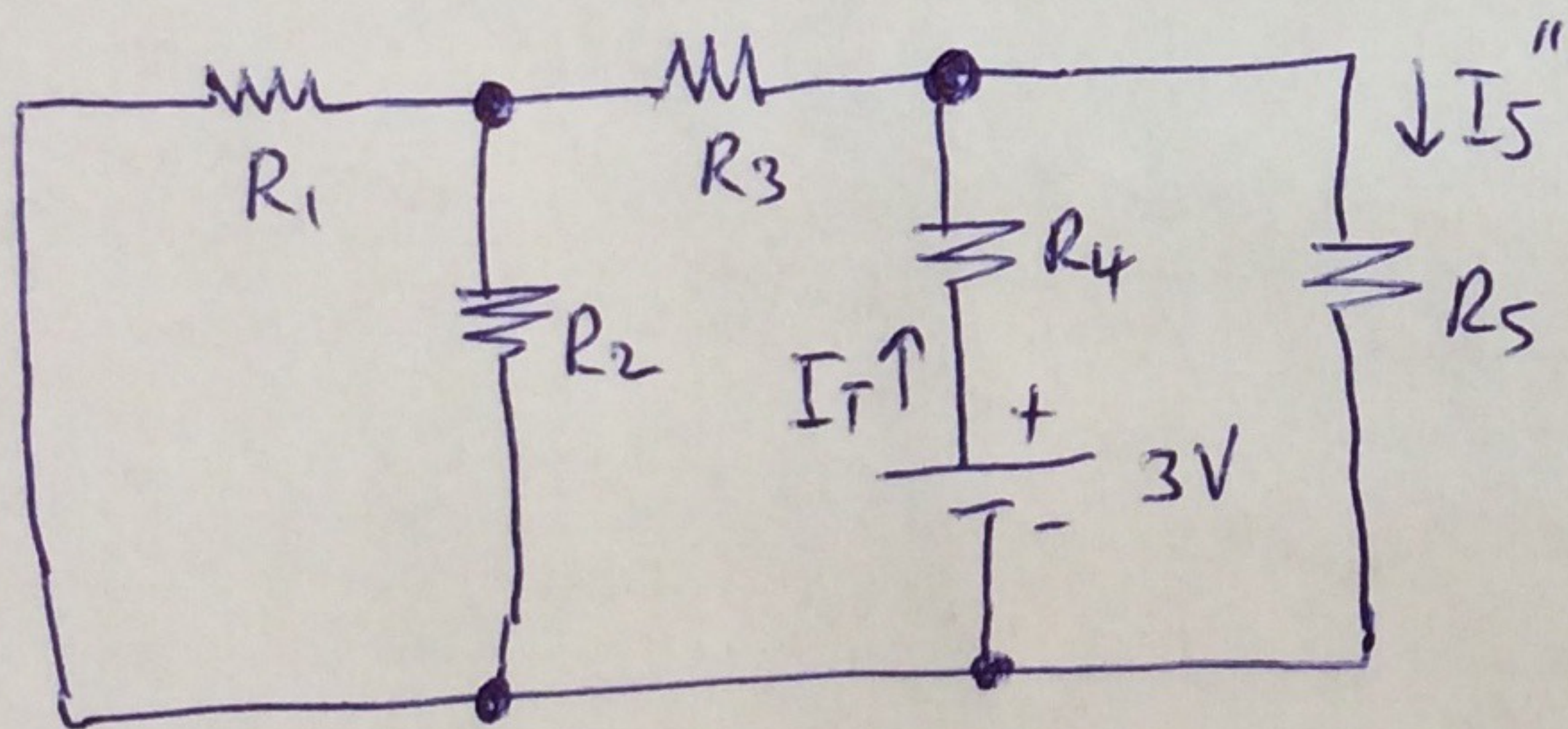

$$R_1 // R_2 = 0.6875 \text{ k}\Omega$$

$$R_3 + 0.6875 = 1.6875 \text{ k}\Omega$$

$$R_5 // 1.6875 = 0.955 \text{ k}\Omega$$

$$R_T = R_4 + 0.955 = 1.955 \text{ k}\Omega$$

$$I_T = \frac{3V}{R_T} = \frac{3V}{1.955 \text{ k}\Omega} = 1.53 \text{ mA}$$

From current division,

$$I_{S''} = \frac{1.6875}{1.6875 + R_5} \times I_T = \underline{\underline{0.66 \text{ mA}}}$$


$$\Rightarrow I_S = I_{S'} + I_{S''} = 0.09 + 0.66 = \underline{\underline{0.75 \text{ mA}}}$$

32) In order to transfer maximum power, the external resistor should be equal to the Thevenin resistance.

$$\Rightarrow R_L = R_{TH} = 72.96 \Omega$$

34) Using superposition, we obtain the following result.

Step 1: Kill 1.5V

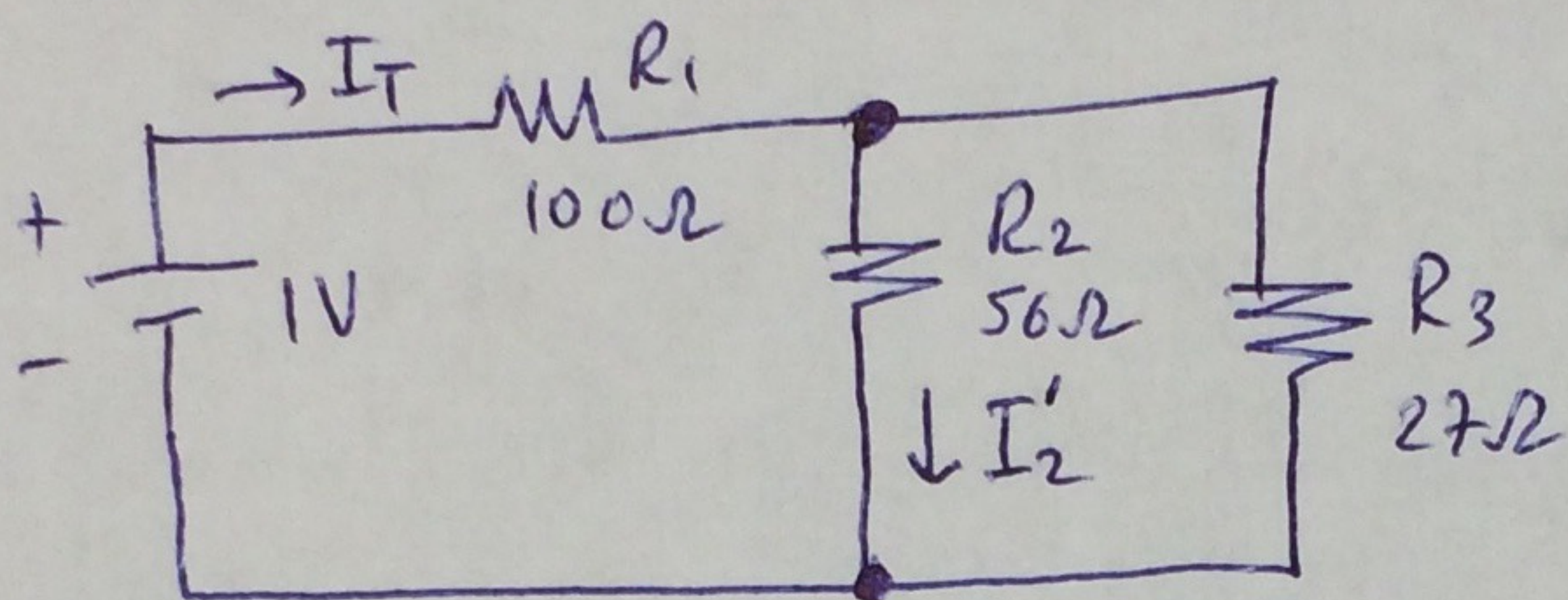

$$R_T = R_1 + R_2 \parallel R_3 = 118.22 \Omega$$


$$I_T = \frac{1V}{118.22 \Omega} = 8.45 \text{ mA}$$

From current division

$$I_2' = \frac{R_3}{R_2 + R_3} I_T$$

$$= \frac{27}{56 + 27} \times 8.45 = 2.75 \text{ mA}$$

Step 2: Kill 1V:

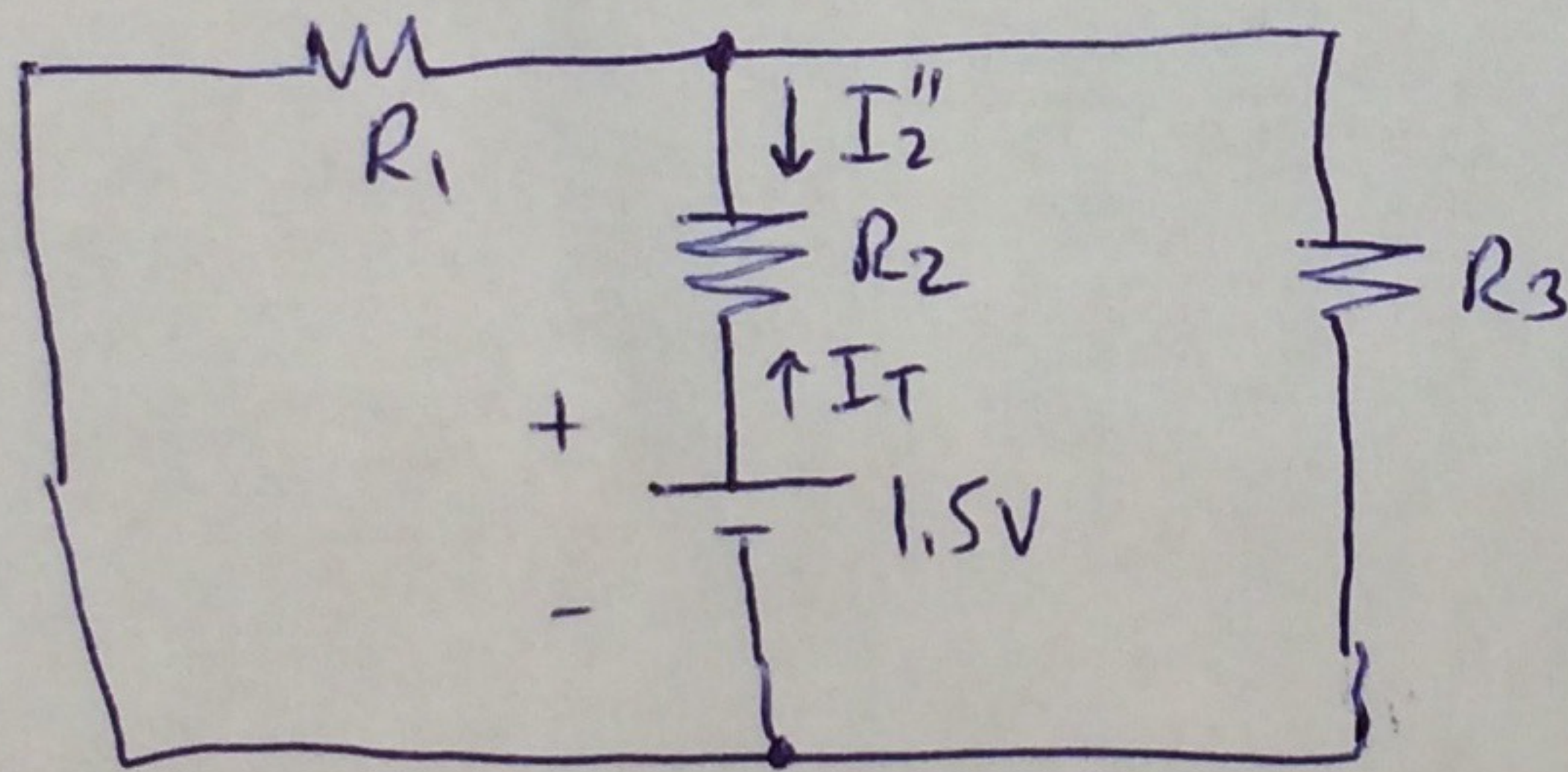

$$R_T = R_2 + R_1 \parallel R_3 = 77.26 \Omega$$


$$I_2'' = -I_T = -\frac{1.5}{R_T} = -19.4 \text{ mA}$$

$$\Rightarrow I_2 = I_2' + I_2'' = 2.75 - 19.4 = -16.65 \text{ mA}$$

HW2 - Solutions

28 b)


Remove R_L

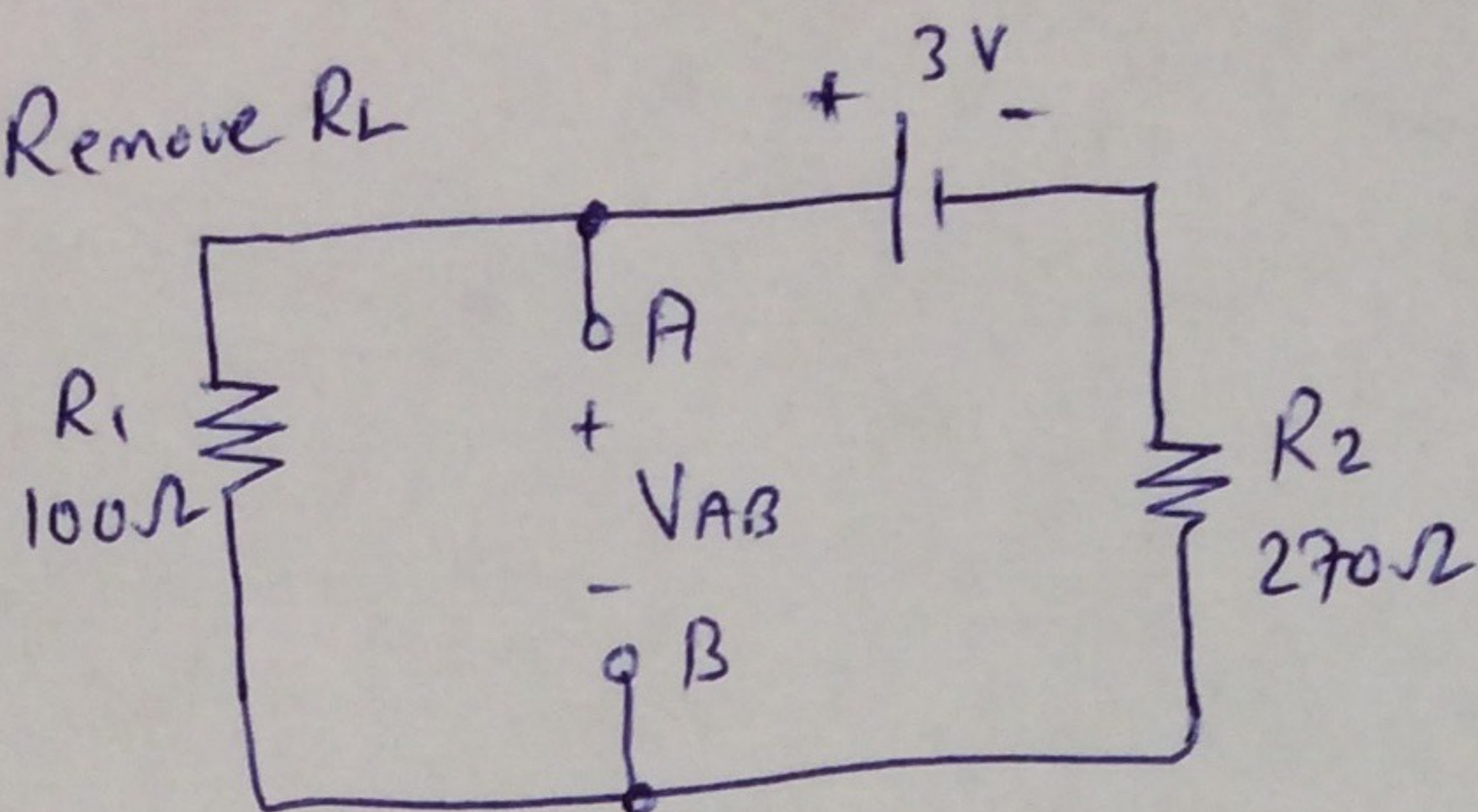

$$V_{AB} = V_{TH} = \frac{R_1}{R_1 + R_2} \times 3$$


$$= \frac{100}{370} \times 3 = 0.81V$$

Kill 3V:

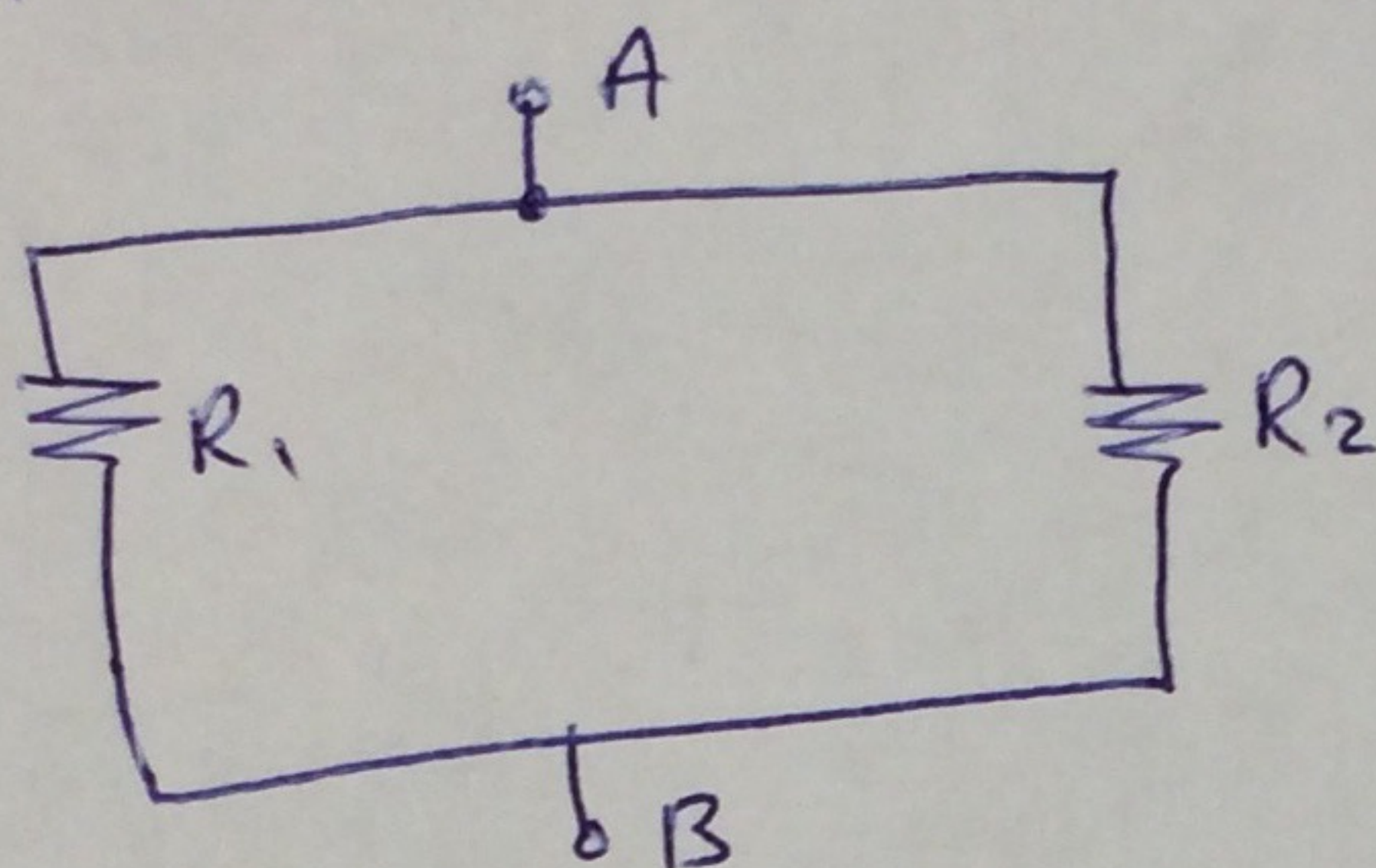


$$R_{TH} = R_1 \parallel R_2 = 72.97\Omega$$

Thevenin equivalent

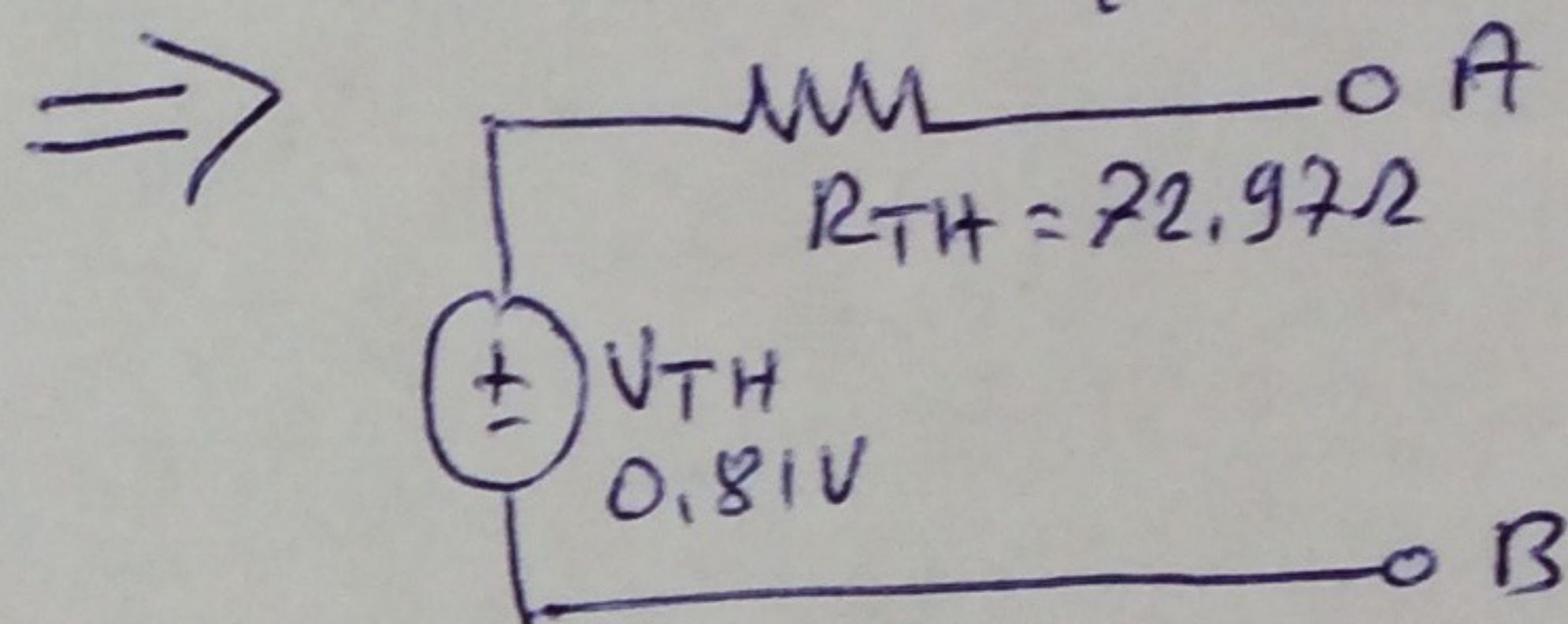


c) Remove R_L

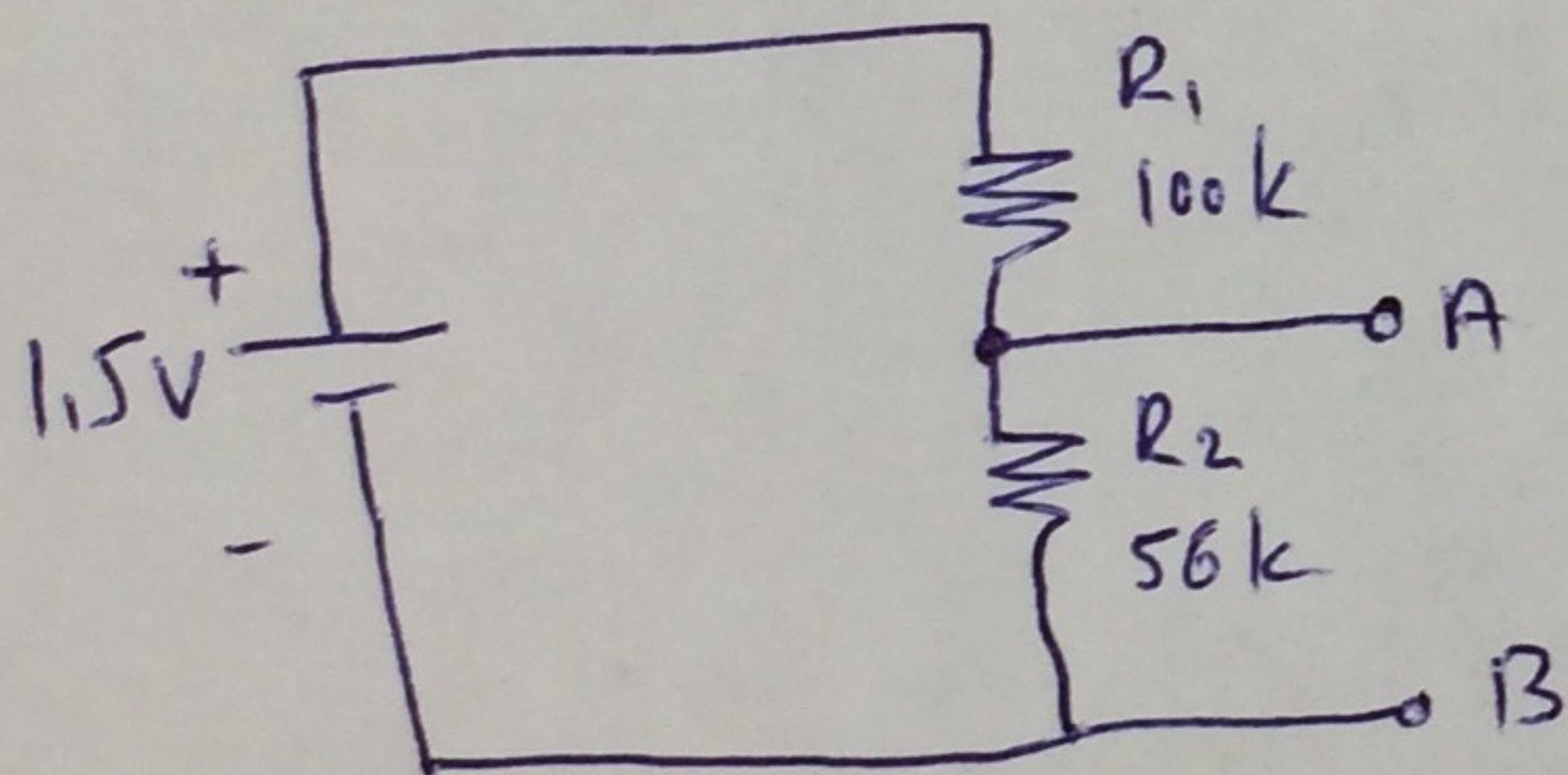

$$V_{AB} = V_{TH} = \frac{R_2}{R_1 + R_2} \times 1.5 = \frac{56}{156} \times 1.5$$

$$= 0.54V$$

Kill 1.5V:

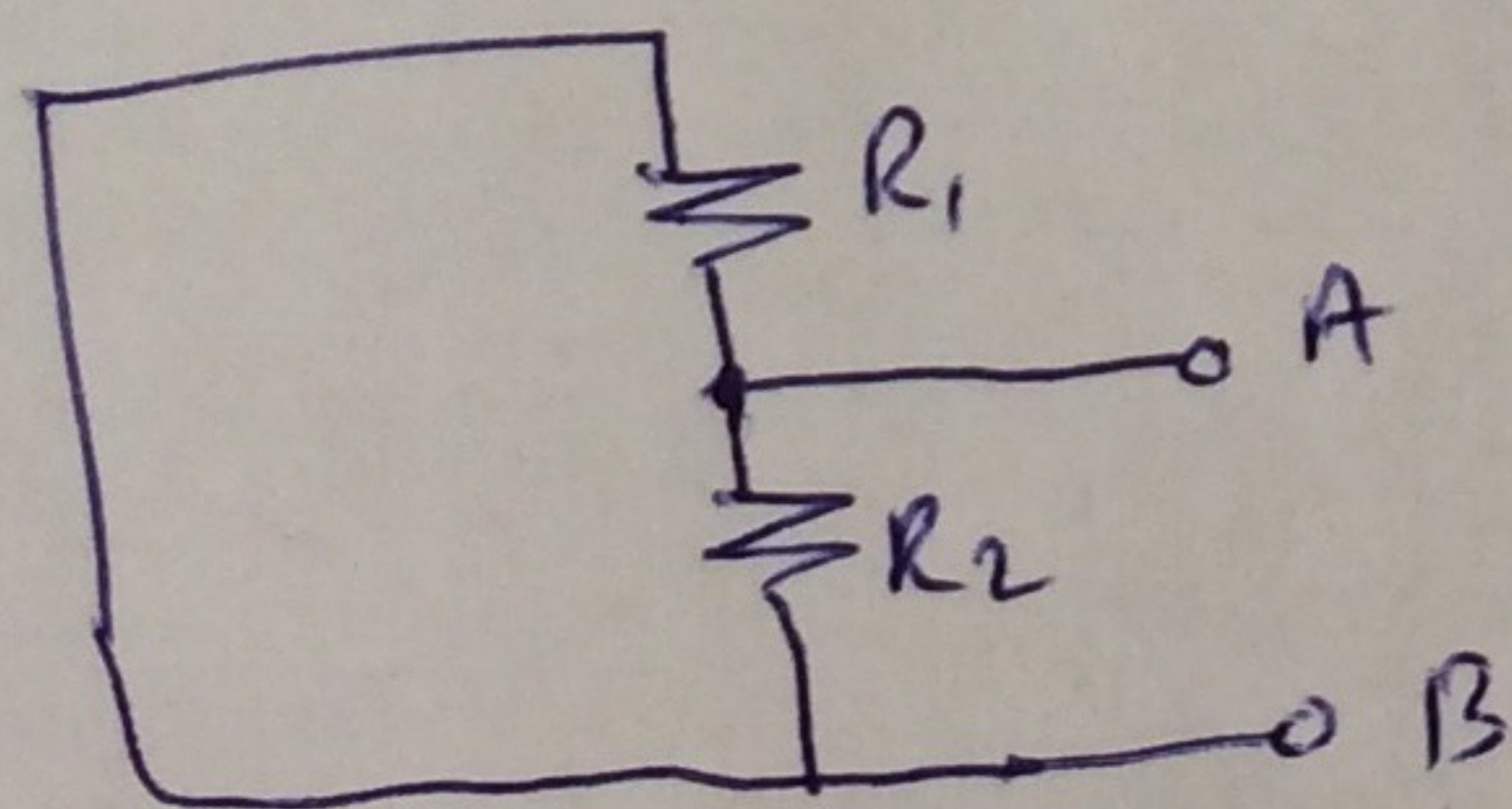

$$R_{TH} = R_1 \parallel R_2 = 35.9k\Omega$$

Thevenin equivalent

