

Homework #1
 - Solutions -


7) a) $R_T = 1k\Omega + 4.7k\Omega + 2.2k\Omega = 7.9k\Omega = 7900\Omega$

b) $R_T = 10\Omega + 10\Omega + 12\Omega + 1\Omega = 33\Omega$

c) $R_T = 1M\Omega + 560k\Omega + 1M\Omega + 680k\Omega + 10M\Omega$
 $= 1 + 0.56 + 1 + 0.68 + 10 = 13.24M\Omega = 13240k\Omega$

10) $R_T = 20k\Omega = R_1 + R_2 + R_3 + R_4 + R_5$
 $= 4.7k\Omega + 1k\Omega + 2.2k\Omega + 3.9k\Omega + R_5$
 $= 11.8k\Omega + R_5$
 $\Rightarrow R_5 = R_T - 11.8k\Omega = 20 - 11.8 = \underline{\underline{8.2k\Omega}}$

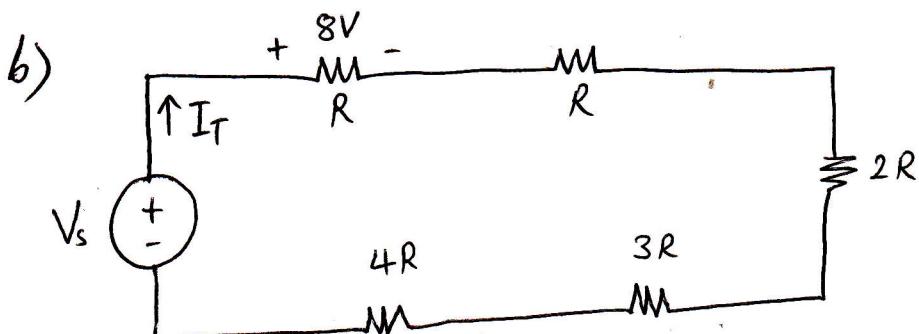23) a) $15V = 2 + V_2 + 3.2 + 1 + 1.5 + 0.5$
 $= 8.2 + V_2 \quad \Rightarrow \quad V_2 = 15 - 8.2 = \underline{\underline{6.8V}}$



The same amount of I_T is passing through all resistors. Therefore
 $V_R = IR = 8V$, $V_{2R} = 16V$, $V_{3R} = 24V$, $V_{4R} = 32V$


$$Vs = V_R + V_R + V_{2R} + V_{3R} + V_{4R} = 8 + 8 + 16 + 24 + 32 \\ = \underline{\underline{88V}}$$

25) a) $V_{AB} = \frac{47}{100+47} \times 12 = \underline{\underline{3.836V}}$

b) $V_{AB} = \frac{2.2+3.3}{1.0+2.2+3.3} \times 8 = \underline{\underline{6.769V}}$

27) a) You are not supposed to solve this question!

b)

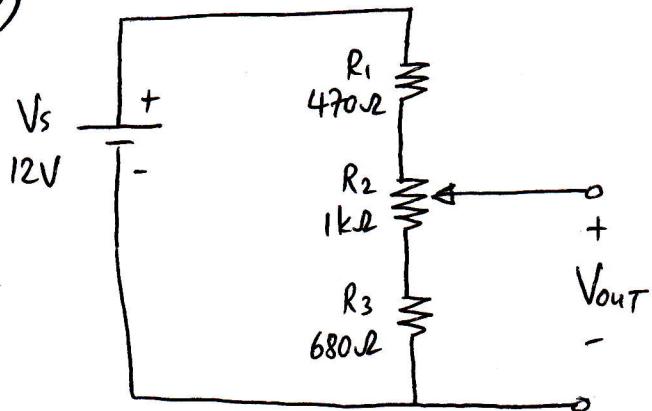

$$V_{out, min} = \frac{R_3}{R_1 + R_2 + R_3} \times V_s$$

$$= \frac{0.68}{0.47 + 1 + 0.68} \times 12 = \underline{\underline{3.795V}}$$

$$V_{out, max} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} V_s$$

$$= \frac{1.68}{0.47 + 1 + 0.68} \times 12 = \underline{\underline{9.376V}}$$

32) $R_T = 5.6 + 5.6 + 1 + 1 = 13.2 \text{ k}\Omega$

$$I_T = \frac{10V}{13.2\text{k}\Omega} = 0.757mA$$

$$V_A = 10V$$

$$V_B = \frac{5.6 + 1 + 1}{R_T} \times 10 = 5.757V$$

$$V_C = \frac{1 + 1}{R_T} \times 10 = 1.515V$$


$$V_D = \frac{1}{R_T} \times 10 = 0.757V$$

$$6) \text{ a)} R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{4,7 \times 2,2}{4,7 + 2,2} = \underline{\underline{1,498 \text{ k}\Omega}}$$

$$\text{b)} R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{27 \times 56}{27 + 56} = \underline{\underline{18,216 \Omega}}$$

$$\text{c)} R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{1,5 \times 2,2}{1,5 + 2,2} = \underline{\underline{0,891 \text{ k}\Omega}}$$

11) a)

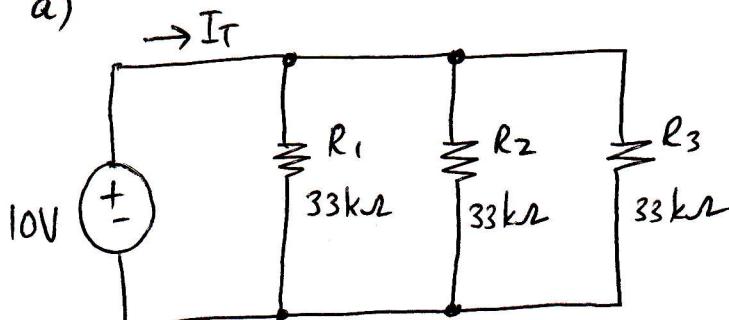


$$R_{eq2,3} = \frac{R_2 R_3}{R_2 + R_3} = \underline{\underline{16,5 \text{ k}\Omega}}$$

$$R_T = \frac{R_1 R_{eq2,3}}{R_1 + R_{eq2,3}} = \frac{16,5 \times 33}{16,5 + 33}$$

$$R_T = \underline{\underline{11 \text{ k}\Omega}}$$

$$I_T = \frac{10V}{R_T} = \frac{10V}{11 \text{ k}\Omega} = \underline{\underline{0,909 \text{ mA}}}$$

b)

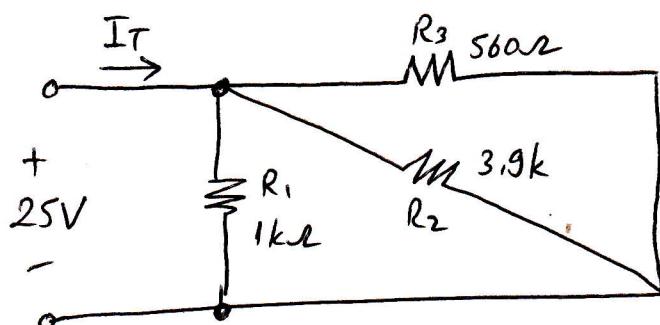

$$R_{2,3} = \frac{R_2 R_3}{R_2 + R_3} = \frac{3.9 \times 560}{3.9 + 560} = \underline{\underline{0.489 \text{ k}\Omega}}$$

$$R_T = \frac{R_1 R_{2,3}}{R_1 + R_{2,3}} = \frac{1 \times 0.489}{1 + 0.489} = \underline{\underline{0.328 \text{ k}\Omega}}$$


$$I_T = \frac{25V}{R_T} = \frac{25V}{0.328 \text{ k}\Omega} = \underline{\underline{76,219 \text{ mA}}}$$

21)

$$A1 = \frac{R_2}{R_1 + R_2} A_3 = \frac{2,7}{1+2,7} \times 3 = \underline{\underline{2,189 \text{ A}}}$$

$$A2 = \frac{R_1}{R_1 + R_2} A_3 = \frac{1}{1+2,7} \times 3 = \underline{\underline{0,81 \text{ A}}}$$

36)

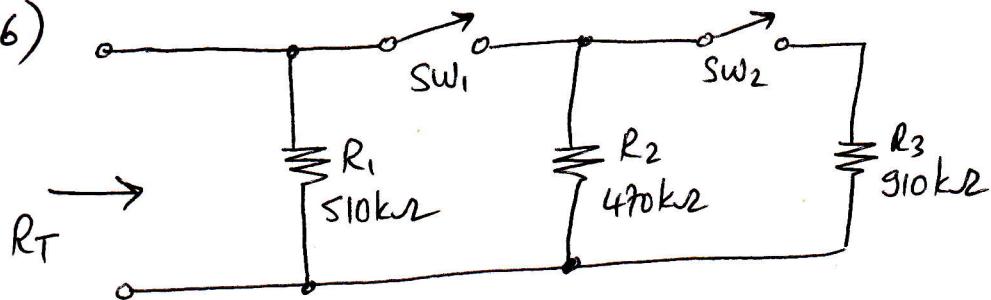

a) $R_T = R_1 = \underline{\underline{510\text{k}\Omega}}$

b) $R_T = \frac{R_1 R_2}{R_1 + R_2} = \underline{\underline{244.59\text{k}\Omega}}$


c) $R_T = R_1 = \underline{\underline{510\text{k}\Omega}}$

$$R_{2,3} = \frac{R_2 R_3}{R_2 + R_3} = 309.92\text{k}\Omega$$

d) $R_T = R_1 // R_2 // R_3$

$$R_T = \frac{R_1 R_{2,3}}{R_1 + R_{2,3}} = \underline{\underline{192.77\text{k}\Omega}}$$

28)

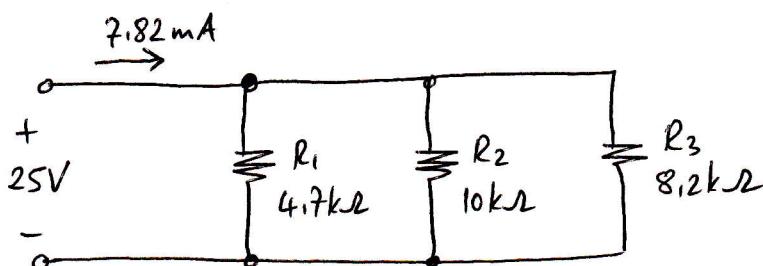

$$R_{2,3} = \frac{R_2 R_3}{R_2 + R_3} = 4.5\text{k}\Omega$$

$$R_T = \frac{R_1 R_{2,3}}{R_1 + R_{2,3}} = 2.298\text{k}\Omega$$


$$I_T = \frac{25\text{V}}{2.298\text{k}\Omega} = 10.879\text{mA} \quad (\text{when all resistors are connected})$$

Clearly, the ampere meter measures 7.82mA which means that one of the resistor is burned out (open circuited)

$$R_{1,2} = \frac{R_1 R_2}{R_1 + R_2} = 3.197\text{k}\Omega \implies I_T = \frac{25\text{V}}{3.197\text{k}\Omega} = 7.82\text{mA}$$

This means that R₃ is open!!

29)

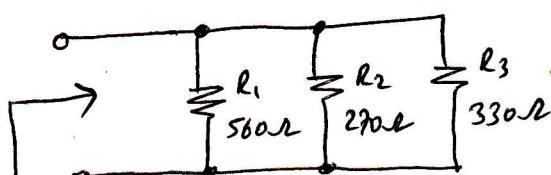

$$R_T = 207.6\text{k}\Omega$$

$$R_{1,2} = \frac{R_1 R_2}{R_1 + R_2} = 182.16\text{k}\Omega$$

$$R_{2,3} = \frac{R_2 R_3}{R_2 + R_3} = 148.5\text{k}\Omega$$

$$R_{1,3} = \frac{R_1 R_3}{R_1 + R_3} = \underline{\underline{207.6\text{k}\Omega}} \implies \text{Therefore, } R_2 \text{ is open.}$$