



**COMPUTER ENGINEERING DEPARTMENT  
CMPE-224 DIGITAL LOGIC SYSTEMS**

**Friday 17/08/2001**


**Q.1) [24 pts]**

A set-dominant flip-flop has set (S) and reset (R) inputs. It differs from a conventional SR flip-flop in that when both S and R are equal to 1, the flip-flop is set.

- a) Obtain the characteristic table of the set-dominant flip-flop.
- b) Draw the state transition diagram of the set-dominant flip-flop.
- c) Obtain the excitation table of the set-dominant flip-flop.
- d) Implement the set-dominant flip-flop using a JK flip-flop and minimum number of gates.

a)

S	R	Q(t+1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	1	Set

 


c)

Q(t)	Q(t+1)	S	R
0	0	0	X
0	1	1	X
1	0	0	1
1	1	X	X

d)

S	R	Q(t)	Q(t+1)	J	K
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	X	1
1	0	0	1	1	X
1	0	1	1	X	0
1	1	0	1	1	X
1	1	1	1	X	0

 
Using K-map (you have to show this):  
J = S, and K = S / R



 **Q.2) [24 pts]**

A sequential circuit has one input  $X$  and one output  $Y$ . The output  $Y$  is equal to 1 if and only if a 3-bit binary number formed by three consecutive bits on  $X$  is divisible by 3 (LSB is applied first). Otherwise, the output  $Y$  is equal to 0. The circuit returns to its initial state after checking the 3-bit binary number.

- Draw your preliminary state transition diagram.
- Find the reduced state table by applying state reduction.
- Make near-optimal state assignments.



b)

PS	NS		Output Y	
	X=0	X=1	X=0	X=1
a	b	c	0	0
b	d	e	0	0
c	f	g	0	0
d	a	a	1	0
e	a	a	0	1
f	a	a	0	0
g	a	a	1	0

- P1 = (abcf) (dg) (e)  
 P2 = (af) (b) (c) (dg) (e)  
 P3 = (a) (f) (b) (c) (dg) (e)

PS	NS		Output Y	
	X=0	X=1	X=0	X=1
a	b	c	0	0
b	d	e	0	0
c	f	d	0	0
d	a	a	1	0
e	a	a	0	1
f	a	a	0	0

Reduced State Table


c)

- d,e are adjacent
- d,f are adjacent
- e,f are adjacent
- b,c are adjacent


d:000	b:001	c:011	f:010
e:100	a:101	----	----

 **Q.3) [30 pts]**

Consider the following 3-bit synchronous counter circuit.



 a) Complete the following timing diagram. (Note that initially  $Q_2Q_1Q_0 = 001$ )




b) Reimplement the above counter using JK flip-flops **ONLY**. Draw the circuit diagram.

b)

Present State			Next State			Flip-Flop inputs					
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>Q2</sub>	K <sub>Q2</sub>	J <sub>Q1</sub>	K <sub>Q1</sub>	J <sub>Q0</sub>	K <sub>Q0</sub>
0	0	1	0	1	1	0	X	1	X	X	0
0	1	1	1	1	1	1	X	X	0	X	0
1	1	1	1	1	0	X	0	X	0	X	1
1	1	0	1	0	0	X	0	X	1	0	X
1	0	0	0	0	1	X	1	0	X	1	X

Using K-map (you have to show this):

 
$$J_{Q2} = Q_2 \quad K_{Q2} = Q_1' \quad J_{Q1} = Q_2' \quad K_{Q1} = Q_0' \quad J_{Q0} = Q_1' \quad K_{Q0} = Q_2$$



 **Q.4) [24 pts]**

Consider the following synchronous sequential circuit that operates in different modes according to the inputs  $S_1S_0$  that are connected in parallel to all Multiplexers selections. Analyze the circuit and fill in the below table.

**Note:** For  $S_1S_0 = 10$  and  $11$  cases, assume that initially  $Q_2Q_1Q_0 = 000$



$S_1$	$S_0$	Circuit Operation
0	0	Complement the outputs
0	1	Shift right
1	0	Even up-counter (0,2,4,6,0,...)
1	1	Johnson counter (000, 001, 011, 111, 110, 100, 000, ...)