

A single-cycle MIPS processor

- An instruction set architecture is an *interface* that defines the hardware operations which are available to software.
- Any instruction set can be implemented in many different ways. Over the next few weeks we'll see several possibilities.
 - In a basic **single-cycle implementation** all operations take the same amount of time—a single cycle.
 - A **multicycle implementation** allows faster operations to take less time than slower ones, so overall performance can be increased.
 - Finally, **pipelining** lets a processor overlap the execution of several instructions, potentially leading to big performance gains.

Single-cycle implementation



- We will describe the implementation a simple MIPS-based instruction set supporting just the following operations.

Arithmetic:	add	sub	and	or	slt
Data Transfer:	lw	sw			
Control:	beq				

- Today we'll build a **single-cycle implementation** of this instruction set.
 - All instructions will execute in the same amount of time; this will determine the clock cycle time for our performance equations.
 - We'll explain the datapath first, and then make the control unit.


Memories

- It's easier to use a **Harvard architecture** at first, with programs and data stored in *separate* memories.
- To fetch instructions and read & write words, we need these memories to be 32-bits wide (buses are represented by dark lines here). We still want byte addressability, so these are $2^{30} \times 32$ memories.
- Blue lines represent control signals. **MemRead** and **MemWrite** should be set to 1 if the **data memory** is to be read or written respectively, and 0 otherwise.
 - When a control signal does something when it is set to 1, we call it **active high** (vs. active low) because 1 is usually a higher voltage than 0.
- For now, we will assume you cannot write to the **instruction memory**.
 - Pretend it's already loaded with a program, which doesn't change while it's running.

  

Instruction fetching

 - The CPU is always in an infinite loop, fetching instructions from memory and executing them.
- The **program counter** or **PC** register holds the address of the current instruction.
- MIPS instructions are each four bytes long, so the PC should be incremented by four to read the next instruction in sequence.



Encoding R-type instructions

- Last lecture, we saw encodings of MIPS instructions as 32-bit values.
- Register-to-register arithmetic instructions use the **R-type** format.
 - **op** is the instruction opcode, and **func** specifies a particular arithmetic operation (see textbook).
 - **rs**, **rt** and **rd** are source and destination registers.


op	rs	rt	rd	shamt	func
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

- An example instruction and its encoding:

add \$s4, \$t1, \$t2 000000 01001 01010 10100 00000 1000000


Registers and ALUs

 - R-type instructions must access registers and an ALU.
- Our **register file** stores thirty-two 32-bit values.
 - Each register specifier is 5 bits long.
 - You can read from two registers at a time.
 - **RegWrite** is 1 if a register should be written.





- Here's a simple **ALU** with five operations, selected by a 3-bit control signal **ALUOp**.

ALUOp	Function
000	and
001	or
010	add
110	subtract
111	slt

 


Executing an R-type instruction

1. Read an instruction from the instruction memory.
2. The source registers, specified by instruction fields *rs* and *rt*, should be read from the register file.
3. The ALU performs the desired operation.
4. Its result is stored in the destination register, which is specified by field *rd* of the instruction word.

  


Encoding I-type instructions

 - The *lw*, *sw* and *beq* instructions all use the *I-type* encoding.
 - *rt* is the *destination* for *lw*, but a *source* for *beq* and *sw*.
 - *address* is a 16-bit signed constant.




- Two example instructions:

 


Accessing data memory

- For an instruction like `lw $t0, -4($sp)`, the base register `$sp` is added to the *sign-extended* constant to get a data memory address.
- This means the ALU must accept *either* a register operand for arithmetic instructions, *or* a sign-extended immediate operand for `lw` and `sw`.
- We'll add a multiplexer, controlled by `ALUSrc`, to select either a register operand (0) or a constant operand (1).

 


MemToReg

- The register file's —Write data|| input has a similar problem. It must be able to store *either* the ALU output of R-type instructions, *or* the data memory output for `lw`.
- We add a mux, controlled by `MemToReg`, to select between saving the ALU result (0) or the data memory output (1) to the registers.

 


RegDst

 - A final annoyance is the destination register of lw is in *rt* instead of *rd*.



lw \$rt, address(\$rs)

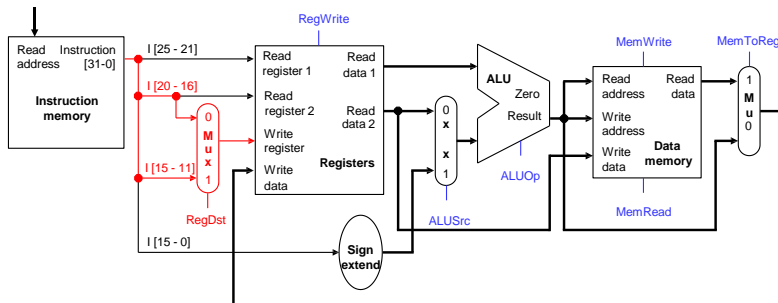- We'll add one more mux, controlled by *RegDst*, to select the destination register from either instruction field *rt* (0) or field *rd* (1).




Branches

- For branch instructions, the constant is not an address but an *instruction offset* from the current program counter to the desired address.

```

beq $at, $0, L
add $v1, $v0, $0
add $v1, $v1, $v1
j   Somewhere
L:  add $v1, $v0, $v0
    
```

 - The target address L is three *instructions* past the *beq*, so the encoding of the branch instruction has 0000 0000 0000 0011 for the address field.




- Instructions are four bytes long, so the actual memory offset is 12 bytes.

The steps in executing a beq


1. Fetch the instruction, like `beq $at, $0, offset`, from memory.
2. Read the source registers, `$at` and `$0`, from the register file.
3. Compare the values by subtracting them in the ALU.
4. If the subtraction result is 0, the source operands were equal and the PC should be loaded with the target address, $PC + 4 + (\text{offset} \times 4)$.
5. Otherwise the branch should not be taken, and the PC should just be incremented to $PC + 4$ to fetch the next instruction sequentially.

Branching hardware

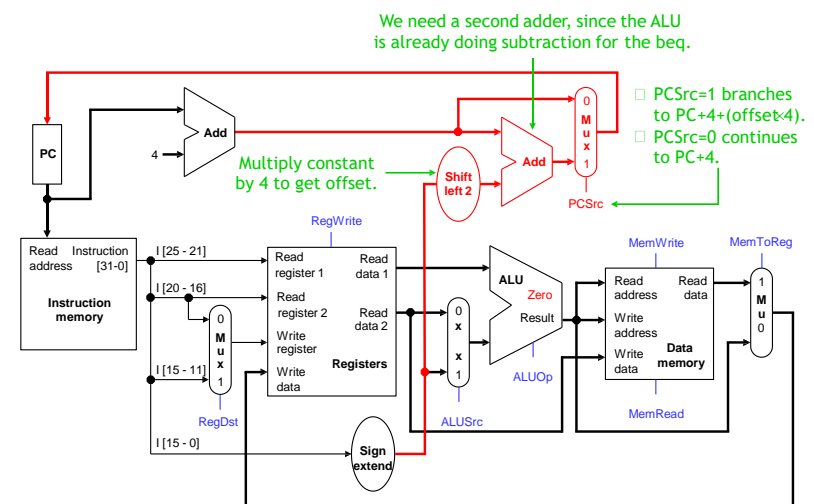


sw instruction path

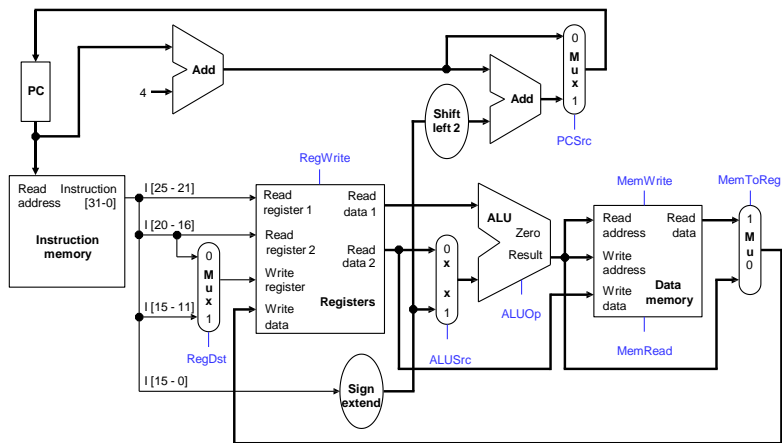- An example store instruction is `sw $a0, 16($sp)`.
- The `ALUOp` must be 010 (add), again to compute the effective address.



beq instruction path

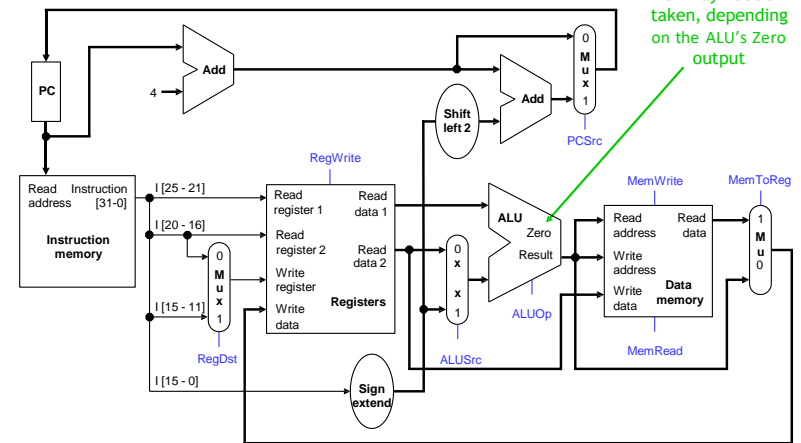- One sample branch instruction is `beq $at, $0, offset`.
- The `ALUOp` is 110 (subtract), to test for equality.




Control signal table

Operation	RegDst	RegWrite	ALUSrc	ALUOp	MemWrite	MemRead	MemToReg
add	1	1	0	010	0	0	0
sub	1	1	0	110	0	0	0
and	1	1	0	000	0	0	0
or	1	1	0	001	0	0	0
slt	1	1	0	111	0	0	0
lw	0	1	1	010	0	1	1
sw	X	0	1	010	1	0	X
beq	X	0	0	110	0	0	X

- **sw** and **beq** are the only instructions that do not write any registers.
- **lw** and **sw** are the only instructions that use the constant field. They also depend on the ALU to compute the effective memory address.
- **ALUOp** for R-type instructions depends on the instructions' func field.
- The **PCSrc** control signal (not listed) should be set if the instruction is **beq** and the ALU's Zero output is true.

Generating control signals


- The control unit needs 13 bits of inputs.
 - Six bits make up the instruction's opcode.
 - Six bits come from the instruction's func field.
 - It also needs the Zero output of the ALU.
- The control unit generates 10 bits of output, corresponding to the signals mentioned on the previous page.
- You can build the actual circuit by using big K-maps, big Boolean algebra, or big circuit design programs.
- The textbook presents a slightly different control unit.

 

The slowest instruction...

- If all instructions must complete within 1 clock cycle, then the cycle time \geq slowest instruction
- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here


reading the instruction memory	2ns	} 8ns
reading the base register \$sp	1ns	
computing memory address \$sp-4	2ns	
reading the data memory	2ns	
storing data back to \$t0	1ns	

 

...determines the clock cycle time

- If we make the cycle time 8ns every instruction will take 8ns, even if they don't need that much time
- For example, the instruction `add $s4, $t1, $t2` really needs just 6ns

reading the instruction memory	2ns	} 6ns
reading registers \$t1 and \$t2	1ns	
computing \$t1 + \$t2	2ns	
storing the result into \$s0	1ns	

 

Summary

A **datapath** contains all the functional units and connections necessary to implement an instruction set architecture

- ❖ For our **single-cycle implementation**, we use two separate memories, an ALU, some extra adders, and lots of multiplexers

- ❖ MIPS is a 32-bit machine, so most of the buses are 32-bits wide

The **control unit** tells the datapath what to do, based on the instruction that's currently being executed

- ❖ Our processor has ten **control signals** that regulate the datapath

- ❖ The control signals can be generated by a combinational circuit with the instruction's 32-bit binary encoding as input

Next, we'll see the performance limitations of this single-cycle machine and try to improve upon it