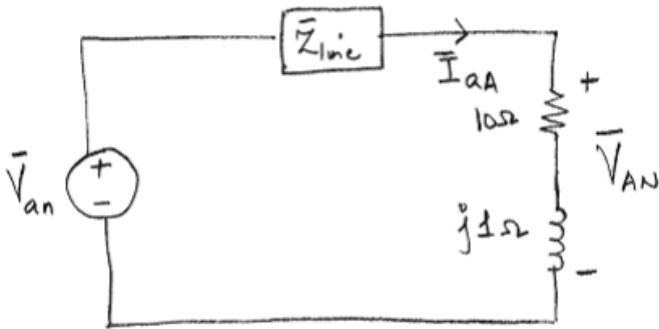


EENG224 HOMEWORK II

1.

In a balanced three phase wye-wye system the load impedance is $10 + j1 \Omega$. The source has phase sequence abc and the line voltage $V_{ab} = 220 \angle 30^\circ \text{ V}_{\text{rms}}$. If the load voltage $V_{AN} = 120 \angle 0^\circ \text{ V}_{\text{rms}}$, determine the line impedance.

Soln.:



$$\bar{Z}_{load} = 10 + j1 \Omega$$

$$\bar{V}_{ab} = 220 \angle 30^\circ \text{ V}_{\text{rms}}$$

$$\bar{V}_{AN} = 120 \angle 0^\circ \text{ V}_{\text{rms}}$$

$$\bar{V}_{an} = \frac{220}{\sqrt{3}} \angle 30^\circ - 30^\circ$$

$$\bar{V}_{an} = 127 \angle 0^\circ \text{ V}_{\text{rms}}$$

$$\bar{I}_{aA} = \frac{120 \angle 0^\circ}{10 + j1} = 11.94 \angle -5.71^\circ \text{ A}_{\text{rms}}$$

$$\text{KVL: } \bar{V}_{an} = \bar{I}_{aA} \bar{Z}_{line} + \bar{V}_{AN}$$


$$\bar{Z}_{line} = \frac{127 \angle 0^\circ - 120 \angle 0^\circ}{11.94 \angle -5.71^\circ}$$

$$\bar{Z}_{line} = 0.59 \angle 5.71^\circ \Omega$$

2.

A three phase abc sequence wye-connected source supplies 14kVA with a power factor 0.75 lagging to a parallel combination of a wye load and a delta load. If the wye load consumes 9 kVA at a power factor of 0.6 lagging and has a phase current of $10 \angle -30^\circ$ A rms determine the phase impedance of delta load.

Soln.:

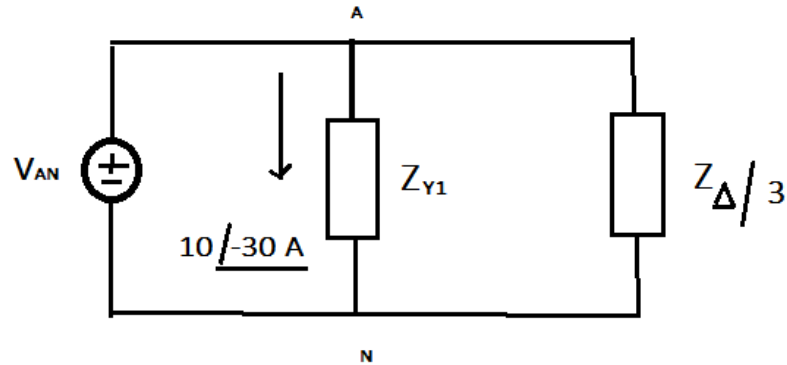

Total complex power is $S_T = 14000 \angle \cos^{-1} 0.75$ VA = $14000 \angle 41.41^\circ$ VA

Wye load complex power is $S_Y = 9000 \angle \cos^{-1} 0.6$ VA = $9000 \angle 53.13^\circ$ VA

Delta load complex power is $S_{\Delta} = S_T - S_Y = 5500 \angle 22^\circ$ VA

Recall that $S_Y = 3 V_{AN} I_{AN}^*$ for Wye load.


$$V_{AN} = \frac{S_Y}{3 I_{AN}^*} = \frac{9000 \angle 53.13^\circ}{30 \angle 30^\circ} = 300 \angle 23.13^\circ \text{ Vrms}$$

Similarly $S_{\Delta} = 3 \frac{V_{AN}^2}{(\frac{Z_{\Delta}}{3})^*} = 9 \frac{V_{AN}^2}{Z_{\Delta}^*}$ From this relation, $Z_{\Delta} = 9 \frac{300^2}{5500 \angle -22^\circ}$

$$Z_{\Delta} = 147.22 \angle 22^\circ \Omega$$

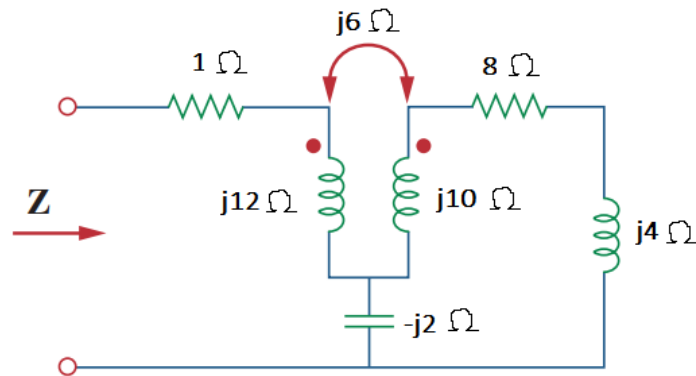
3.

Find the input impedance Z of circuit with transformer shown below.



Soln.:

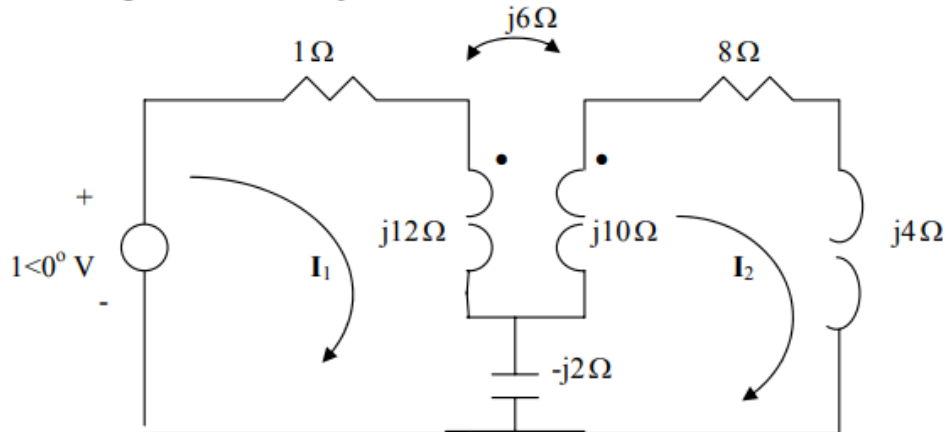Insert a 1-V voltage source at the input as shown below.



For loop 1,

$$1 = (1 + j10)I_1 - j4I_2 \quad (1)$$

For loop 2,


$$0 = (8 + j4 + j10 - j2)I_2 + j2I_1 - j6I_1 \quad \longrightarrow \quad 0 = -jI_1 + (2 + j3)I_2 \quad (2)$$

Solving (1) and (2) leads to $I_1 = 0.019 - j0.1068$

$$Z = \frac{1}{I_1} = 1.6154 + j9.077 = \underline{9.219 \angle 79.91^\circ \Omega}$$

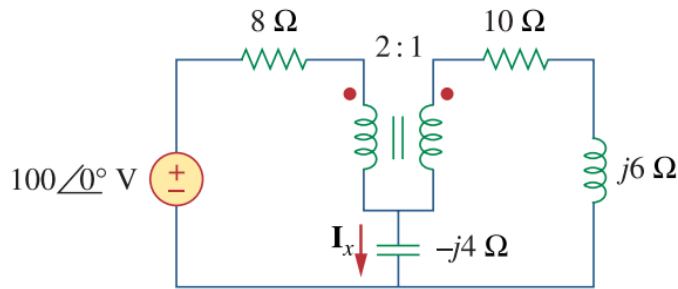
4.

Find I_x in the ideal transformer circuit shown below.



Soln.:

By applying mesh analysis.

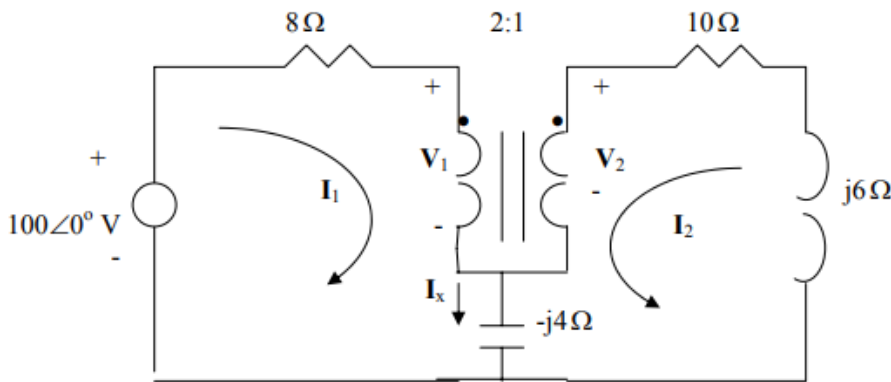

$$100 = (8 - j4)I_1 - j4I_2 + V_1 \quad (1)$$

$$0 = (10 + j2)I_2 - j4I_1 + V_2 \quad (2)$$

$$\frac{V_2}{V_1} = n = \frac{1}{2} \longrightarrow V_1 = 2V_2 \quad (3) \quad \frac{I_2}{I_1} = -\frac{1}{n} = -2 \longrightarrow I_1 = -0.5I_2 \quad (4)$$

Substituting (3) and (4) into (1) and (2),

we obtain

$$100 = (-4 - j2)I_2 + 2V_2$$

$$0 = (10 + j4)I_2 + V_2$$

$$I_2 = -3.5503 + j1.4793$$

$$I_x = I_1 + I_2 = 0.5I_2 = \underline{1.923 \angle 157.4^\circ \text{ A}}$$

