

Q1) [35 points]


Suppose a microprocessor is to control a washing machine using the components: one common-anode 7-segment display unit, one PPI at I/O addresses 400H-403H, and one external switch. The washing machine contains some devices which have to be controlled: WATER VALVE, HEATER, DRAIN PUMP, MAIN MOTOR. The main motor has two speeds in order to allow it to wash and spin. There are three micro-switches in the washing machine which generate 3-bit binary data for each of the four devices according to the following truth table:

MS ₂	MS ₁	MS ₀		Valve Open		Heat On		Motor		Pump On
				Fast	Slow	Fast	Slow			
0	0	0	READY	0	0	0	0	0	0	0
0	0	1	FILL	1	0	0	0	0	0	0
0	1	0	HEAT	0	1	0	0	0	0	0
0	1	1	WASH	0	0	0	1	0	0	0
1	0	0	DRAIN	0	0	0	0	0	0	1
1	0	1	RINSE	1	0	0	1	0	0	0
1	1	0	DRAIN	0	0	0	0	0	0	1
1	1	1	SPIN	0	0	1	0	0	0	0

It is required to display the following message on the 7-segment unit:

When user wants the washing machine to spin (SW is closed) → display 5 on the display unit.

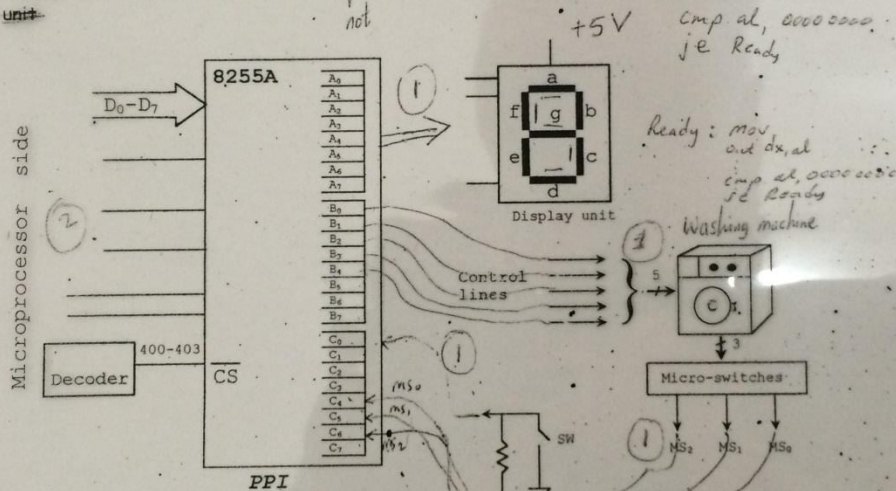When user wants the washing machine to spin (SW is open) → nothing is displayed on the display unit.



- Give the complete hardware configuration of your design. Show all connections and control signals in details.
- Write a complete assembly language program to fulfill the above requirements. Write comments where necessary.

Note1: The command register format of the PPI is:

1	0	0	A	Ch	0	B	C	1
---	---	---	---	----	---	---	---	---

 1=input, 0=output

Note2: The display word format is:

x	a	b	c	d	e	f	g
1	0	1	0	0	1	0	0

 1=OFF, 0=ON

5-bit data control into the data segment and use 3-bit binary data to take them from data segment.

Q1) b)

Completely working = 5

```

DOSSEG
.Model Small
.Data
(2) mov dx, 403h
(2) mov al, 10001001B
(2) out dx, al
(2) dec dx
(3) in al, dx
(3) mov dx, 400h
(3) xor bl, bl
(3) and al, 00000001B
(3) cmp al, 01
(3) je No_spin
(3) mov al, 0A4h ;display S
(3) out dx, al
(3) mov bl, 1
(3) jmp Ready
No_spin: mov al, 0FFh ;dark display
(3) out dx, al
Ready: inc dx mov dx, 401h mov dx, 401h
(2) inc dx 402
(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 00000000B
(2) je Ready
Fill: dec dx
(2) mov al, 10h
(2) out dx, al
(2) inc dx
(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 00010000B
(2) je Fill
Heat: dec dx
(2) mov al, 08h
(2) out dx, al
(2) inc dx
(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 00100000B
(2) je Heat
Wash: dec dx
(2) mov al, 02h
(2) out dx, al
(2) inc dx

```


```

(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 00110000B
(2) je Wash
Drain1: dec dx
(2) mov al, 01h
(2) out dx, al
(2) inc dx
(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 01000000B
(2) je Drain1
Rinse: dec dx
(2) mov al, 12h
(2) out dx, al
(2) inc dx
(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 01010000B
(2) je Rinse
Drain2: dec dx
(2) mov al, 01h
(2) out dx, al
(2) inc dx
(2) in al, dx
(2) and al, 01110000B
(2) cmp al, 01100000B
(2) je Drain2
Spin: cmp bl, 1
(2) jne Stop
(2) mov al, 04h
(2) out dx, al
Stop: mov al, 4Ch
(2) int 21h
(2) end

```


Q.3) [35 pts]

Consider the following system.

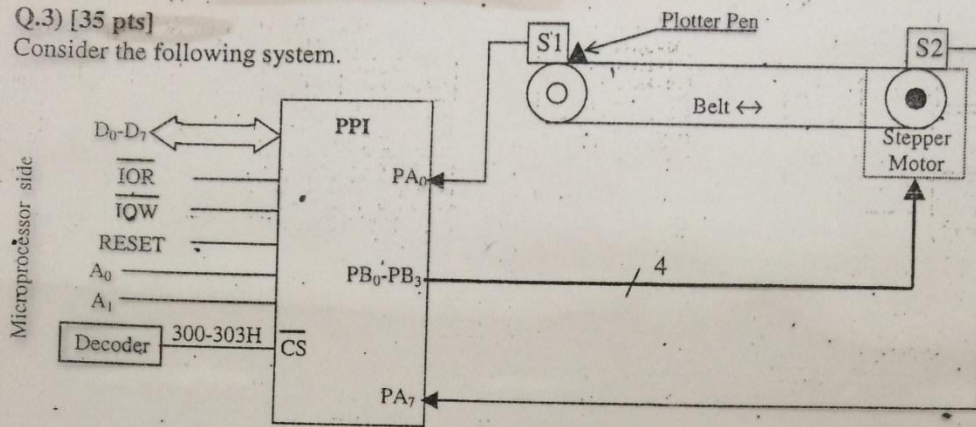

In this system the rotor of the stepper motor is mounted to a belt on which a plotter pen is connected. The plotter pen moves left when the stepper motor rotates counter clockwise, and moves right when the stepper motor rotates clockwise. There are two identical switches (S₁ and S₂) on both sides that are used for end detection.

- A switch normally gives an output of 0 volts. As long as the plotter pen touches a switch, it gives 5 volts.
- A 1 ms delay subroutine called DELAY is available (you don't have to write it).
- The I/O port addresses of the PPI are 300H-303H.
- Initially, assume the plotter pen is touching S₁.
- Although not important, assume the motor rotates 1 degree per step.

You are required to write a complete assembly program that will move the plotter pen from left-to-right then right-to-left 50 times, with a delay of 2 ms between successive steps.

[Your grade will be inversely proportional with the length of your program]

Q.3 Solution)

```
DOSSEG
.Model      small
.Code
mov  dx,303h
mov  al,10010000B ;PortA input, PortB output
out  dx,al
mov  bl,11001100 ;initial pattern
mov  cx,50       ;initialize counter

Right:
mov  dx,301
ror  bl,1       ;move to the right
mov  al,bl
out  dx,al
call Delay
call Delay     ;wait for 2 ms between steps
dec  dx
in   al,dx     ;read PortA
shl  al,1      ;check whether you reached S2
jnc  Right     ;if not, continue moving right


Left:
inc  dx
rol  bl,1      ;move to the left
mov  al,bl
out  dx,al
call Delay
call Delay     ;wait for 2 ms between steps
dec  dx
in   al,dx     ;read PortA
shr  al,1      ;check whether you reached S1
jnc  Left      ;if not continue moving left
loop Right     ;one turn is completed
mov  ah,4ch
int  21h
END
```

Good Luck in the Final Exam...



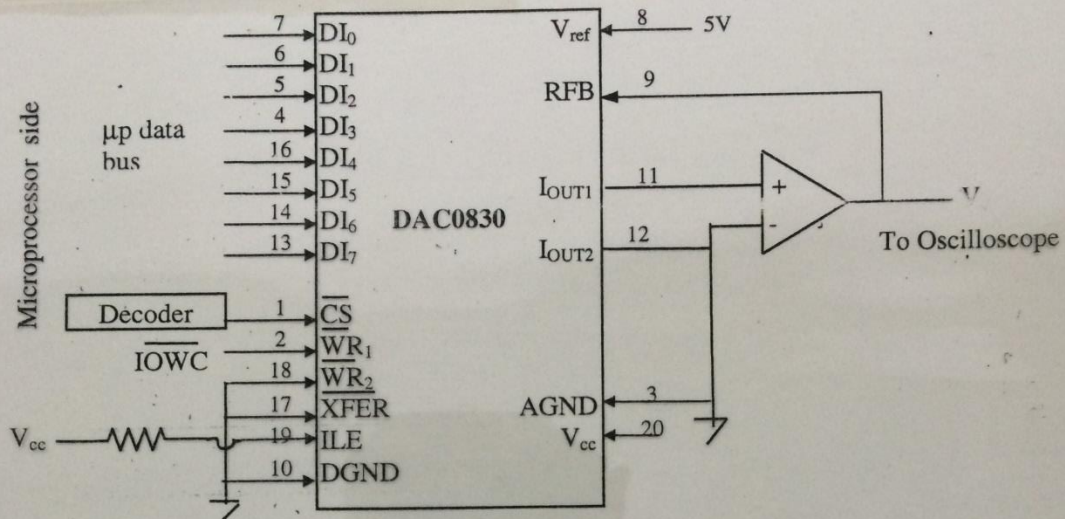Q.4) [20 pts]

The following digital-to-analog converter DAC0830 is interfaced to an 80x86 μ p system at I/O port address 700H as shown below.



The program given below is run.

```


DOSSEG
.MODEL small
.CODE
mov dx, 700h
mov al, 0
Loop1: out dx, al
      call Delay
      inc al
      cmp al, 0FFh
      jb Loop1
      mov bl, 0FFh
Loop2: out dx, al
      call Delay
      dec bl
      jne Loop2
      inc al
      jmp Loop1

Delay: ... ; 2  $\mu$ sec delay
      ret

mov ah, 4ch
int 21h
END
    
```

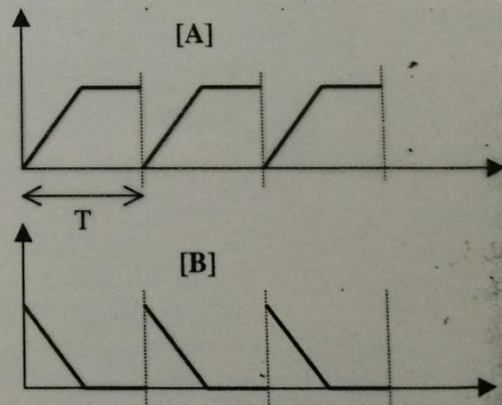a) [15 pts]

Draw the analog waveform that will be seen on the Oscilloscope while running this program.



b) [5 pts]


Approximately, what is the frequency of this waveform?

$$T = 2 \times 256 \times 2 = 1024 \mu\text{s}$$

$$F = 1/T = 1/1024 \mu\text{s} = 976.6 \text{ Hz} \approx 1 \text{ KHz}$$

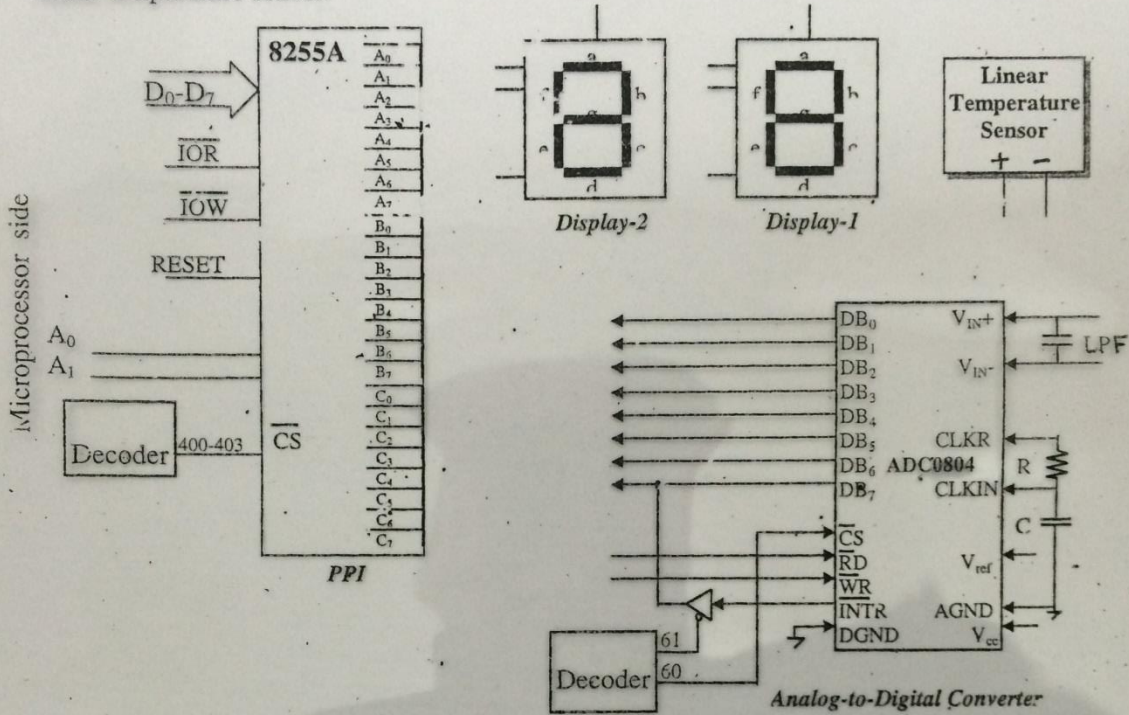Q.3) [23 pts]

You are given the following components: Two common-anode 7-segment displays. One PPI at I/O addresses 400H-403H. One ADC at I/O addresses 60H and 61H, and one linear temperature sensor.



Assume that V_{ref} is set to a value that satisfies the following table:

Temperature To be displayed ($^{\circ}C$)	V_{IN} (mV)	Binary output
00	0	0000 0000
01	10	0000 0001
02	20	0000 0010
03	30	0000 0011
.....
99	990	0110 0011

You are required to interface the above components to an 80x86 μ p to continuously display the currently measured temperature in BCD form on the 7-segment displays.

- a) [8 pts] Give the complete hardware configuration of your design.
- b) [15 pts] Write a complete assembly program to fulfill the above requirements. Write comments where necessary. (Your grade will be inversely proportional to the length of your program)


Note1: The command register format of the PPI is:

1	0	0	A	Ch	0	B	Cl
---	---	---	---	----	---	---	----

 1= input, 0=output

Note2: The display word format is: x a b c d e f g 1=OFF, 0=ON

Q.3) [23 pts]
 a) [8 pts]

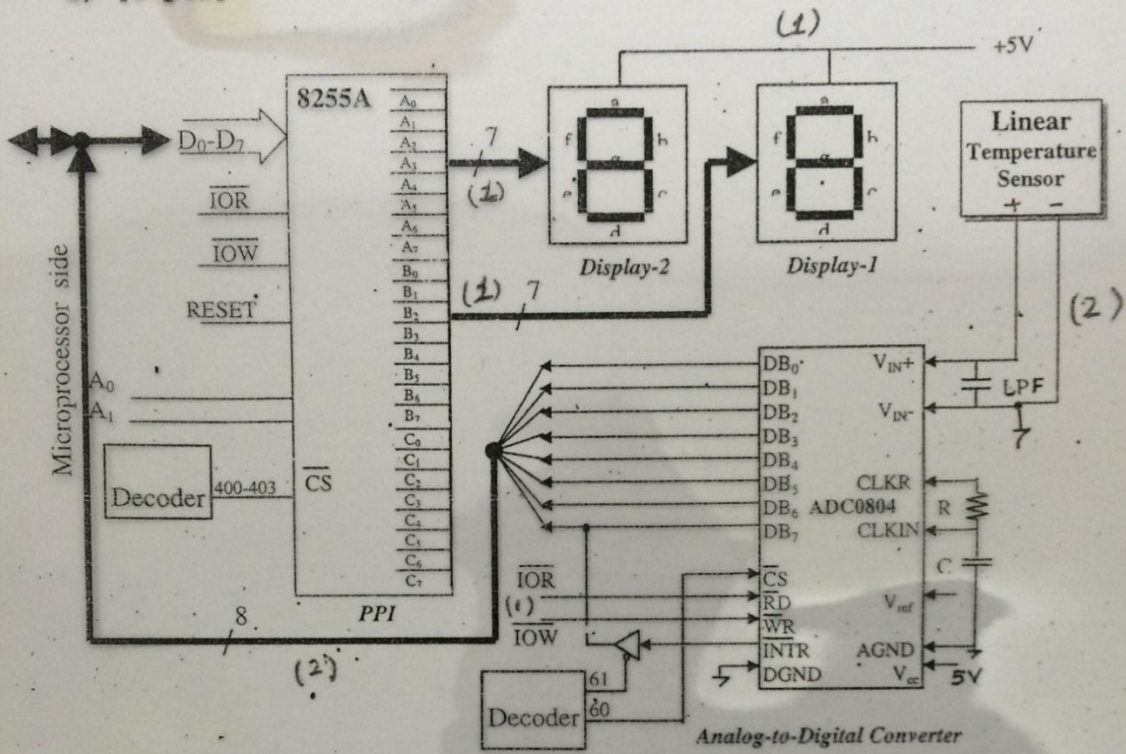

b) [15 pts]

```

Dosseg
.Model small
.Stack 100
.386
.Code
    jmp     Start
1 LUT: DB 81h,CFh,92h, ...;display words of 0-9
    Begin: mov     dx,403h
        2 ( mov     al,10000000B ;PortA and PortB are outputs
          out     dx,al
Start:  out     60h,al           ;start conversion
notyet: in      al,61h         ;read INTR
        3 ( test     al,80h         ;conversion finished ?
          jnz     notyet       ;poll until INTR=0
          in     al,60h         ;get temperature from the ADC
        1 ( add     al,0         ;convert the read temperature
          daa                    ;to BCD

          push   ax             ;save the two BCD numbers
          xor   bh,bh           ;use bx as index
        4 ( mov     bl,al
          and   bl,0Fh         ;prepare the first BCD digit and
          mov   al,byte ptr CS:[offset LUT+bx] ;get its display word
          mov   dx,401h        ;display, the first digit
          out   dx,al          ;on PortB

          pop   ax
          mov   bl,al
        4 ( shr     bl,4         ;prepare the second BCD digit and
          mov   al,byte ptr CS:[offset LUT+bx] ;get its display word
          dec   dx             ;display the second digit
          out   dx,al         ;on PortA
          jmp   Start

          mov   ax,4ch         ;leave control to DOS
          int  21h
          END
```